


Lecture 9 Multiplexer, Decoder, and PLD

- SSI (small-scale integration)
 - NAND, NOR, NOT, flip flop etc
 - Gate count < 10 .
- MSI (medium-scale integration)
 - Adders, multiplexers, decoders, registers, counters
 - Gate count < 100
- LSI
- VLSI (very large-scale integration)
 - Memory chips, microprocessors

Multiplexers


- Multiplexers are selectors.
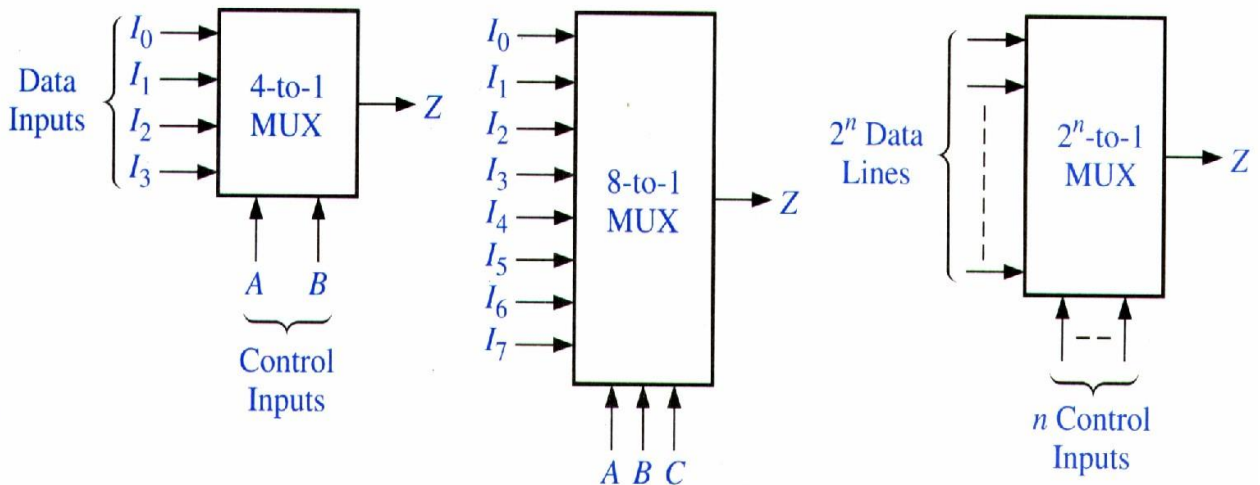
$$Z = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3. \text{ (4-to-1 MUX)}$$




Logic Diagram for MUX

- 8-to-1 MUX

 

Application of MUX


- Select data.

 


Application of MUX

Crossbar switch

 - As $s=0$, x_1 to y_1 , x_2 to y_2 .
- As $s=1$, x_1 to y_2 , x_2 to y_1 .



(a) A 2x2 crossbar switch

 


(b) Implementation using multiplexers

Using Mux for logic function, XOR

- $f = w_1 \text{ xor } w_2$


w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 

Better

- Modify the truth table.
- When $w_1 = 0$, $f = w_2$. Otherwise, $f = \sim w_2$


w_1	w_2	f		w_1	f
0	0	0	}	0	w_2
0	1	1			
1	0	1	}	1	$\overline{w_2}$
1	1	0			

 

Using Mux to Implement a barrel shifter

s_1	s_0	y_3	y_2	y_1	y_0
0	0	w_3	w_2	w_1	w_0
0	1	w_0	w_3	w_2	w_1
1	0	w_1	w_0	w_3	w_2
1	1	w_2	w_1	w_0	w_3



(a) Truth table

 

(b) Circuit


Buffers/Tri-state Buffer

- Driving capability
- High impedance

  



Tri-state Buffer Application

- Data transfer between registers

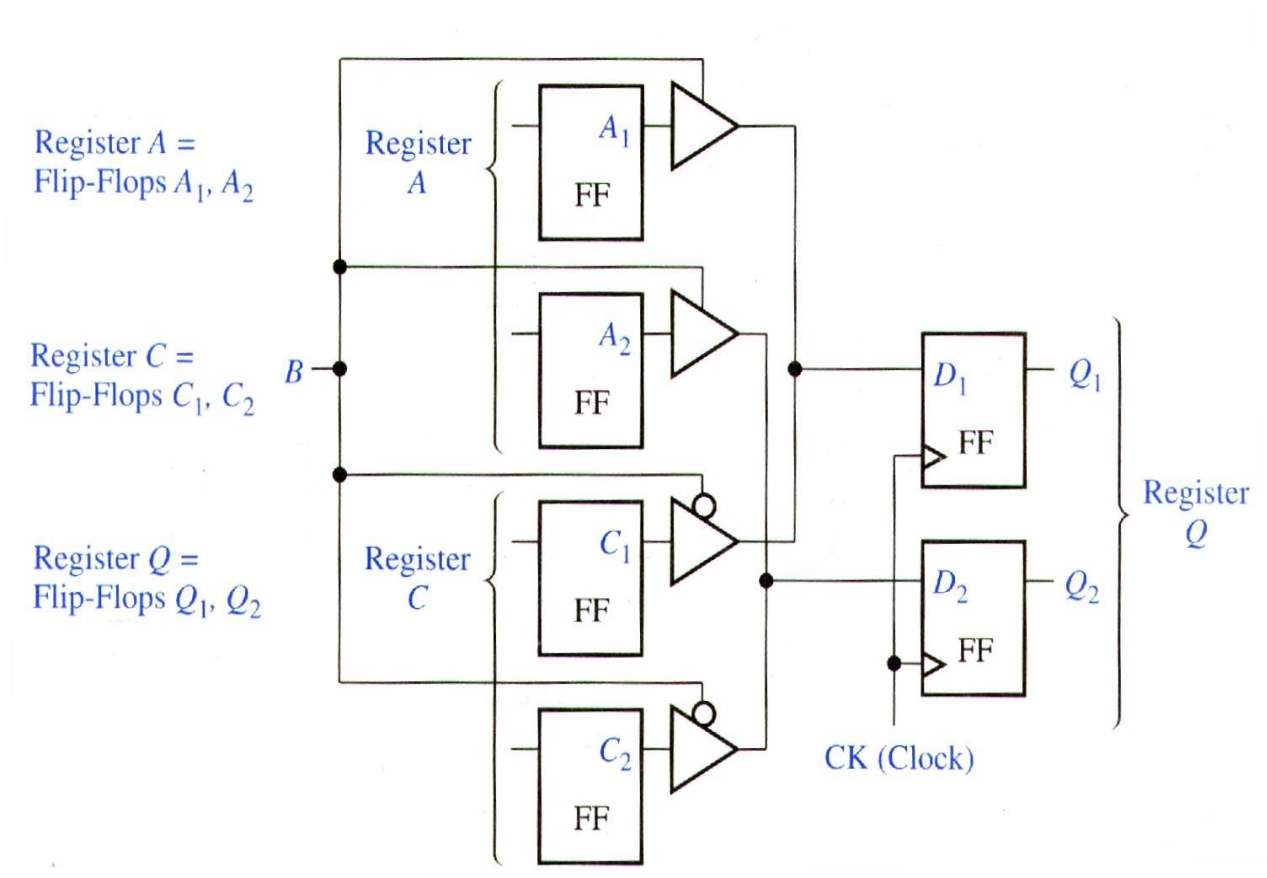


Tri-state Buffer Application (cont.)

- Source selection

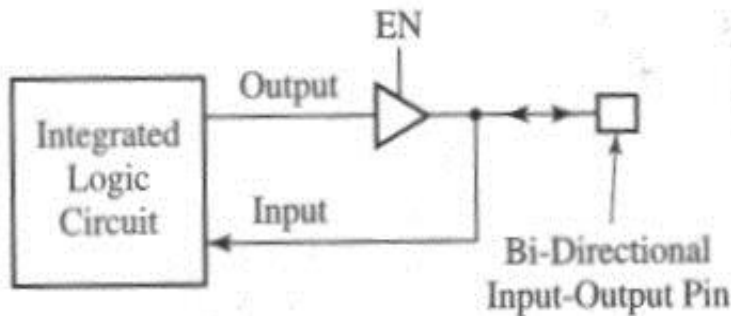 


Decoder

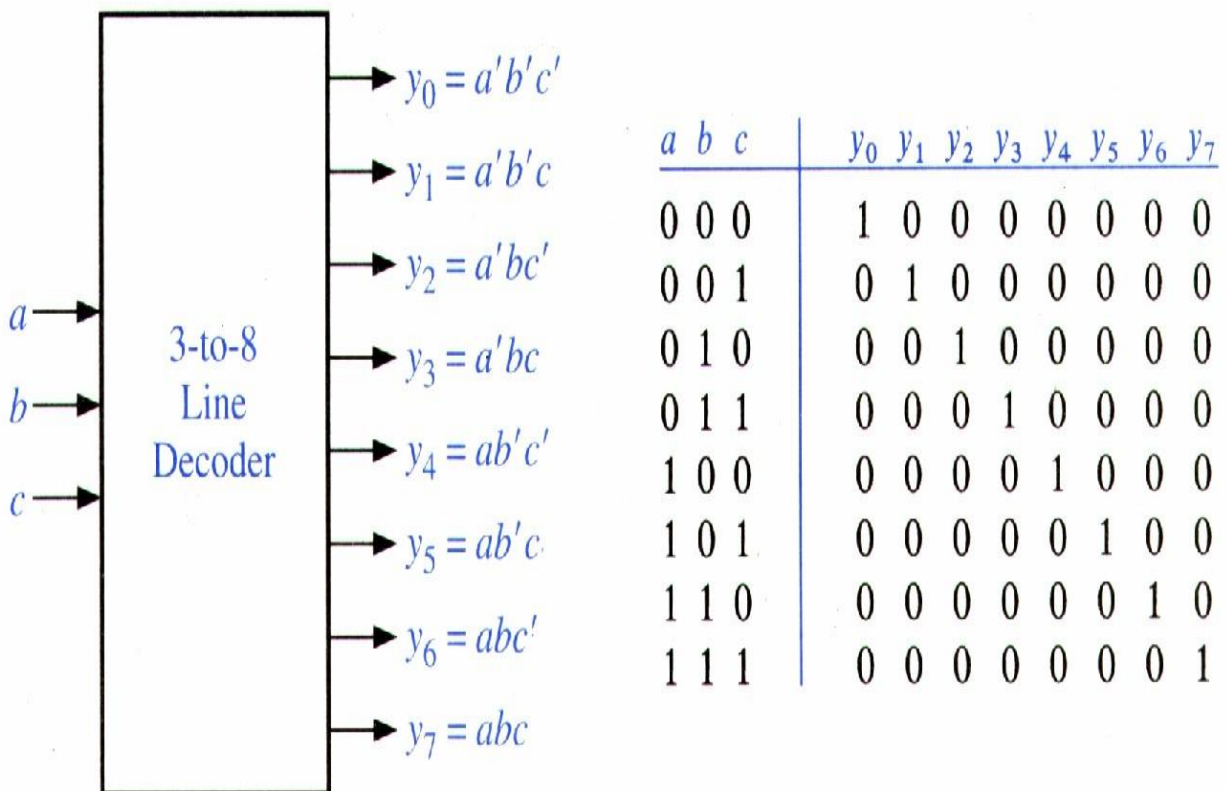- 3-to-8 line decoder
 - An n -to- 2^n decoder generates all 2^n minterms of the n input variables.




More Decoder

- 2-to-4 decoder: minterm generator

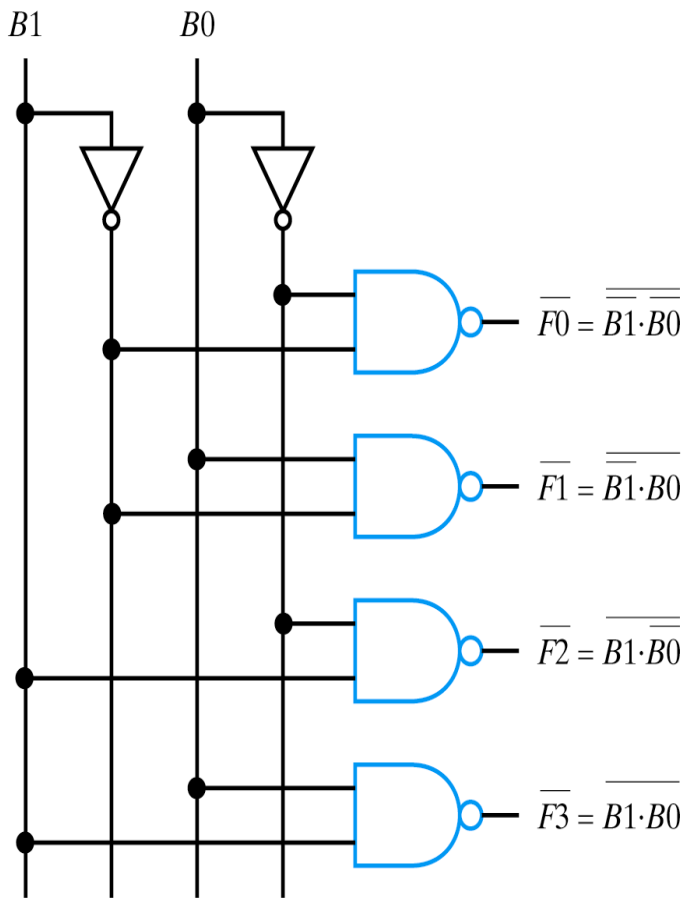

(a)

 


(b)


Figure 3.5.3 Decoder: (a) gate-level circuit diagram, (b) logic symbol.

Decoder (cont.)

- 4-to-10 line decoder

 

(a) Logic diagram

 


(b) Block diagram

BCD Input				Decimal Output									
A	B	C	D	0	1	2	3	4	5	6	7	8	9
0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	0	0	1	1	0	1	1	1	1	1	1	1	1
0	0	1	0	1	1	0	1	1	1	1	1	1	1
0	0	1	1	1	1	0	1	1	1	1	1	1	1
0	1	0	0	1	1	1	1	0	1	1	1	1	1
0	1	0	1	1	1	1	1	0	1	1	1	1	1
0	1	1	0	1	1	1	1	1	0	1	1	1	1
0	1	1	1	1	1	1	1	1	1	0	1	1	1
1	0	0	0	1	1	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	0
1	0	1	0	1	1	1	1	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1	1	1	1	1	1
1	1	0	0	1	1	1	1	1	1	1	1	1	1
1	1	0	1	1	1	1	1	1	1	1	1	1	1
1	1	1	0	1	1	1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1	1	1	1	1	1	1

 (c) Truth table

ROM

- Read-only memory: stored data can not be changed under normal operating conditions.



(a) block diagram



A	B	C	F_0	F_1	F_2	F_3
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

typical data stored in ROM (2^3 words of 4 bits each)

(b) truth table for ROM


ROM (cont.)

- ROM size = $2^n \times m$ bits.

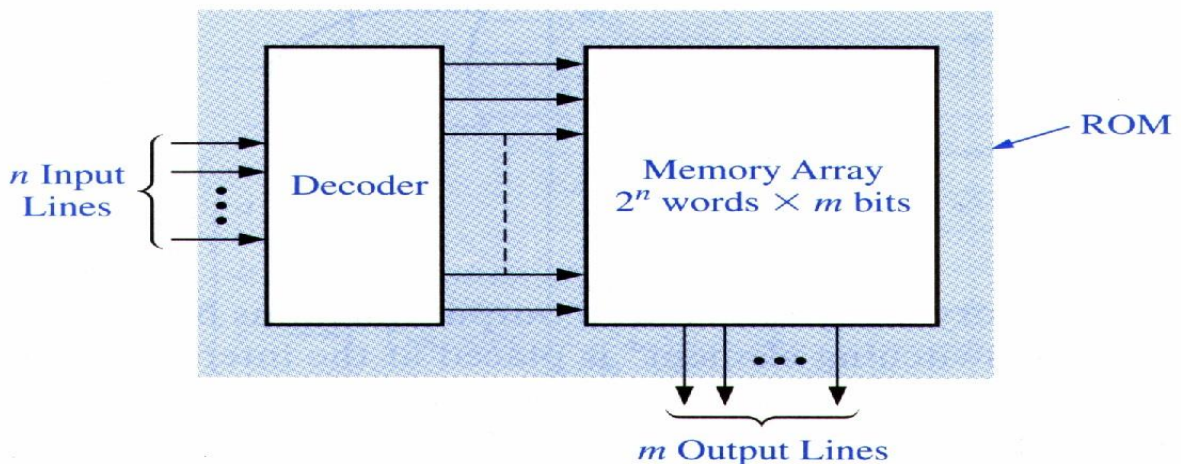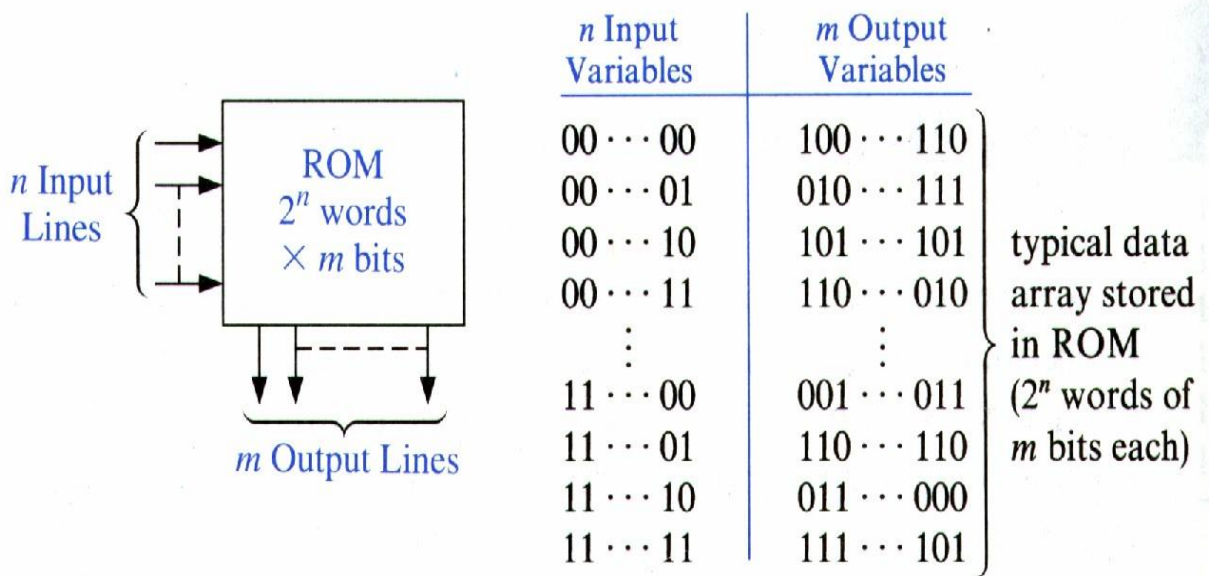


ROM Basic Structure

 - 8-word x 4 bit ROM
 - $F_0 = m_0 + m_1 + m_4 + m_6$



Multiple-Output Network Using ROM

- BCD to Excess-3 code

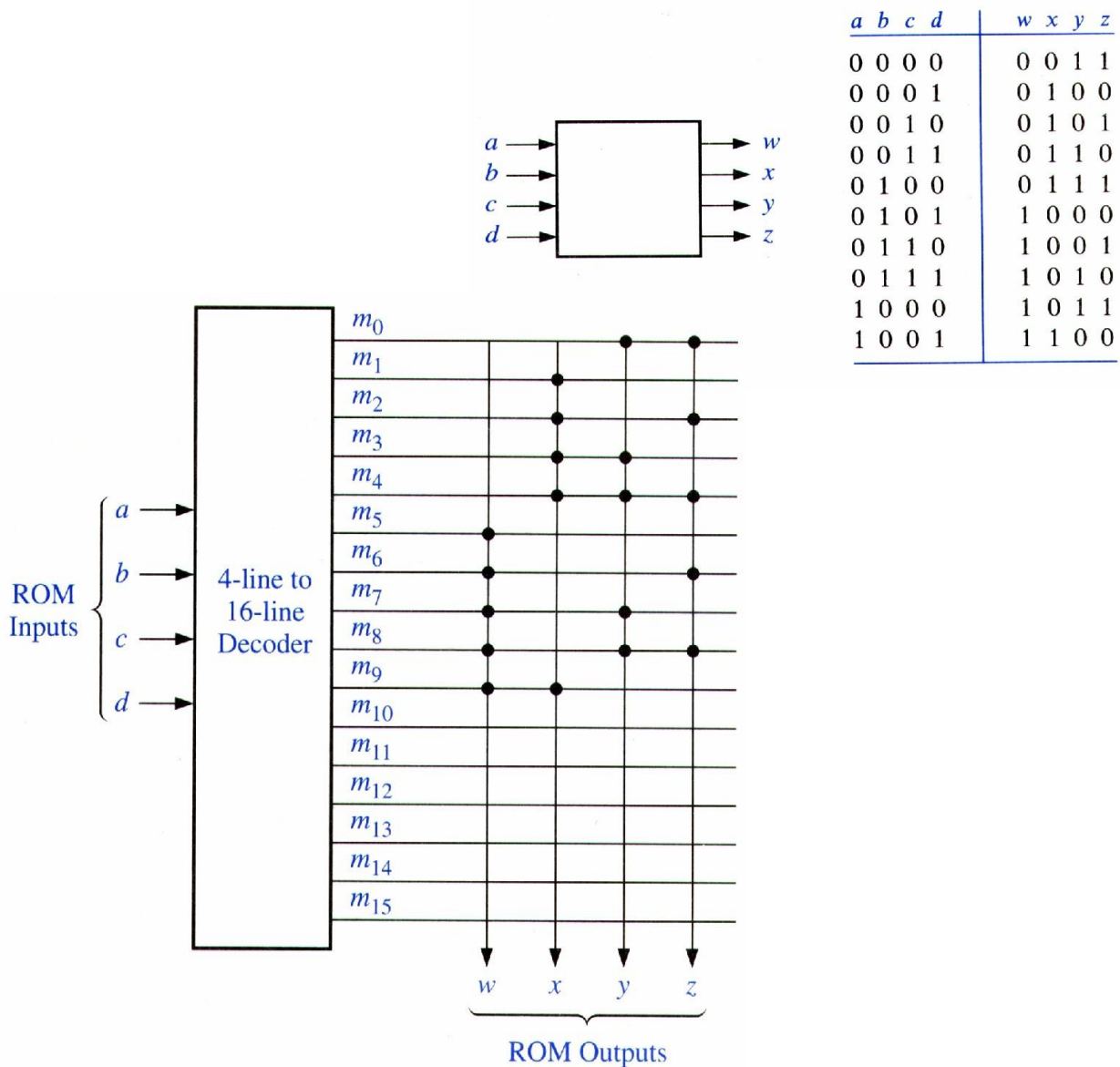


Types of ROM

- Mask-programmable ROM
 - Contents are stored during fabrication.
- Field-programmable ROM
 - PROM: programmable ROM
 - Fusible link (PROM programmer)
 - EPROM: erasable PROM
 - Use ultraviolet light for erasure.
 - EEPROM: electrically erasable PROM.
 - Flash memory

Programmable Logic Devices

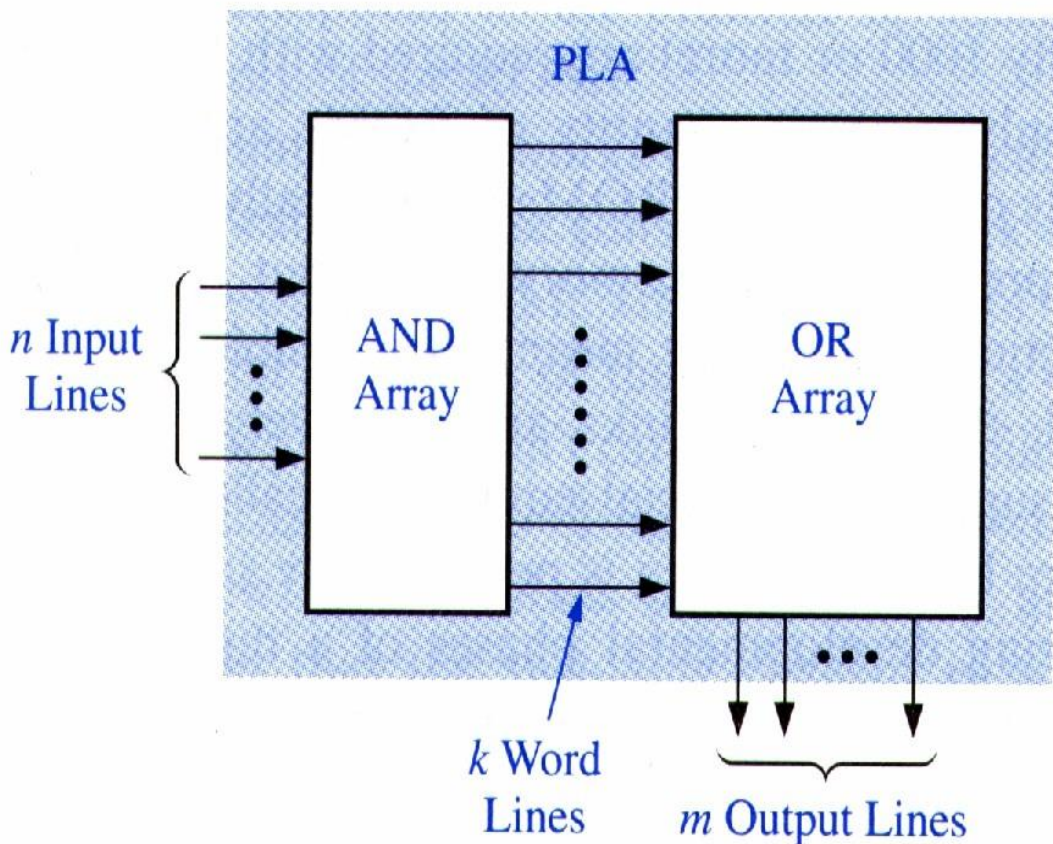- PLA (programmable logic array)
 - Realize m functions of n variables.



Implementation procedure for PLA

- Prepare the truth table based on your system
- Write the Boolean expression in SOP (sum of product) form.
- Obtain the minimum SOP form to reduce the number of product terms to a minimum.
- Decide the input connection of the AND matrix for generating the required product term.
- Then decide the input connections of OR matrix to generate the sum terms.
- Decide the connections of invert matrix.
- Program the PLA.

Programmable Symbology


 
 
 
 
 
 
 


Figure 3.6.2 Programmable symbology summary for the different types of PLDs.

PLA

 - PLA 3 inputs, 5 product terms, 4 outputs.



Product Term	Inputs			Outputs			
	A	B	C	F ₀	F ₁	F ₂	F ₃
A'B'	0	0	—	1	0	1	0
AC'	1	—	0	1	1	0	0
B	—	1	—	0	1	0	1
BC'	—	1	0	0	0	1	0
AC	1	—	1	0	0	0	1

$$F_0 = A'B' + AC'$$

$$F_1 = AC' + B$$

$$F_2 = A'B' + BC'$$

$$F_3 = B + AC$$

PLA

- PLA circuit


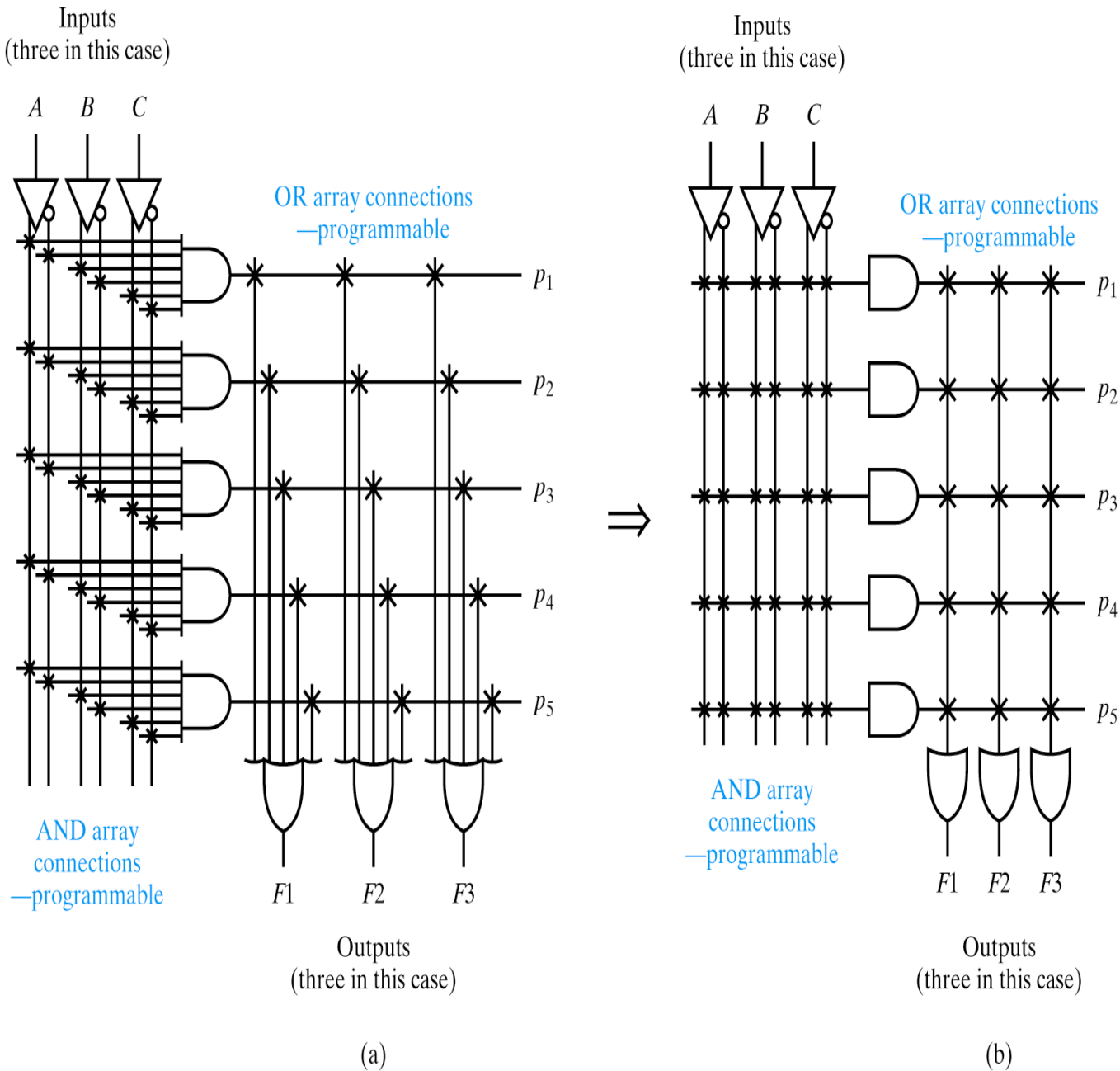


Figure 3.6.4 PLA circuit: (a) circuit representation using gates, (b) simplified circuit representation using gates.

PLA (cont.)

 - PLA 3 inputs, 5 product terms, 4 outputs. AND-OR array.




PLA Application

- $f_1 = a'bd + abd + ab'c' + b'c$
- $f_2 = c + a'bd$
- $f_3 = bc + ab'c' + abd$
 - If $abcd = 0111$, 1st, 5th, 6th rows are selected. $f_1 = 1 + 0 + 0$, $f_2 = 1 + 1 + 0$, etc.

a	b	c	d	f_1	f_2	f_3
0	1	–	1	1	1	0
1	1	–	1	1	0	1
1	0	0	–	1	0	1
–	0	1	–	1	0	0
–	–	1	–	0	1	0
–	1	1	–	0	0	1


(a) PLA table

 

 (b) PLA structure


Programmable Array Logic (PAL)

- AND array is programmable. OR array is fixed.
- Use input buffer to drive many ANDs.



Programmable Array Logic (PAL)

- Full Adder using a PAL

 

Why prefers PLA rather than ROM

- A combinational circuit may occasionally have **don't-care** conditions. When implemented with a ROM, **a don't care condition becomes an address input that will never occur.**
- The words at the don't care address need not be programmed and may be left in their original state(all 0's or all 1's).
- This has the result that all the bit patterns available in ROM are used, but for the don't care addresses you really can do without them.


What Programmable Means

- "programmable" does not indicate that all PLAs are **field-programmable**.
- Many are mask-programmed during manufacture in the same manner as a **mask ROM**.
 - This is particularly true of PLAs that are embedded in more complex and numerous integrated circuits such as microprocessors.
- PLAs that can be programmed after manufacture are called **FPGA** (Field-programmable gate array)

Complex Programming Logic Devices


- Xilinx XCR3064XL CPLD
 - Function block (16 macrocells)= PLA
 - Macrocell = a flip flop + multiplexers
 - IA routes signals

Input of function block

 


Function Block and MC

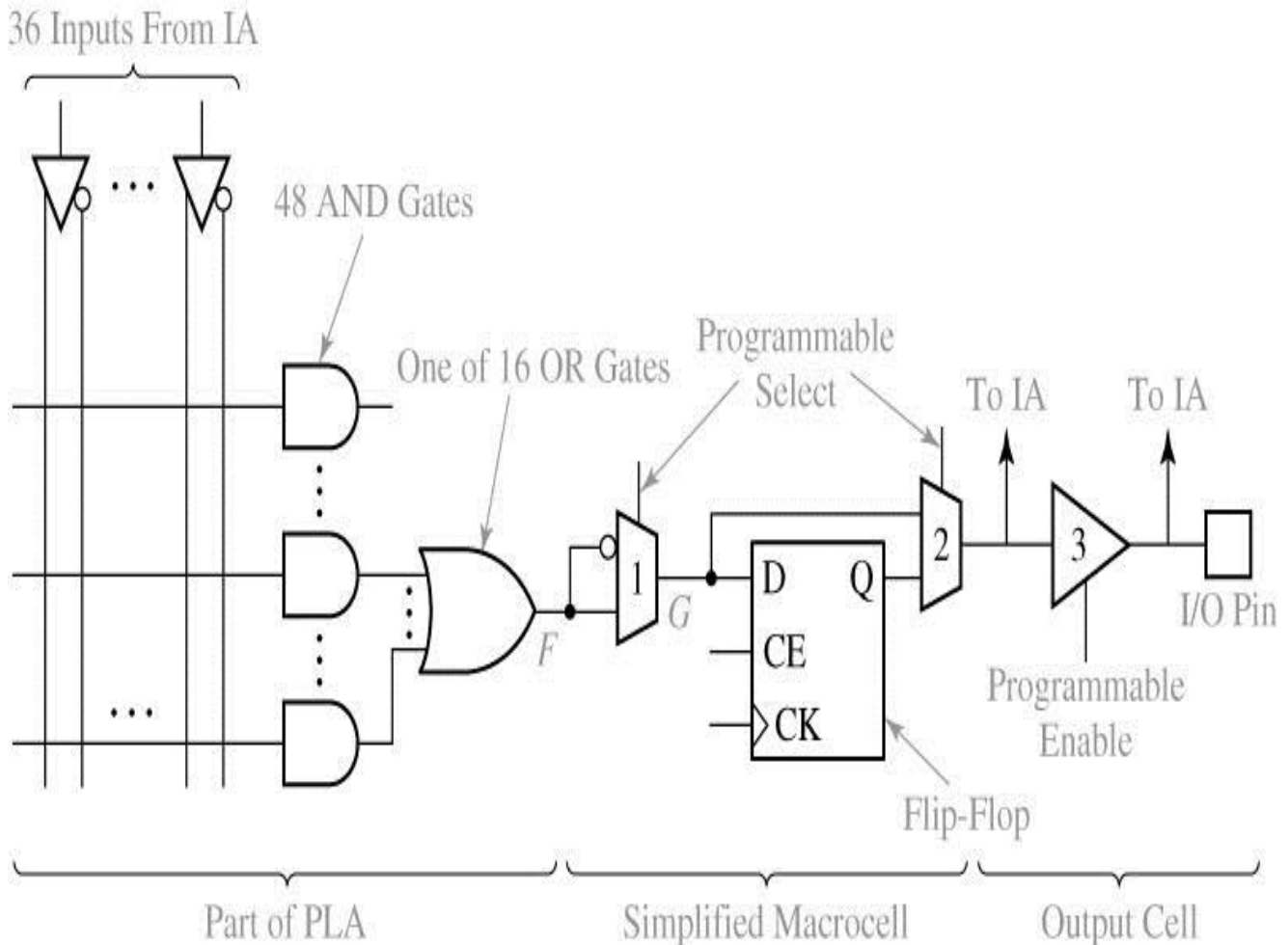- Signal from PLA -> macrocell -> I/O pin
- Use CAD tool to fit the design into the PLD.




Field Programmable Gate Arrays (FPGA)

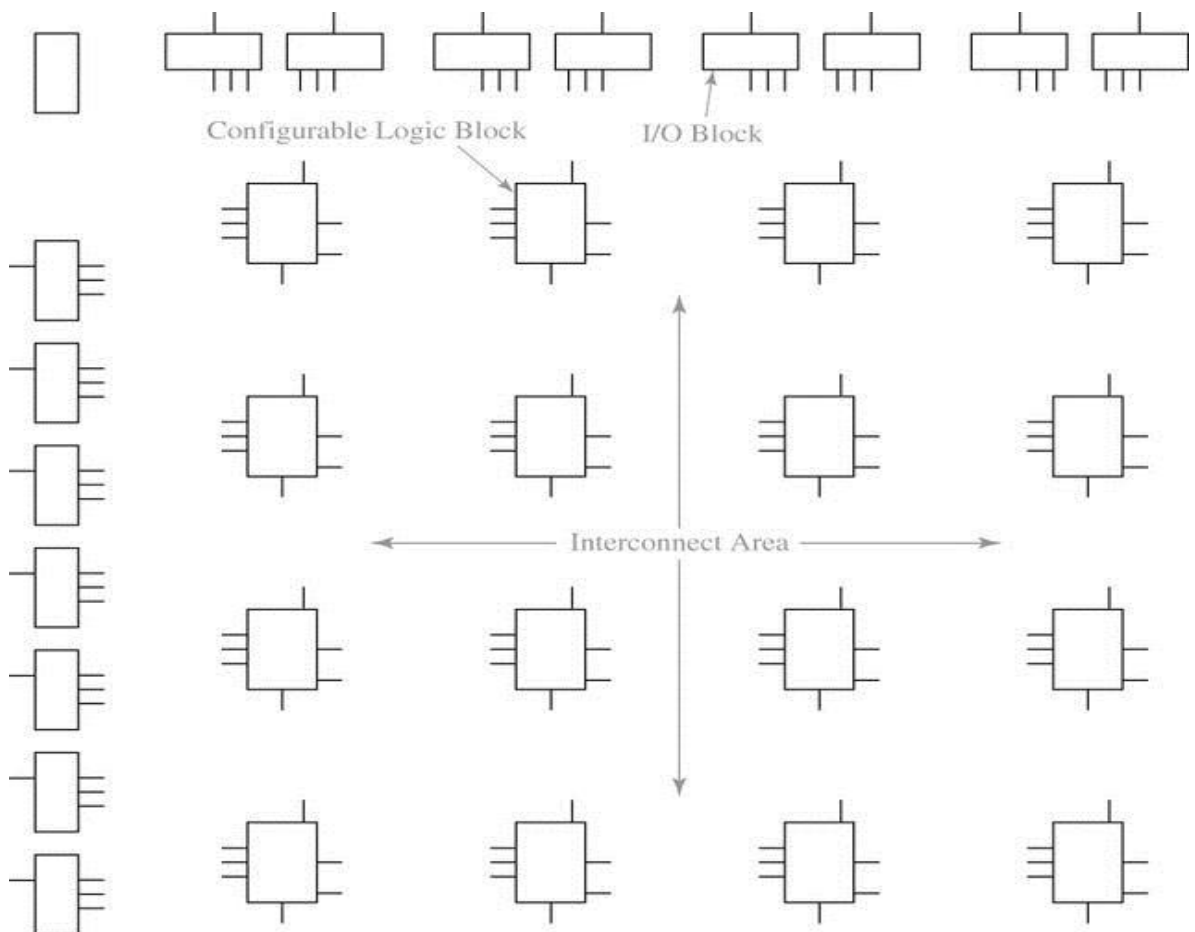- Logic cell: configurable logic blocks (CLBs)
- Input/Output blocks (I/O blocks)




Configurable Logic Block

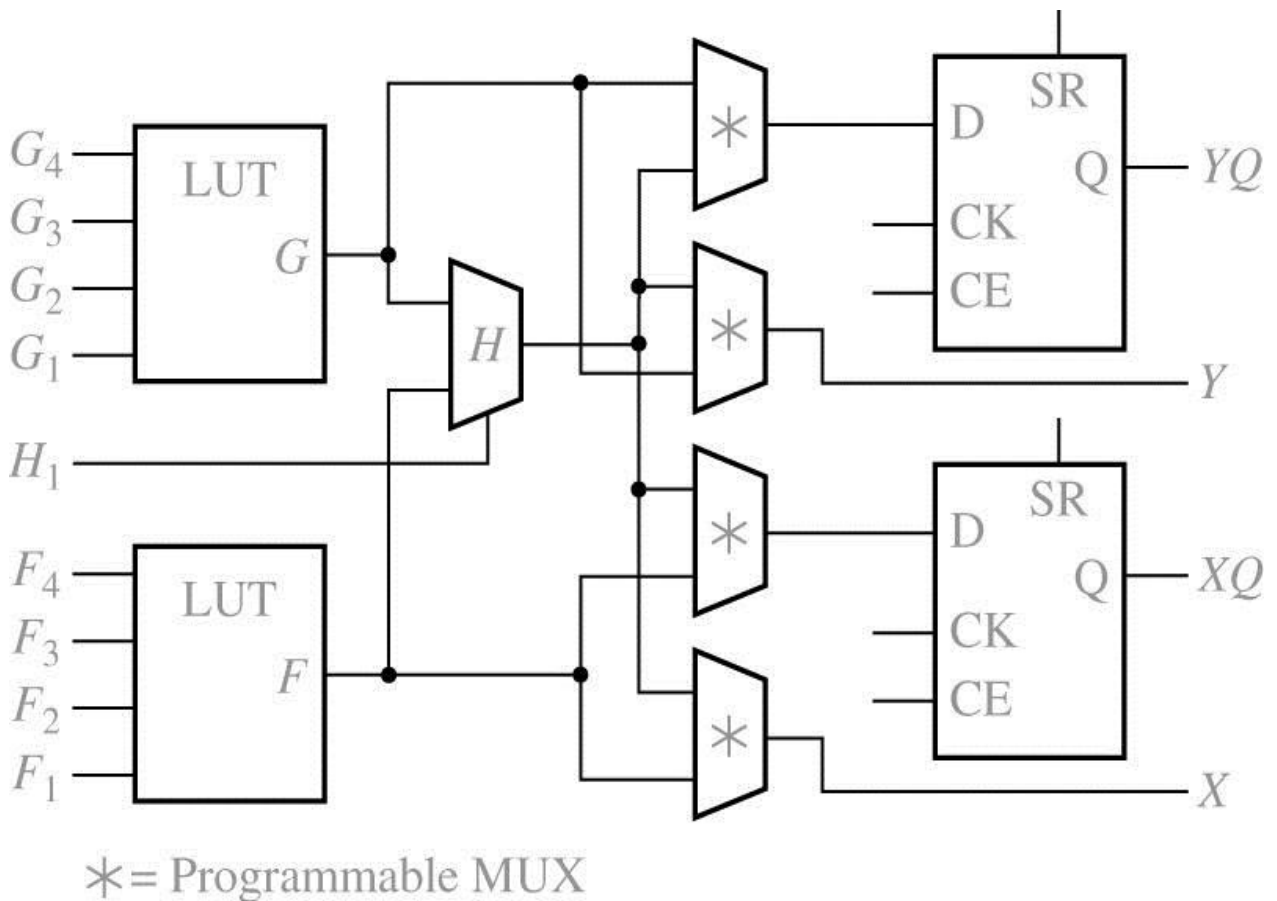- Inside a CLB: function generators (LUT), FFs, and MUXs
- LUT: lookup table (truth table) is a reprogrammable ROM (16 1-bit words)



A Lookup Table (LUT)

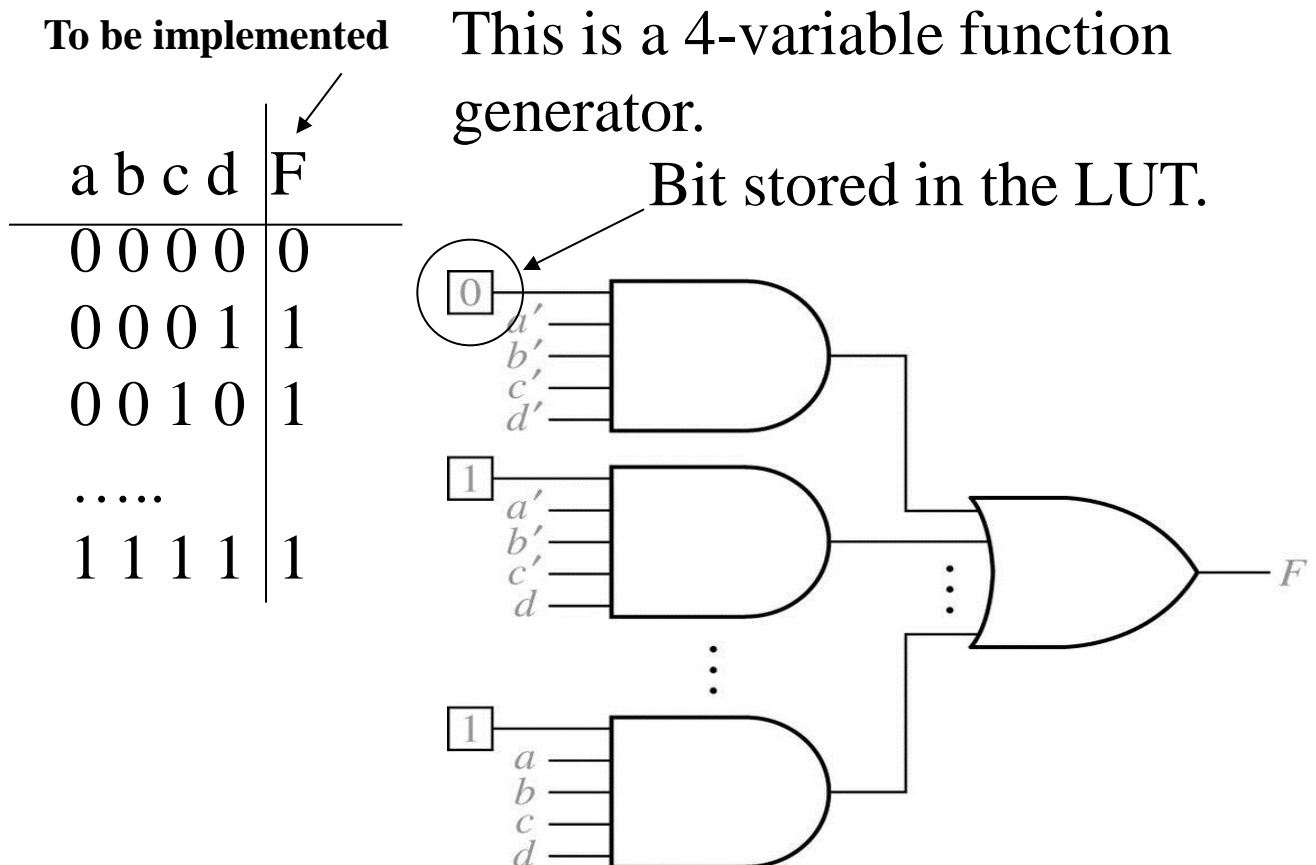- If we want $F = abc$ (one minterm)
 - 1110 (and $F=1$) + 1111 (and $F=1$)
- Or if we want $F = a'b'c'd' + a'b'cd' + \dots abcd$. (15 minterms)
- Require a single function generator. Program the LUT table to get what we want.




Shannon's Expansion Theorem

- What if # of variables > 4 variables

$$\begin{aligned}
 f(x_1, x_2, \dots, x_n) &= x_i' f(x_1, x_2, \dots, x_{i-1}, 0, x_{i+1}, \dots, x_n) + \\
 &\quad x_i f(x_1, x_2, \dots, x_{i-1}, 1, x_{i+1}, \dots, x_n) \\
 &= x_i' f_0 + x_i f_1
 \end{aligned}$$


$$f(a, b, c, d, e) = a' f(0, b, c, d, e) + a f(1, b, c, d, e)$$

 Let $a = 0$, what lefts are terms with b, c, d, e



$$2\text{-}1 \text{ MUX } F = a'I_1 + a I_2$$

(a) 5-variable function

 

(b) 6-variable function