

Lecture 10 Flip-Flops/Latches

- Sequential switching network
 - Output depends on present input and past sequence of inputs.
 - Need to remember past history.
 - Flip-flop (latch) is a memory that has a pair of complementary outputs.

Gate Delay

- Propagation delay
- Timing diagram


 



Figure 11-1
Propagation Delay in an Inverter

Network with Feedback

 - Inverter with feedback.
 - Propagation delay ($d = \frac{1}{2}$ period of CK)
 - Oscillate between 1 and 0.




(a) Inverter with feedback

 


(b) Oscillation at inverter output

- Stable state

 


(a)

 


(b)

S-R Latch

 
- Set-reset latch
 - Use NOR gate to construct a stable state network




(a)

 


(b)

 


(a)

 

(b)

 


(a)

 

(b)


S-R Latch (cont.)

 - When $S=R=1$, the S-R latch will not operate properly. (Is it a stable state, if $S=R=1$?)
 - Q and P are not complementary.
 - If $S=R=1$ changed to $S=R=0$, then the network will oscillate assuming both gates have the same delay. (Critical race occurs)



S-R Latch Timing and State

- S duration > delay time

 


- S-R latch behavior
 - Present state
 - The state of Q output at the time the input signals are applied.
 - Next state
 - The state of Q output after the latch has reacted to the input signals.

$S(t)$	$R(t)$	$Q(t)$	$Q(t + \epsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	—
1	1	1	—

} inputs not allowed

S R latch Analysis

 - Total state table
- If next state = present state, stable



		Current input ($S(t), R(t)$)				Next state $(y_0(t + t_{pd}), y_1(t + t_{pd}))$
		(0, 0)	(0, 1)	(1, 0)	(1, 1)	
Present state $(y_0(t), y_1(t))$	(0, 0)	(1, 1)	(1, 0)	(0, 1)	(0, 0)	
	(0, 1)	(0, 1)	(0, 0)	(0, 1)	(0, 0)	
	(1, 0)	(1, 0)	(1, 0)	(0, 0)	(0, 0)	
	(1, 1)	(0, 0)	(0, 0)	(0, 0)	(0, 0)	

K-map for $Q(t+\epsilon)$

- $Q^+ = S + R'Q$ (SR=0)
 - S and R can not be 1 at the same time.
 - Q: present state
 - Q^+ : next state
 - Next state equation or characteristic equation.



$R(t) \backslash S(t) \ Q(t)$		$S(t)$	
		00	01
$R(t) \ Q(t)$	00	0	1
	01	1	1
	11	0	X
	10	0	X

$$Q(t + \epsilon) = S(t) + R'(t) Q(t)$$

Debouncing Circuit

- Use S-R latch for debouncing.
- Pull-down resistors
- a switch to b.

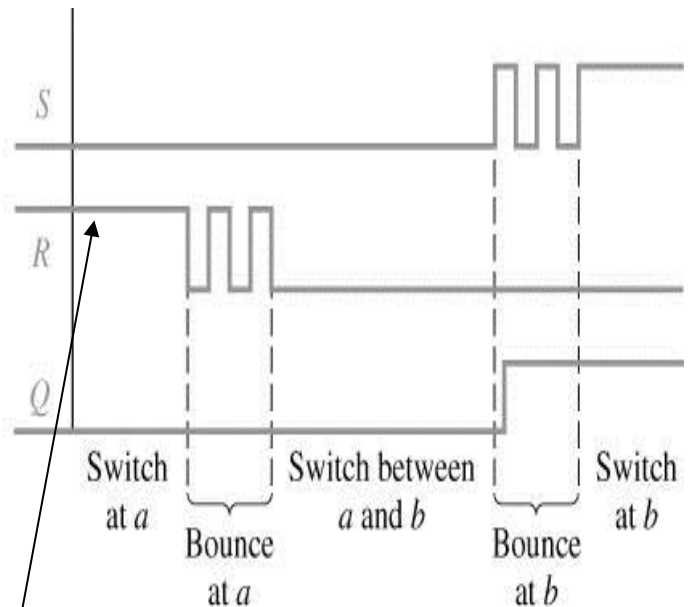 $S = 1$ set Q
 $S = 0, (R=0)$
 Q remained




$R = 1$ set $Q = 0$


S-R Latch using NAND gates

- S#-R# Latch, when S#= 0 sets $Q = 1$ and R#=0 resets $Q = 0$

S#	R#	Q	Q+
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	-
0	0	1	-

 



(a)

 

(b)

Gated D Latch

  
- Gate input G
 - Transparent latch (when $G = 1$, $Q = D$)




G	D	Q	Q_+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Edge-Triggered D Flip-Flop

 
- Output changes in response to clock edge



(a) Rising-edge trigger

 


(b) Falling-edge trigger

 


D Flip-Flop

 - Using two gated D latches
- Output changes occur at the rising edge
 - $CK = H$, output follows input.
 - $CK = L$, output remains




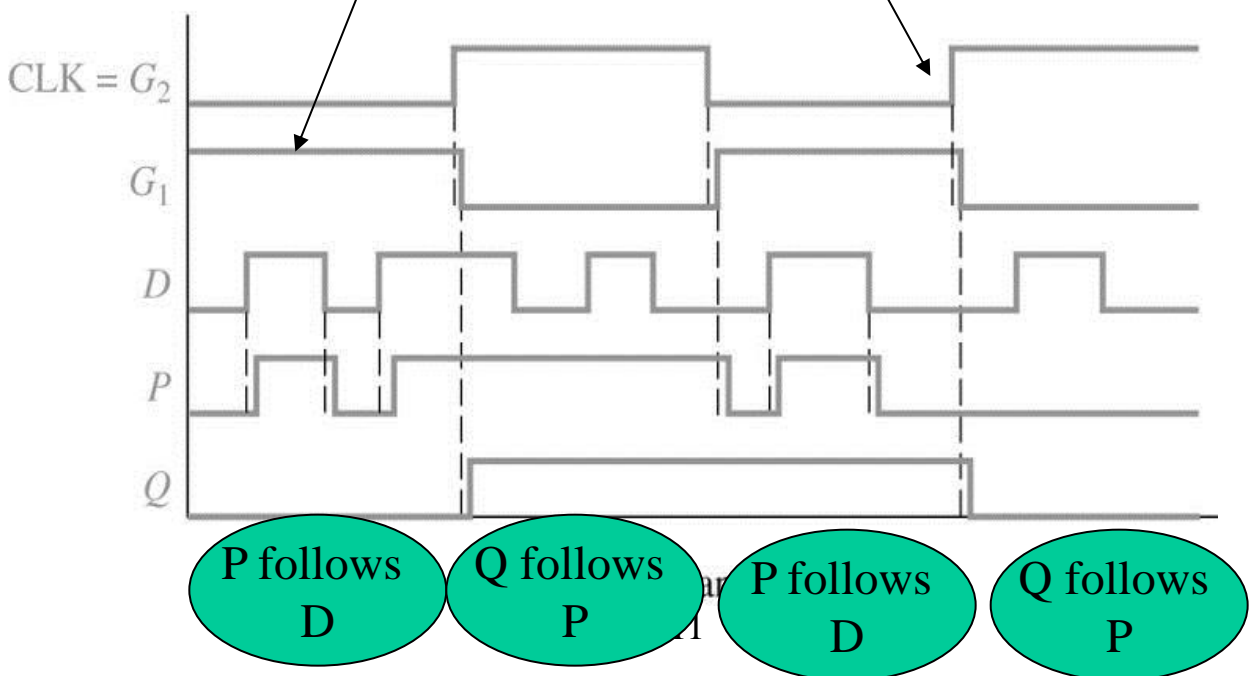(a) Construction from two gated D latches




D Flip-Flop

 - Output changes occur at the rising edge



 (a) Construction from two gated D latches




(b) Time analysis

$\Delta t = D1$ latch's propagation delay
This is the setup time for this FF.


Setup and Hold Time

 - Edge-Triggered D FF
 - Propagation delay of a FF is the time btw the active edge of the clock and resulting change in the output




Minimum Clock Period

 
- t_p
 - inverter = 2 ns,
 - FF = 5 ns
- Setup time 3 ns




(a) Simple flip-flop circuit

 

(b) Setup time not satisfied

 



(c) Setup time satisfied

 

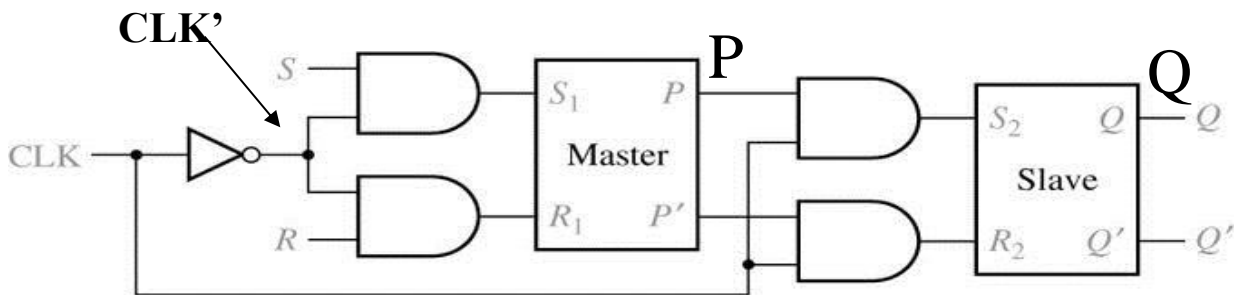 
(d) Minimum clock period

Master-Slave S-R Flip-Flop

- FF has a clock input.
- Change state after rising edge
- This figure shows a case that (S, R) are changed at CLK = H (A,B), then at CLK=L for C.
 - What if (S,R) becomes (1,0) nears t5? (OK)
- Actually (S,R) should be set to change (for set or reset) at the time near the end of M on and before S on. (to avoid miss-interpretation at t5)



(a) Implementation with two latches

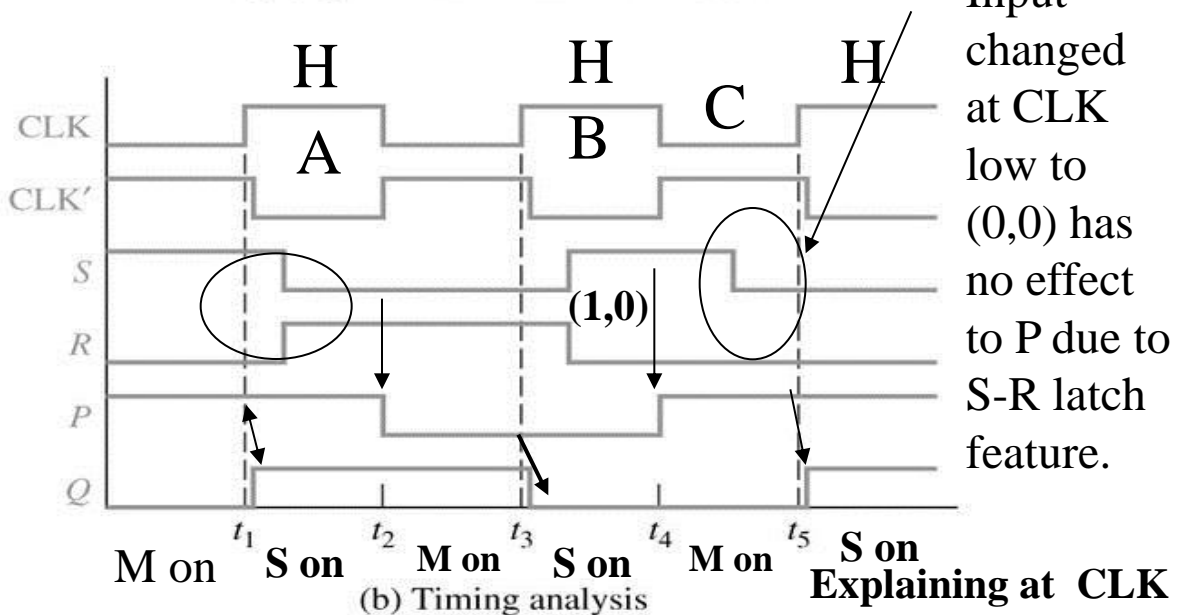


Toggle FF


- T flip-flop
 - Single input
 - When $T = 1$, at clock edge, T FF changes state. If $T = 0$, no state changes.

T	Q	Q ⁺
0	0	0
0	1	1
1	0	1
1	1	0

$Q^+ = T'Q + TQ' = T \text{ xor } Q$

 

(a)

 


T FF


- T flip-flop
 - Converted from D to T
 - $Q^+ = D = Q \text{ xor } T = TQ' + T'Q$

T	Q	Q^+
0	0	0
0	1	1
1	0	1
1	1	0

$Q^+ = T'Q + TQ' = T \text{ xor } Q$

 

(a) Conversion of J-K to T

 


(b) Conversion of D to T


J-K Flip Flop

- J-K FF = S-R FF + T FF.
 - Allow $J = K = 1$. This case works like a T FF.
 - Split T to J and K

J	K	Q	$Q^+ = JQ' + K'Q$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 


(a) J-K flip-flop

 

(c) J-K flip-flop timing


J-K Flip Flop

- J-K FF rising edge trigger

 


(a) J-K flip-flop

J	K	Q	$Q^+ = JQ' + K'Q$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

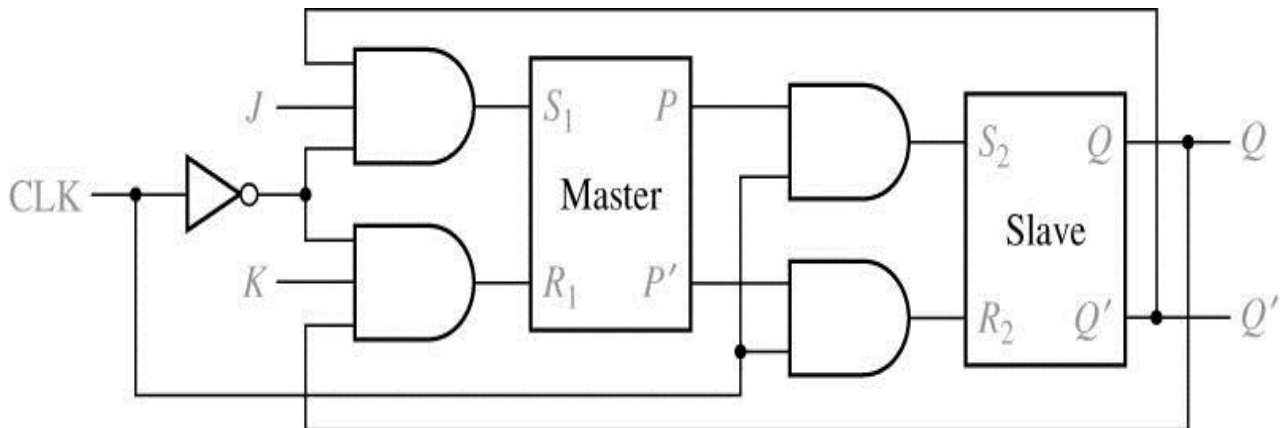


Master-Slave J-K Flip-Flop

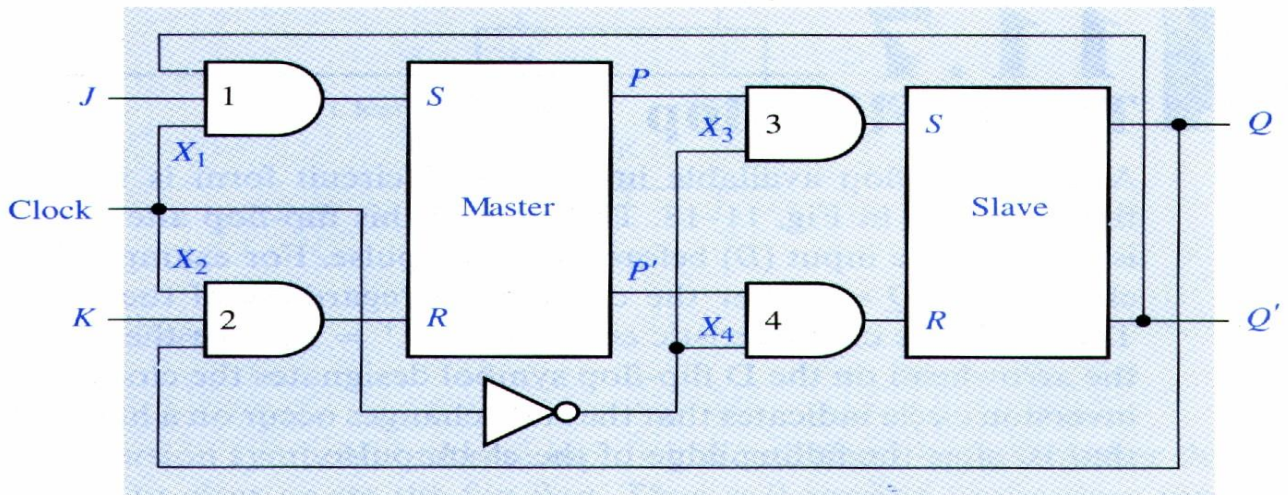- Clocked J-K FF (falling edge)
 - Realization using two S-R latches
 - Note where J and K change.




(a) Master-slave J-K flip-flop

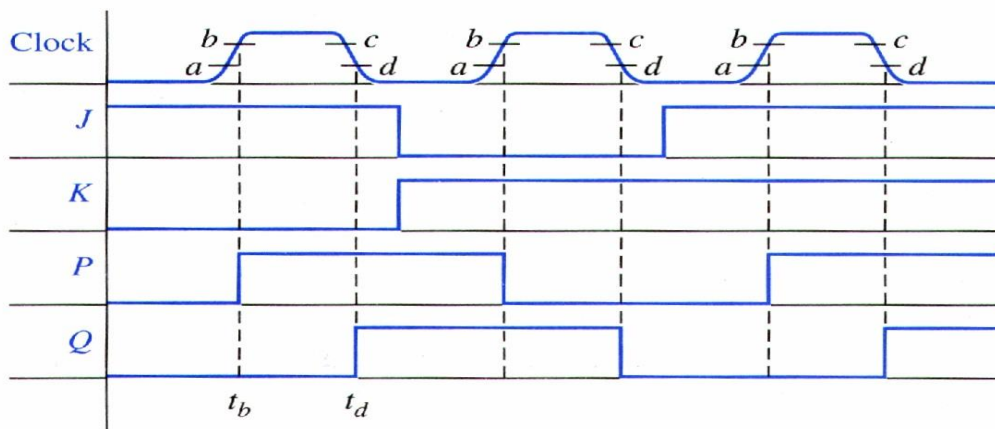

 
(b) Internal timing diagram for master-slave J-K flip-flop

T Flip-Flop Implementation

- Conversion
 - Using a J-K FF
 - Using a D FF




(a) Conversion of J-K to T

 

 (b) Conversion of D to T


D FF Register

- Register = many clocked D FFs
- $Q^+ = D$



Clear and Presets

 
- Active low inputs
- Asynchronous clear and preset



(a)


Ck	D	PreN	ClrN	Q^+
x	x	0	0	(not allowed)
x	x	0	1	1
x	x	1	0	0
↑	0	1	1	0
↑	1	1	1	1
0,1,↓	x	1	1	Q (no change)

(b)

 

Clock Enable

 - D-CE flip-flop
- Hold existing data even input changes.
- $Q^+ = Q.CE' + D.CE$
- In Fig. c, $Q^+ = D = Q.CE' + D_{in}.CE$
 - No gating in clock line, no synchronization problem.




Clocked Latches

Clocked latch:


The state changed whenever the inputs change and the clock is asserted.

 A D latch with NOR gates and clock (level trigger)




Unclocked Latch

 - SR latch
 - State may change if input changes.



S R latch Analysis

 
- Total state table
- Next internal state



		Current input ($S(t), R(t)$)				
		(0, 0)	(0, 1)	(1, 0)	(1, 1)	
Present state $(y_0(t), y_1(t))$	(0, 0)	(1, 1)	(1, 0)	(0, 1)	(0, 0)	Next state $(y_0(t + t_{pd}), y_1(t + t_{pd}))$
	(0, 1)	(0, 1)	(0, 0)	(0, 1)	(0, 0)	
	(1, 0)	(1, 0)	(1, 0)	(0, 0)	(0, 0)	
	(1, 1)	(0, 0)	(0, 0)	(0, 0)	(0, 0)	


D Flip Flop

 - Master latch with a slave latch
 - State changes only at clock edge.
 - Falling edge.




Timing Requirement

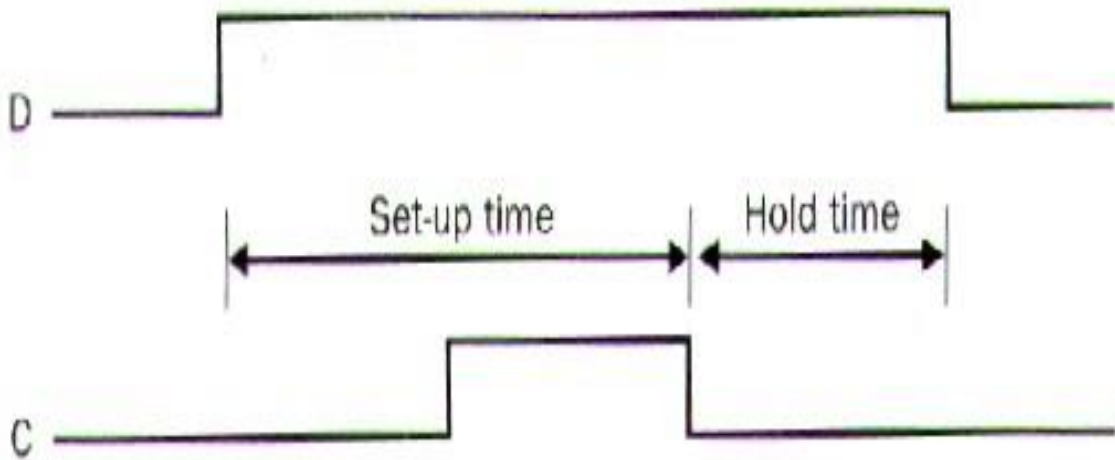- Falling edge trigger
 - Set up time
 - Hold time
 - **Hold time requirement is either 0 or very small.**



Clock Period Requirement

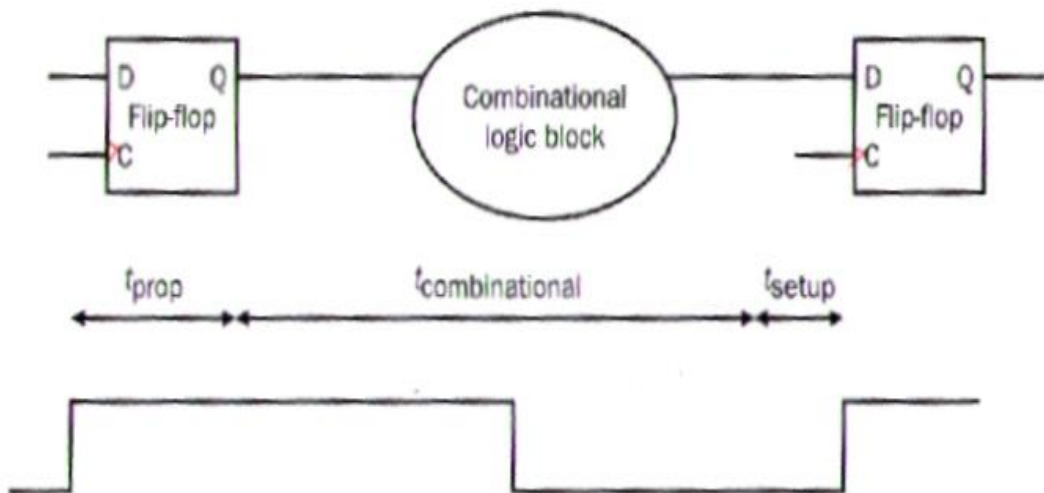- Clock period requirement
 - $t_{\text{propagation}} + t_{\text{combinational}} + t_{\text{setup}} + t_{\text{skew}}$
 - $t_{\text{propagation}}$ is the time for FF inputs to FF outputs.
 - t_{skew} is the time difference when two state elements see a clock edge.



Asynchronous inputs

- Why makes it a synchronous input?
 - Used to change state of a system
 - If not synchronized, the signals may violate the setup time or hold time of a receiving device.
- Metastable behavior
 - State in the middle of 1 and 0.