
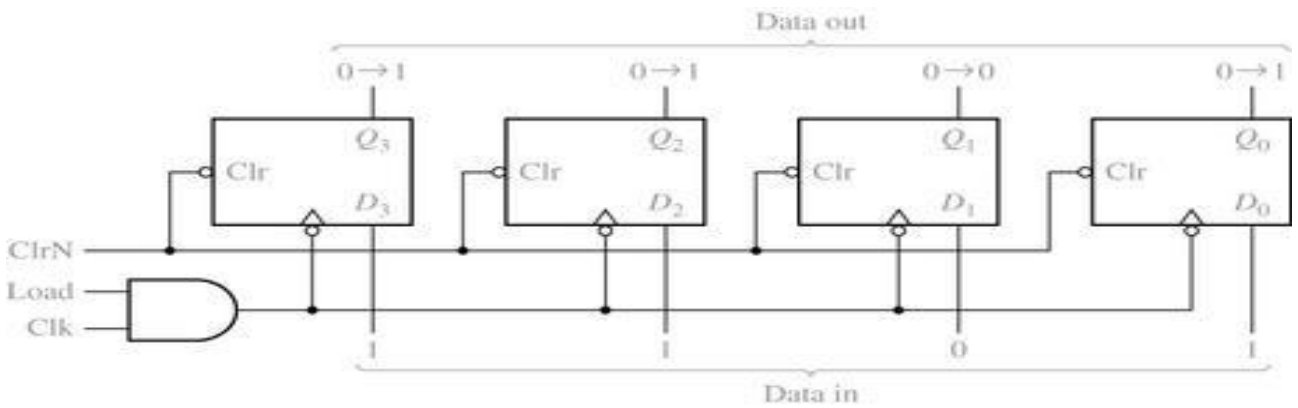


Lecture 11 Registers and Counters

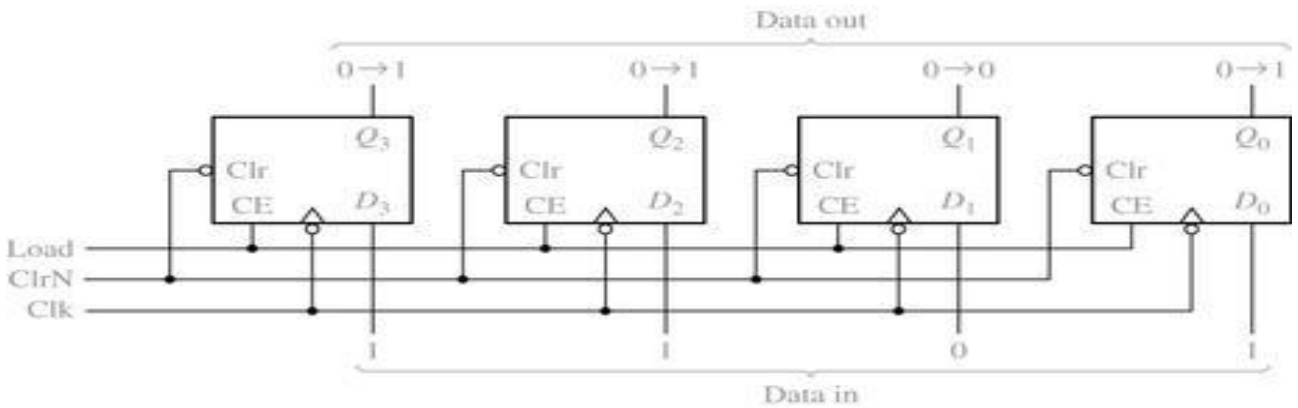
- Registers can be formed by a group of D flip-flops with a common clock.



(a) Using gated clock




(b) With clock enable

 

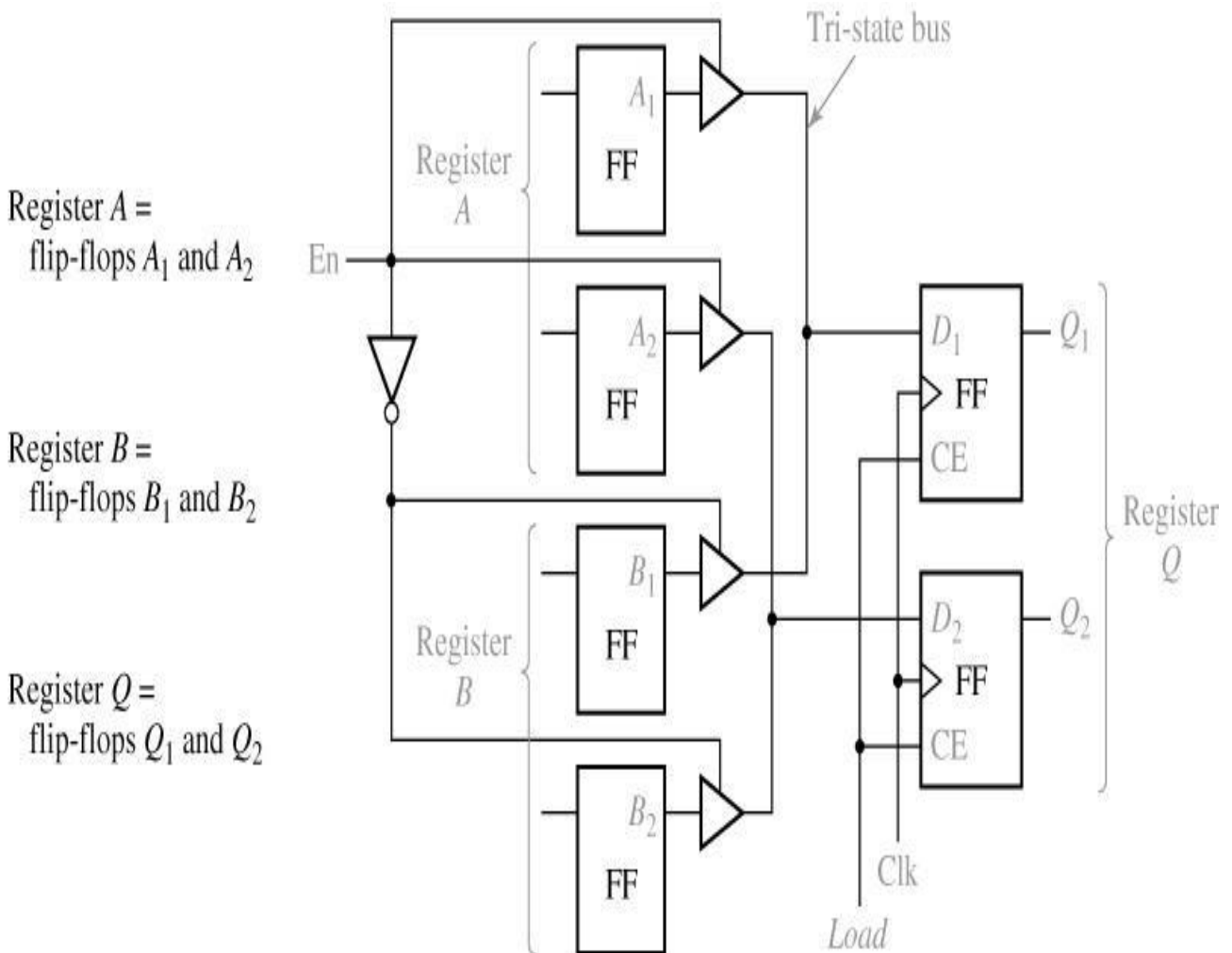(c) Symbol


Data Transfer btw Registers

- Bus is a group of wires.
- Load: write control




Register with Tri-State Output

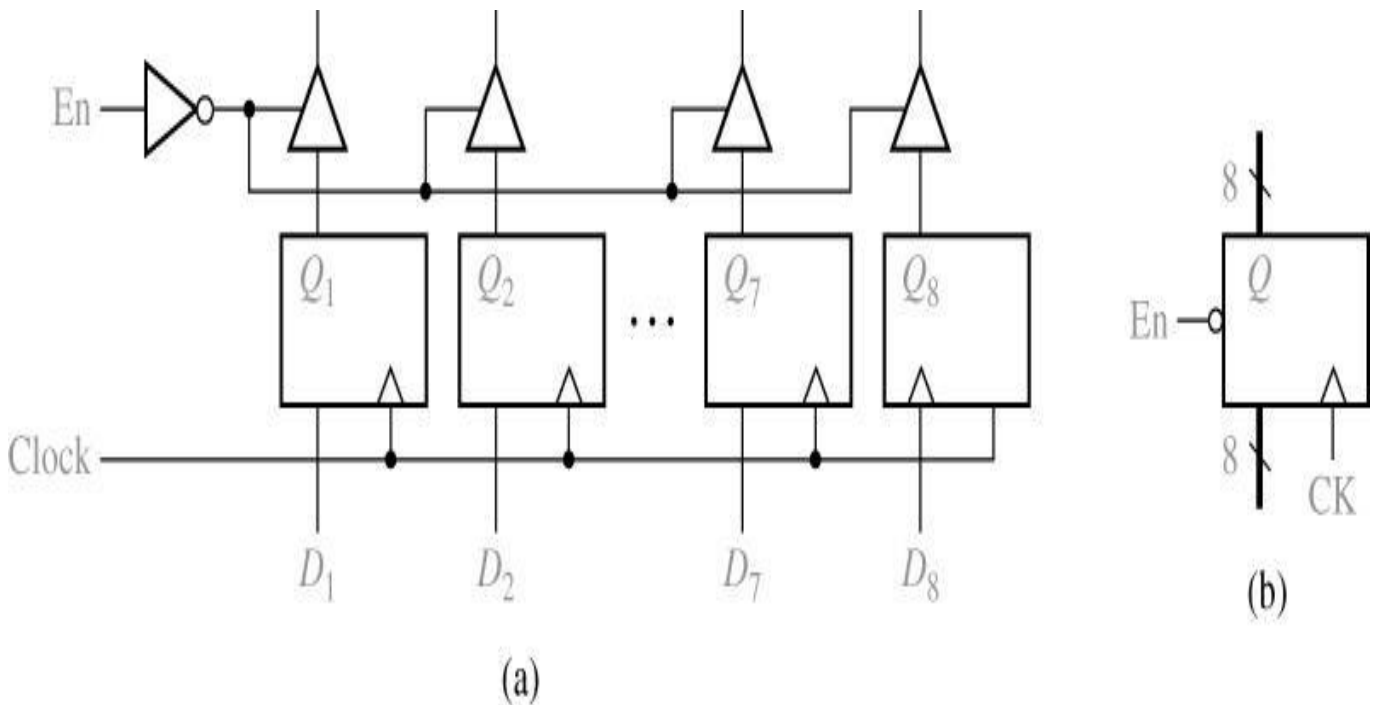- Physically connected, electrically disconnected.




Tri-State Bus

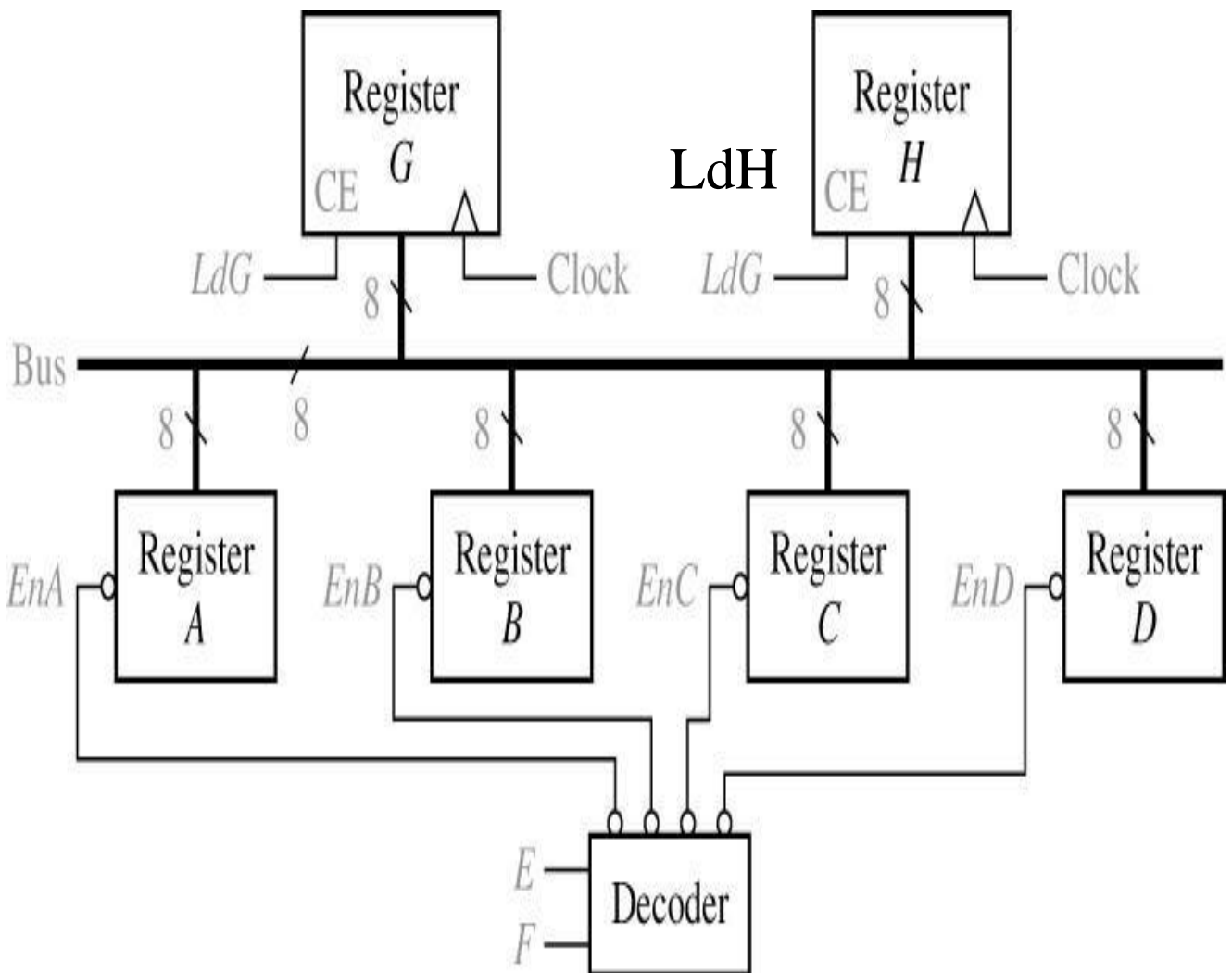- Physically connected, electrically disconnected.




Accumulator

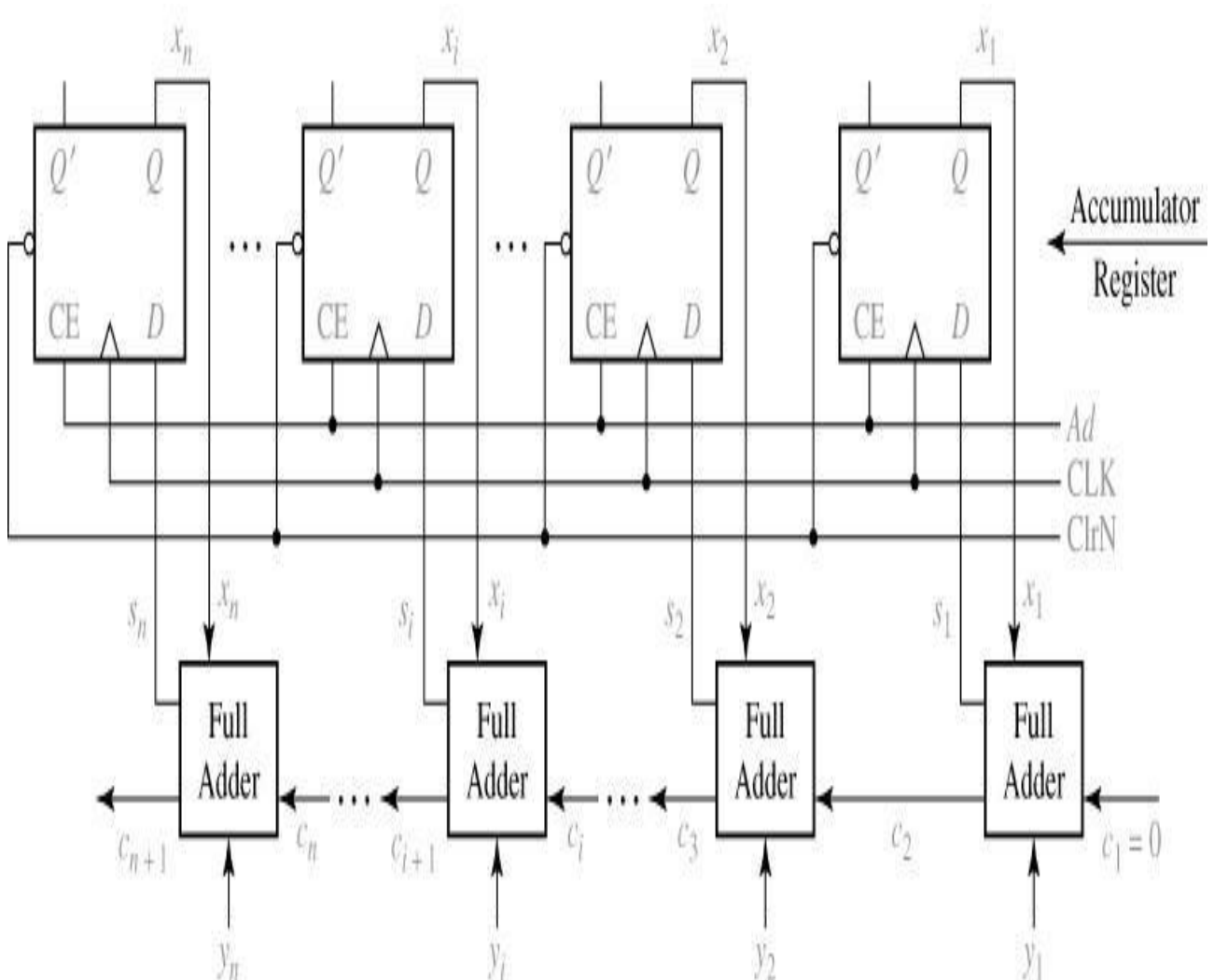- Accumulator is a register. One operand is in the accumulator.
- Ad signal is used to load the adder outputs into the Acc FF on the rising clock edge.




An Accumulator Cell

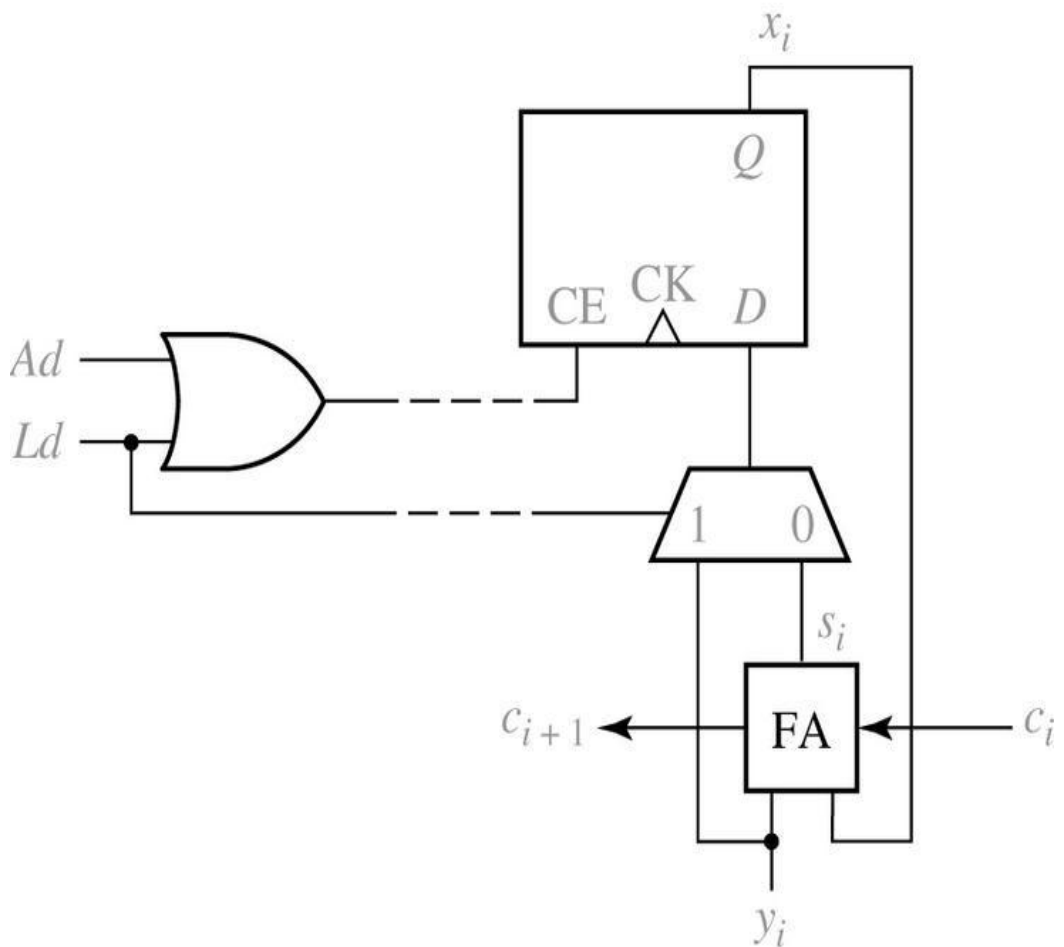- How to load the first operand?
- Ld is used to select y which is loaded into the accumulator flip-flop.




Shift Registers

 - Right shift
- When enabled, shift occurs on the rising edge.
 - The output loaded into each FF is the value before the rising clock edge because of the propagation delay.






(a) Flip-flop connections

 

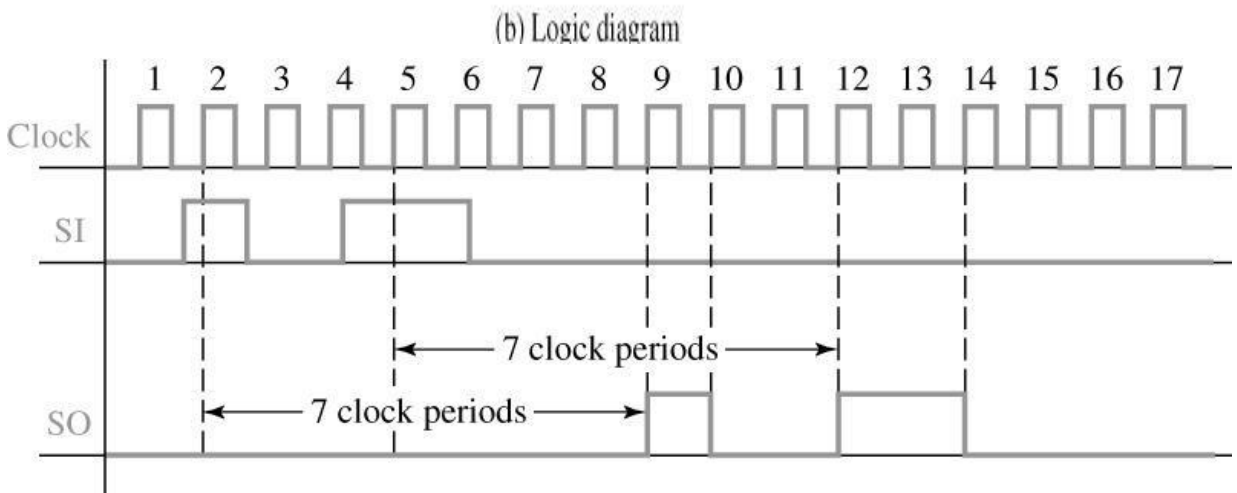  (b) Timing diagram


Shift Register Timing

- The output loaded into each FF is the value before the rising clock edge
- If initial value = 0101, and serial input = 1101, then 0101 -> 1010 -> 1101 ..




Parallel-in Parallel-out Right Shift Register

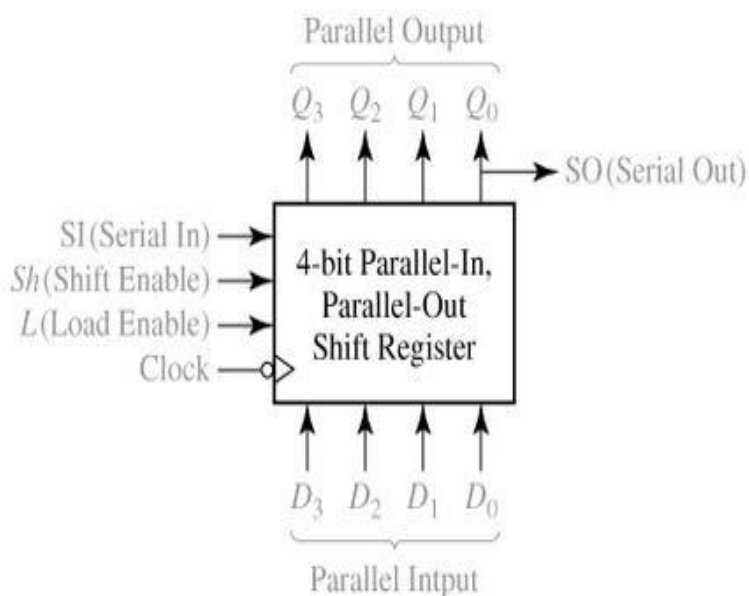- All 4 bits can be loaded or read out at the same time.




(a) Block diagram

 

 
(b) Implementation using flip-flops and MUXes

Shift Register with Feedback

- Initial state = 000
- After the rising clock edge, the state is 100
- If the register is in 010, the next state is 101. Not in the main loop.
- This is a counter.



(a) Flip-flop connections

 


(b) State graph

Synchronous Counter

- Synchronous counter
 - FFs are synchronized by a common input pulse.
- Example: Construct a binary counter using three T FF to count pulses.
 - 000, 001, 010, 011, 100, 101, 110, 111, 000

Synchronous Binary Counter

 - 000, 001, 010, 011, 100, 101, 110, 111, 000 T_C, T_B, T_A
 - A changes whenever a rising clock edge occurs.
 - B changes when $A = 1$.
 - C changes when $B = 1$ and $A = 1$ and a rising clock edge occurs.



Synchronous Binary Counter

- Using a state table to design the counter. Whenever A and A^+ differs, FF A must change state, thus $T_A = 1$
 - If B and B^+ differs, $T_B = 1$, etc.
 - If $CBA = 011$, $C^+B^+A^+ = 100$, then $T_C T_B T_A = 111$. ($T_C = f(A, B, C)$, etc)
 - That is, if T FF changes state ($Q^+ \neq Q$), T must be 1.

TABLE 12-2
State Table
for Binary
Counter

| Present State | | | Next State | | | Flip-Flop Inputs | | |
|---------------|-----|-----|------------|-------|-------|------------------|-------|-------|
| C | B | A | C^+ | B^+ | A^+ | T_C | T_B | T_A |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |

Synchronous Binary Counter (cont.)

- T_C, T_B, T_A (flip flop inputs) as function of A, B, C
 - Because we have A, B, C as they are, T_A, T_B, T_C are the results of (A, B, C) in order to get what we want in A^+, B^+, C^+). Therefore T_A, T_B, T_C are functions of A, B, C .
 - Consider T_A, T_B, T_C as multiple output
 - From K-map : $T_C = BA, T_B = A, T_A = 1$

| | | | |
|------|----|-------|---|
| | | C | |
| | | 0 | 1 |
| BA | 00 | 0 | 0 |
| | 01 | 0 | 0 |
| | 11 | 1 | 1 |
| | 10 | 0 | 0 |
| | | T_C | |

| | | | |
|------|----|-------|---|
| | | C | |
| | | 0 | 1 |
| BA | 00 | 0 | 0 |
| | 01 | 1 | 1 |
| | 11 | 1 | 1 |
| | 10 | 0 | 0 |
| | | T_B | |

000 to 111 counter


- Use D FFs
- $D_A = A^+ = A'$
- $D_B = B^+ = B \text{ xor } A$
- $D_C = C^+ = C \text{ xor } BA$
- B changes state when A=1
- C changes state when AB = 1

TABLE 12-2
State Table
for Binary
Counter

| Present State | | | Next State | | | Flip-Flop Inputs | | |
|---------------|---|---|----------------|----------------|----------------|------------------|----------------|----------------|
| C | B | A | C ⁺ | B ⁺ | A ⁺ | T _C | T _B | T _A |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |


Binary Counter with D FFs

 - $D_A = A^+ = A' = 1 \text{ xor } A$
- $D_B = B^+ = B \text{ xor } A$
- $D_C = C^+ = C \text{ xor } BA$
 - C changes state when $AB = 1$



Up-Down Counter

 
- State transition
- Use D FFs
- U and D can not both equal 1 at the same time.
- For $D=1$, B changes state when $A = 0$
- For $U=1$, B changes state when $A = 1$



| CBA | $C^+B^+A^+$ | |
|-----|-------------|-----|
| | U | D |
| 000 | 001 | 111 |
| 001 | 010 | 000 |
| 010 | 011 | 001 |
| 011 | 100 | 010 |
| 100 | 101 | 011 |
| 101 | 110 | 100 |
| 110 | 111 | 101 |
| 111 | 000 | 110 |

Up-Down Counter

 
- Construct a truth table
- $A^+ = \text{function}(C, B, A, U, D)$
 - Then simplify this function for A^+
- Or observe the table:
 - When $U = 1$ or $D = 1$, $A^+ = A'$. When $U = 0$, $D = 0$, A remains unchanged. Thus $A^+ = A'U + A'D + AU'D'$
 - Or $A^+ = A'(U + D) + A(U + D)'$
 - $U = 1$ or $D = 1$, $A^+ = A'$. $U = 0$ and $D = 0$, $A^+ = A$.



| CBA | $C^+B^+A^+$ | |
|-----|-------------|-----|
| | U | D |
| 000 | 001 | 111 |
| 001 | 010 | 000 |
| 010 | 011 | 001 |
| 011 | 100 | 010 |
| 100 | 101 | 011 |
| 101 | 110 | 100 |
| 110 | 111 | 101 |
| 111 | 000 | 110 |

Up-Down Counter

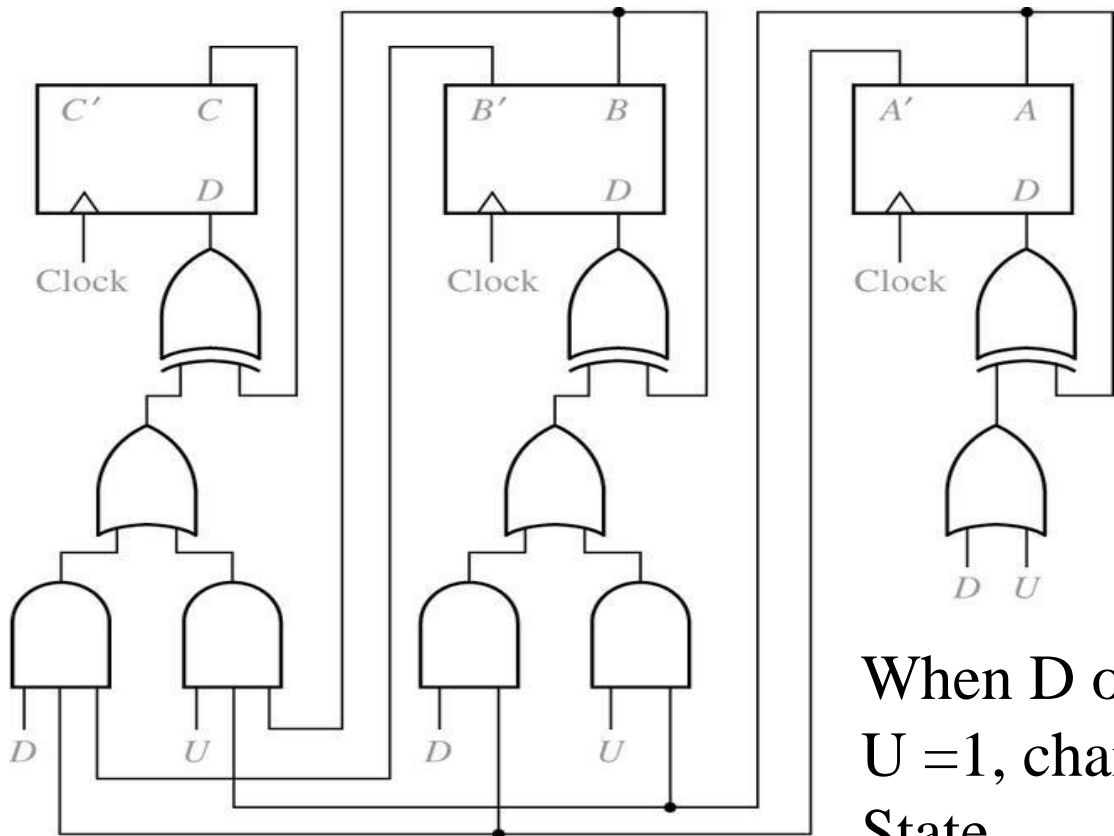
- $D_A = A^+ = A \text{ xor } (U + D)$
- $D_B = B^+ = B \text{ xor } (UA + DA')$
- $D_C = C^+ = C \text{ xor } (UBA + DB'A')$
- Homework: find B^+ and C^+ .



When D or U = 1, change State.

Loadable Counter

 - When Load ($Ld=1$), data is loaded into the counter on the rising clock edge.
- When $Ct = 1$, the counter is incremented on the rising clock edge.



(a)


| ClrN | Ld | Ct | C ⁺ | B ⁺ | A ⁺ | |
|------|----|----|-------------------|----------------|----------------|-------------|
| 0 | X | X | 0 | 0 | 0 | |
| 1 | 1 | X | D_C | D_B | D_A | (load) |
| 1 | 0 | 0 | C | B | A | (no change) |
| 1 | 0 | 1 | Present state + 1 | | | |

(b)

$Ld'Ct$ changes state.

Loadable Counter

 - When $Ld=1$, Dins are selected and clocked in since the output of each AND gate is 0.
- When $Ct = 1$, $Ld=0$, it becomes equivalent to the UP counter.
- $D_A = A^+ = (Ld'.A + Ld.D_{Ain}) \text{ xor } Ld'.Ct$
- $D_B = B^+ = (Ld'.B + Ld.D_{Bin}) \text{ xor } Ld'.CtA$
- $D_C = C^+ = (Ld'.C + Ld.D_{Cin}) \text{ xor } Ld'.CtAB$



Counters with Non-Binary Sequence

- State graph
 - The next state of 000 is 100.
 - 001 has no next state from the graph.

FIGURE 12-21
State Graph for Counter


 


TABLE 12-3
State Table for
Figure 12.21


| C | B | A | C ⁺ | B ⁺ | A ⁺ |
|---|---|---|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | – | – | – |
| 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | – | – | – |
| 1 | 1 | 0 | – | – | – |
| 1 | 1 | 1 | 0 | 1 | 0 |

Counters with Non-Binary Sequence (cont.)

 - Alternatively, we use
 - Next-state maps (Q^+) to find T_C , T_B , T_A .
 - In C^+ map (000), when $C = 0$, $C^+ = 1$, so $T_C = 1$. $T = 1$ whenever $Q^+ \neq Q$.




(a) Next-state maps for Table 12-3

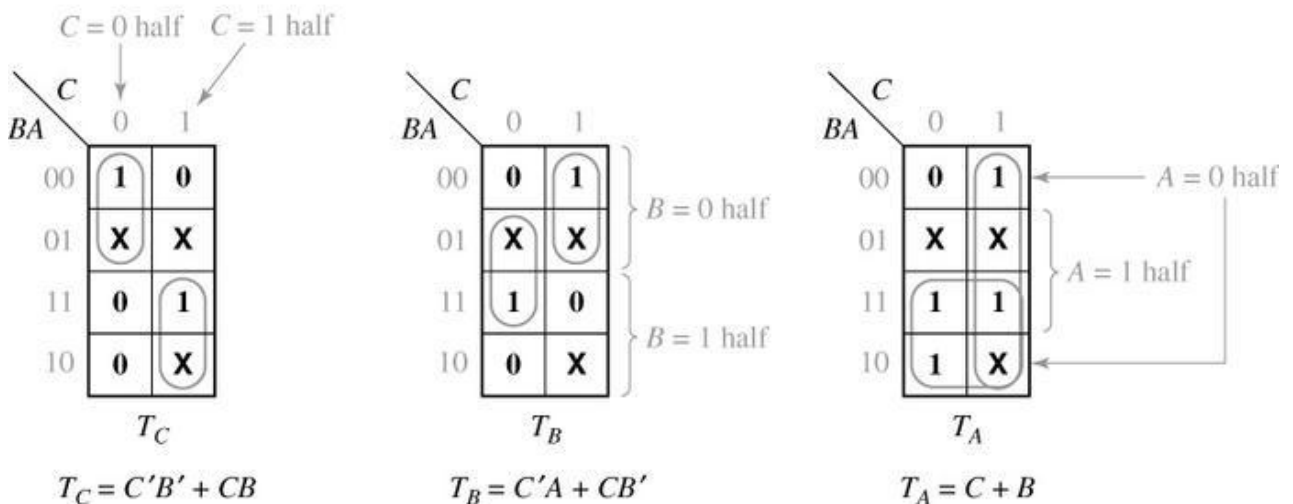

 
(b) Derivation of T inputs

Counters with Non-Binary Sequence (cont.)

- Using clocked T FF.
 - Next-state maps
 - $T = 1$ whenever $Q^+ \neq Q$, which means $T = Q^+ \oplus Q$.





Input for T Flip-Flop

 

Counters with Non-Binary Sequence (cont.)

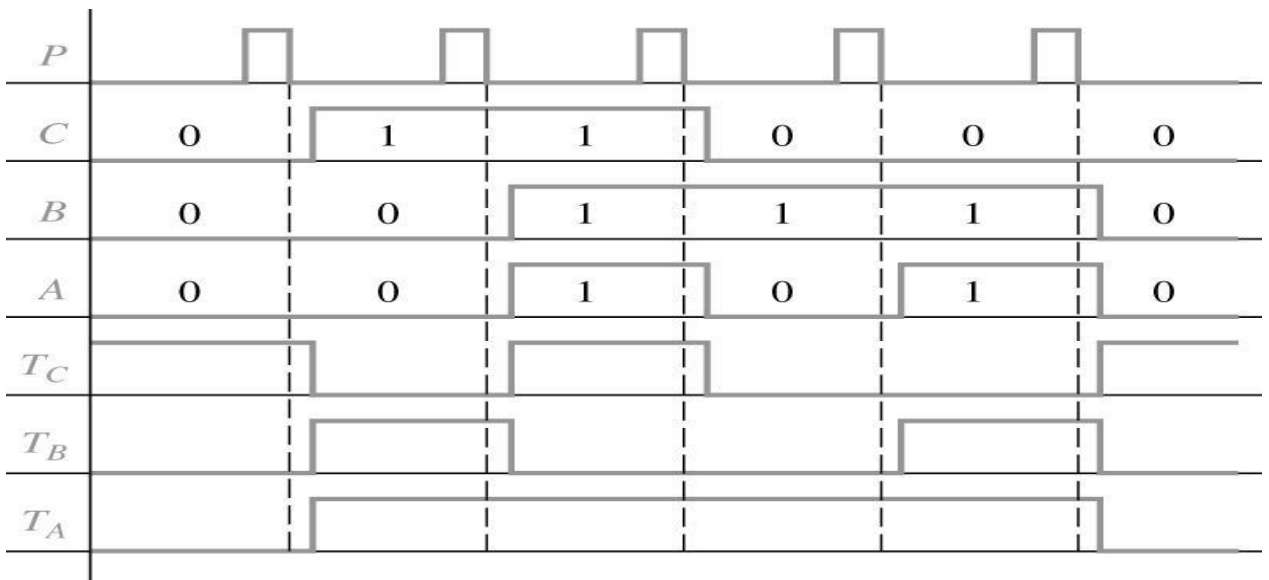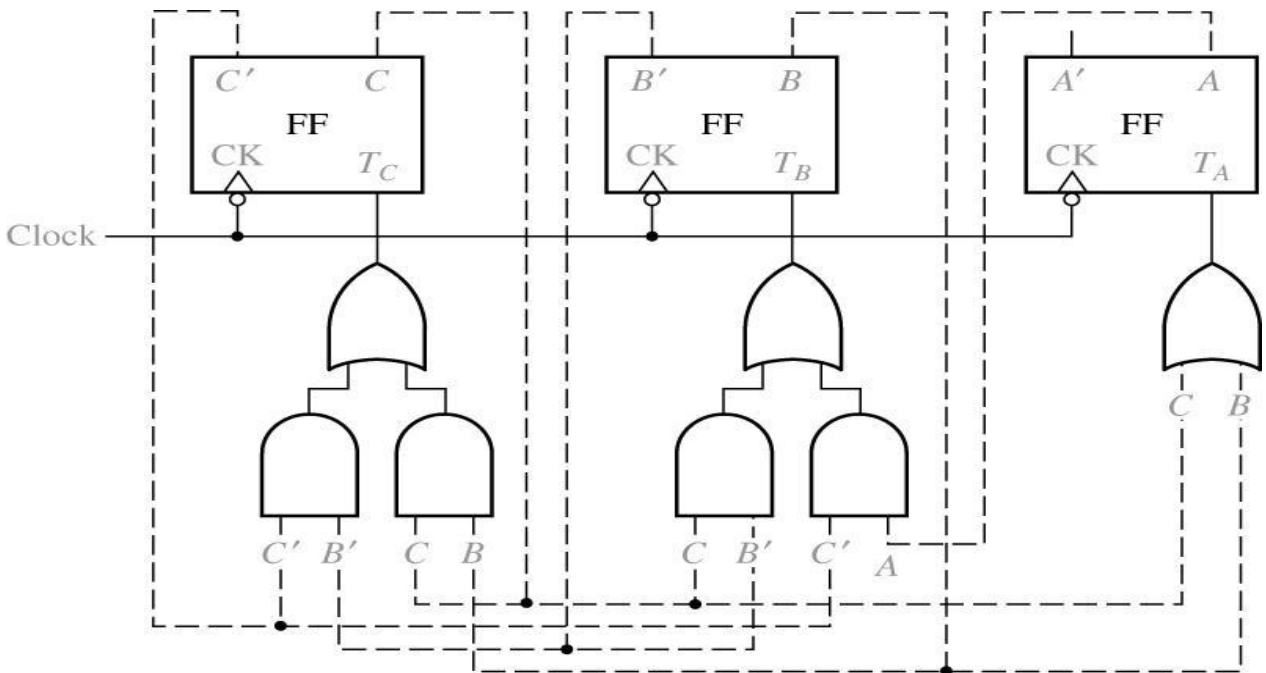- The resultant circuit and timing diagram.



Counters with Non-Binary Sequence (cont.)

- Summary of procedure
 - Form a state table of Q and Q^+
 - Plot Q^+ map with respect to Q .
 - Plot T map w.r.t Q . T_Q map is formed from the Q^+ map by complementing the $Q = 1$ entries and leaving $Q = 0$ entries unchanged.
 - Find input equation of each T using the T_Q map.

Counter Using S-R FF

- S-R Table

- Problem (the same counter)
- Get S_A from Table 12-5 (c)

TABLE 12-5
S-R Flip-Flop
Inputs

| | | (a) | |
|---|---|-----|----------------|
| S | R | Q | Q ⁺ |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | - |
| 1 | 1 | 1 | - |

} inputs not
} allowed

| | | (b) | |
|---|----------------|-----|---|
| Q | Q ⁺ | S | R |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |


| | | (c) | |
|---|----------------|-----|---|
| Q | Q ⁺ | S | R |
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | X | 0 |

TABLE 12-6


| C | B | A | C ⁺ | B ⁺ | A ⁺ | S _C | R _C | S _B | R _B | S _A | R _A |
|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | X | 0 | X |
| 0 | 0 | 1 | - | - | - | X | X | X | X | X | X |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X | X | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | X | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | X | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | - | - | - | X | X | X | X | X | X |
| 1 | 1 | 0 | - | - | - | X | X | X | X | X | X |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | X | 0 | 0 | 1 |

Counter Using S-R FF

 
- Get K-map (of S_A , R_A , etc) from state table.
- Problem (the same counter Fig 12-21)



(a) Next-state maps

 

(b) S-R flip-flop equations

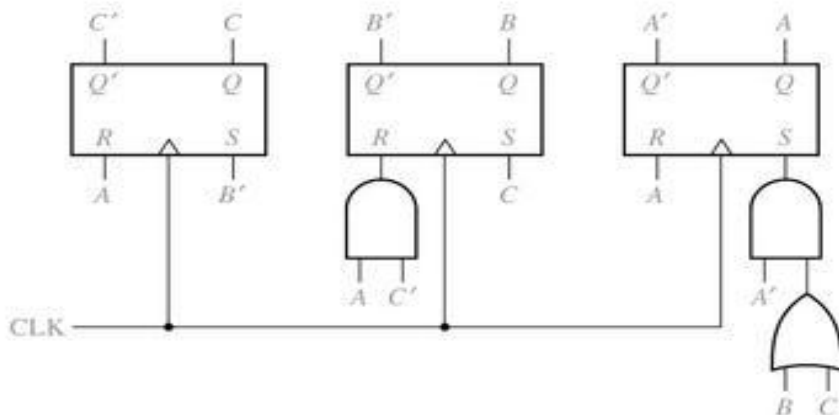

(c) Logic circuit

Counter Using Clocked J-K FF

- Procedure is similar to S-R FF.

TABLE 12-7
J-K Flip-Flop
Inputs


| (a) | | | | (b) | | | | (c) | | | |
|-----|---|---|----------------|-----|----------------|---|---|-----|----------------|---|---|
| J | K | Q | Q ⁺ | Q | Q ⁺ | J | K | Q | Q ⁺ | J | K |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | X |
| 0 | 0 | 1 | 1 | | | | | 0 | 1 | 1 | X |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | X | 1 |
| 0 | 1 | 1 | 0 | | | | | 1 | 1 | X | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | | |
| 1 | 0 | 1 | 1 | | | | | 1 | 1 | | |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | | |
| 1 | 1 | 1 | 0 | | | | | 1 | 0 | 1 | 0 |

TABLE 12-8


| C | B | A | C ⁺ | B ⁺ | A ⁺ | J _C | K _C | J _B | K _B | J _A | K _A |
|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | X | 0 | X | 0 | X |
| 0 | 0 | 1 | - | - | - | X | X | X | X | X | X |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 | X | X | 0 | 1 | X |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | X | X | 1 | X | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | X | 0 | 1 | X | 1 | X |
| 1 | 0 | 1 | - | - | - | X | X | X | X | X | X |
| 1 | 1 | 0 | - | - | - | X | X | X | X | X | X |
| 1 | 1 | 1 | 0 | 1 | 0 | X | 1 | X | 0 | X | 1 |

Counter Using Clocked J-K FF (cont.)


- Find J-K input equations

 

(a) Next-state maps

 

(b) J-K flip-flop input equations

 

(c) Logic circuit (omitting the feedback lines)