


Lecture 12

Analysis of Clocked Sequential Network

- Given a sequential network and input sequence, analyze the network to determine the FF state sequence and output sequence.
 - First by tracing the 1 and 0 signals through the network.
 - Next by constructing a state graph or state table to represent the behavior of the network.


A Sequential Parity Checker

- Parity
 - Odd parity and even parity.
 - Add 1 or 0 to a datum so that the total number of 1's is odd (odd parity) or even (even parity).
 - Error detection.
- Example
 - Serial data input, one bit at a time.
 - Output $Z = 1$ if total number of 1 inputs received is odd.
 - If the input is odd parity, and the final output $Z = 1$. This is correct.
 - A final output $Z = 0$ indicates that an error in transmission has occurred.

 


A Sequential Parity Checker (cont.)

 - Assume that X is synchronized with the clock and changes only between clock pluses.
- X is determined at the active clock edge.
- Clock input is used to distinguish consecutive 0's or 1's.



A Sequential Parity Checker (cont.)

 - A state graph
 - S_0 : even number of 1's received
 - S_1 : odd number of 1's received.



- State table

Table 13-1
State Table for Parity Checker

Present State	(a) Next State		Present Output
	$X=0$	$X=1$	
S_0	S_0	S_1	0
S_1	S_1	S_0	1

Q	(b) Q^+		T		Z
	$X=0$	$X=1$	$X=0$	$X=1$	
0	0	1	0	1	0
1	1	0	0	1	1

A Sequential Parity Checker (cont.)

- Two states are required. We can use a FF.
 - A T FF can be used. When Q and Q^+ differs, $T = 1$. Note that T is input to FF. Both Q and Q^+ are outputs of the FF. (Homework: Use a D FF)
 - In the table, when $X = 1$, $T = 1$, so $T = X$.

Table 13-1
State Table for Parity Checker

Present State	(a) Next State		Present Output
	$X = 0$	$X = 1$	
S_0	S_0	S_1	0
S_1	S_1	S_0	1

Q	(b) Q^+		T		Z
	$X = 0$	$X = 1$	$X = 0$	$X = 1$	
0	0	1	0	1	0
1	1	0	0	1	1

 


Figure 13-4


Analysis by Signal Tracing and Timing Charts

- Given a clocked sequential network, procedure for analysis is as follows:
 - Assume initial state (0) for FF.
 - For the first input in the given sequence, determine the network output and the FF inputs.
 - Apply clock to the FFs and determine the new FF states after the next active clock edge.
 - Determine the outputs due to the new state.
 - Repeat for each input in the given sequence sequence.
- This is a timing chart.

Moore Machine


– Output depends on only the present state of FF. This network is referred to as a Moore machine. (Output displaces w.r.t. input in Moore network)

 - $X = 0\ 1\ 1\ 0\ 1$
- $A = 0\ 1\ 0\ 1\ 0\ 1$
- $B = 0\ 0\ 1\ 1\ 1\ 1$
- $Z = (0)1\ 1\ 0\ 1\ 0$





Moore Machine (cont.)

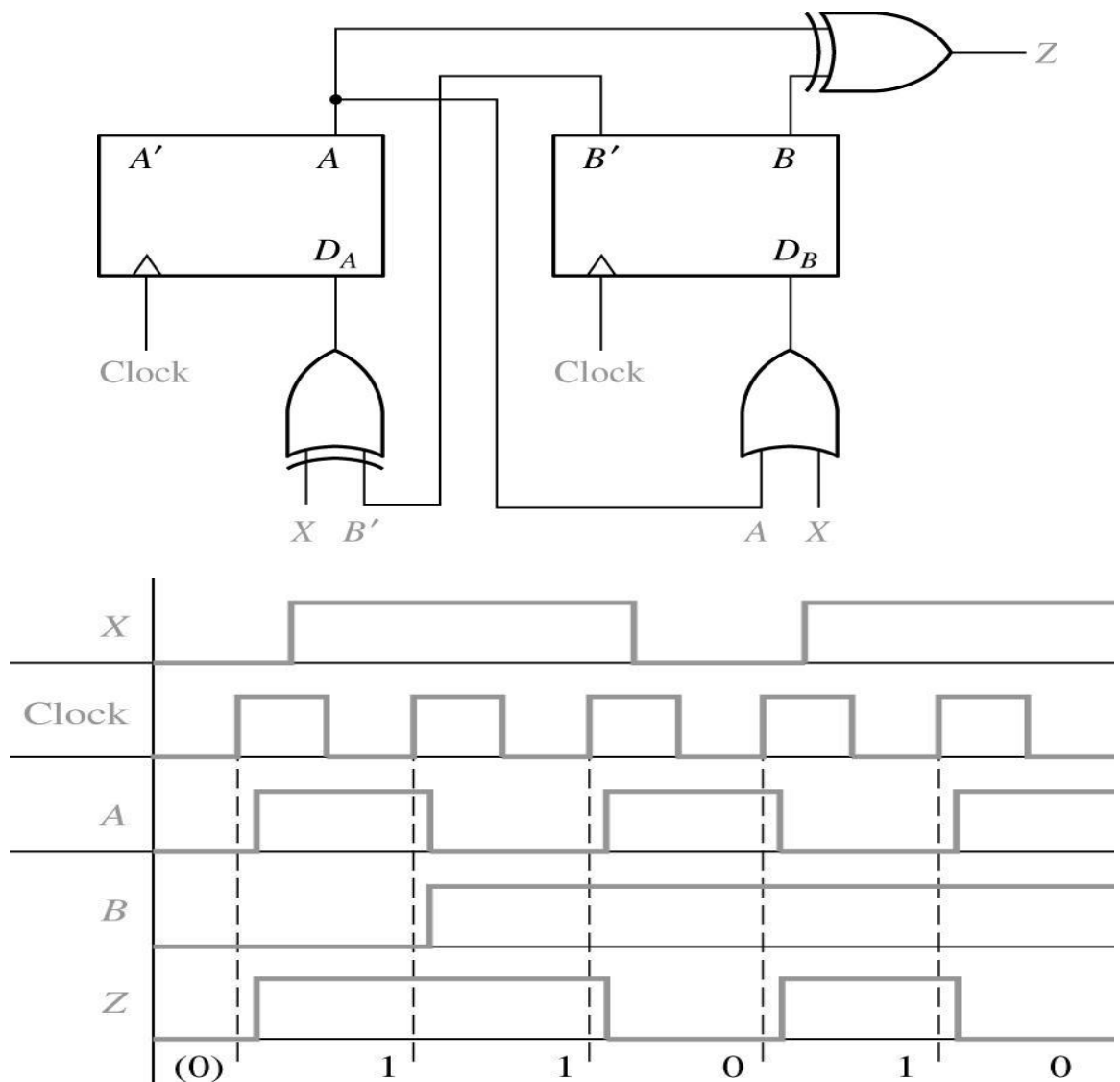- Assume $X = 01101$
 - Initially, $X = 0$, $D_A = 1$, $D_B = 0$. So after rising clock edge, $A = 1$, and $B = 0$.



Mealy Machine

  - Output depends on the input and the FF states. That is, Z may change either when input changes or the FF state changes.
- Example: Output does not displace w.r.t input. Input dominates.



Mealy Machine (cont.)

- $X = 1 \ 0 \ 1 \ 0 \ 1$
- $A = 0 \ 0 \ 0 \ 1 \ 1 \ 0$
- $B = 0 \ 1 \ 1 \ 1 \ 1 \ 0$
- $Z = 1(0)1 \ 0(1)0 \ 1$ (glitches or spikes)

False 0
output


 


Figure 13-8
Timing Chart for Network of Fig. 13-7

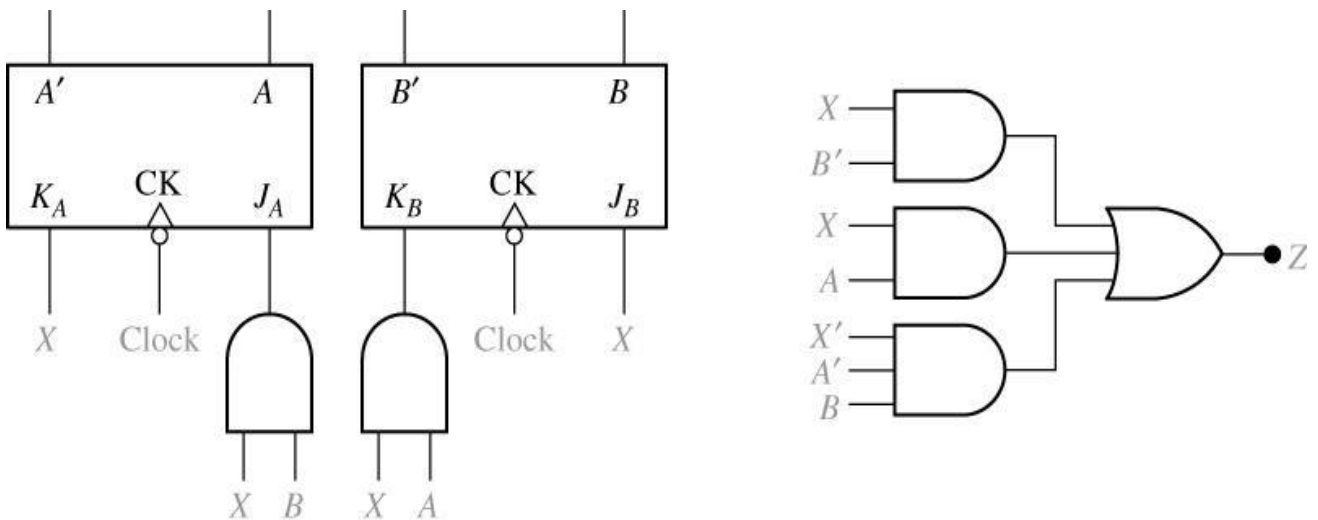

State table and graph constructions

- State table constructions
 - Network inputs, present state, and next state.
 - Determine the FF input equation and output equations.
 - Derive the next-state equations for each FF from its input equations using
 - $Q^+ = D$
 - $Q^+ = T \oplus Q$
 - $Q^+ = S + R'Q$
 - $Q^+ = JQ' + K'Q$
 - Plot a next-state map
 - Combine these maps to form state table. (This is also called a transition table.)

Example: State Table

- Step (Moore machine)
 - Input equations and output equation
 - $D_A = X \oplus B'$, $D_B = X + A$, $Z = A \oplus B$
 - Next state equations
 - $A^+ = X \oplus B'$
 - $B^+ = X + A$
 - Next state K map: $A^+ = f(A, B, X)$. A next state = function of present states and inputs

		X	
		0	1
AB	00	1	0
	01	0	1
	11	0	1
	10	1	0

A^+

		X	
		0	1
AB	00	0	1
	01	0	1
	11	1	1
	10	1	1

B^+

Example: State Table (cont.)

- Moore State table

 


TABLE 13-2
Moore State
Tables for
Figure 13-5

AB	(a) A^+B^+		Z	Present State	(b) Next State		Present Output (Z)
	X = 0	X = 1			X = 0	X = 1	
00	10	01	0	S_0	S_3	S_1	0
01	00	11	1	S_1	S_0	S_2	1
11	01	11	0	S_2	S_1	S_2	0
10	11	01	1	S_3	S_2	S_1	1

State Graph

- Moore State graph

 


TABLE 13-2
Moore State
Tables for
Figure 13-5

AB	(a) A ⁺ B ⁺		Z	Present State	(b) Next State		Present Output (Z)
	X = 0	X = 1			X = 0	X = 1	
00	10	01	0	S ₀	S ₃	S ₁	0
01	00	11	1	S ₁	S ₀	S ₂	1
11	01	11	0	S ₂	S ₁	S ₂	0
10	11	01	1	S ₃	S ₂	S ₁	1

Mealy Machine Example

- Next state equation
 - $A^+ = J_A A' + K_A A = XBA' + X'A$
 - $B^+ = J_B B' + K_B B = XB' + (AX)'B = XB' + X'B + A'B$
 - $Z = X'A'B + XB' + XA$

		X	
		0	1
AB	00	0	0
	01	0	1
11	1	0	
10	1	0	

A^+

		X	
		0	1
AB	00	0	1
	01	1	1
11	1	0	
10	0	1	

B^+

		X	
		0	1
AB	00	0	1
	01	1	0
11	0	1	
10	0	1	

Z

Mealy Machine Example

- State table

 


TABLE 13-3
Mealy State
Tables for
Figure 13-7

(a)

AB	A^+B^+		Z	
	$X=0$	1	$X=0$	1
00	00	01	0	1
01	01	11	1	0
11	11	00	0	1
10	10	01	0	1

(b)

Present State	Next State		Present Output	
	$X=0$	1	$X=0$	1
S_0	S_0	S_1	0	1
S_1	S_1	S_2	1	0
S_2	S_2	S_0	0	1
S_3	S_3	S_1	0	1

Example: Mealy Machine (cont.)

- Mealy state graph
 - If present input changes, the output will change *immediately*. But the present state will not change until after the clock edge.

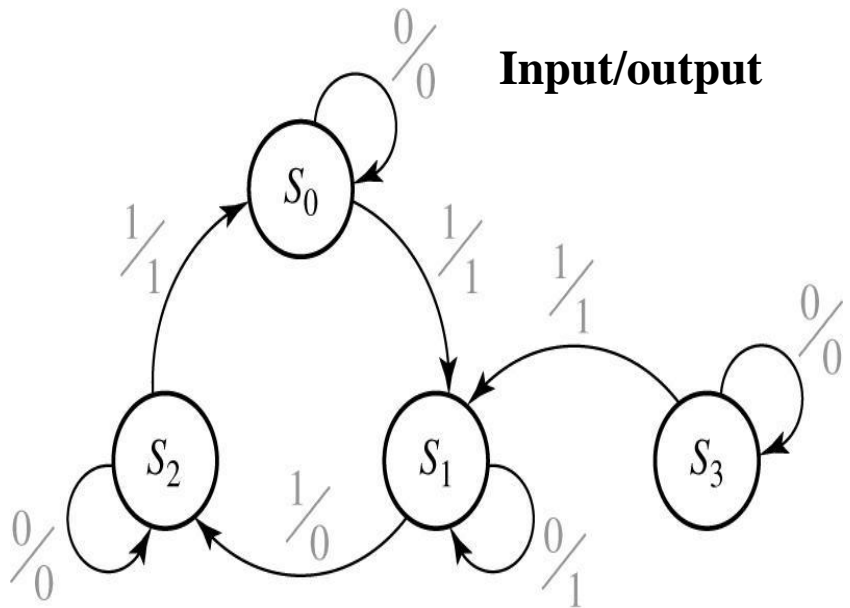


TABLE 13-3
Mealy State
Tables for
Figure 13-7

(a)

AB	A ⁺ B ⁺		Z	
	X = 0	1	X = 0	1
00	00	01	0	1
01	01	11	1	0
11	11	00	0	1
10	10	01	0	1


(b)

Present State	Next State		Present Output	
	X = 0	1	X = 0	1
S ₀	S ₀	S ₁	0	1
S ₁	S ₁	S ₂	1	0
S ₂	S ₂	S ₀	0	1
S ₃	S ₃	S ₁	0	1

A Serial Adder


- Two operands are fed in serially beginning at x_0, y_0 (store carry)

FIGURE 13-12
Serial Adder

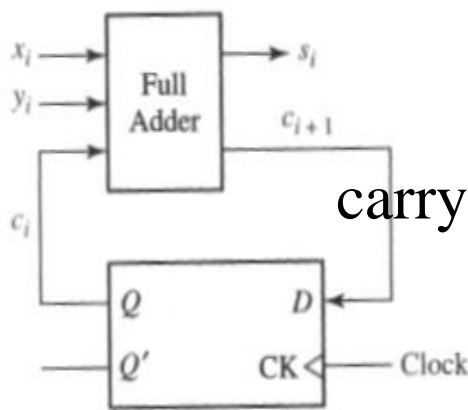

x_i	y_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Read answer (s) before the rising edge

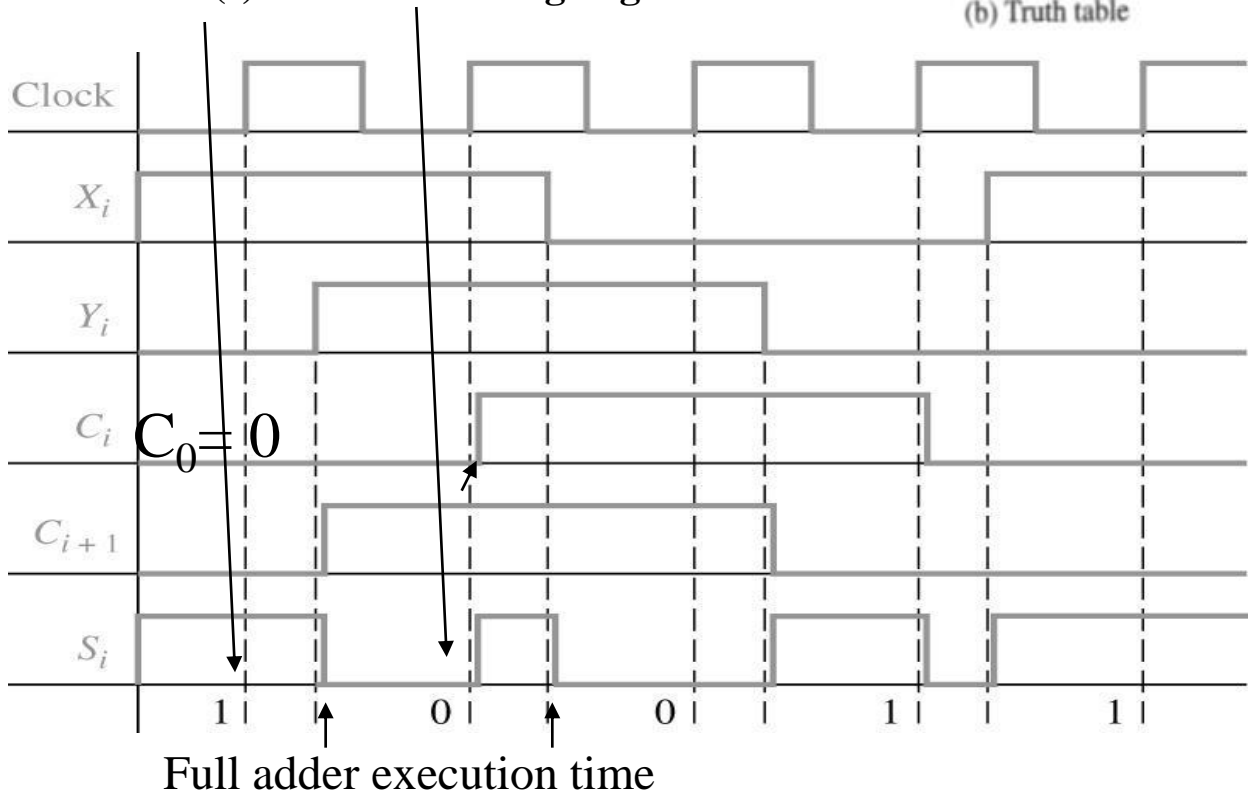

Serial Adder

- Mealy machine (S_0 $c_i = 0$, S_1 : $c_i = 1$)


 


FIGURE 13-12
Serial Adder

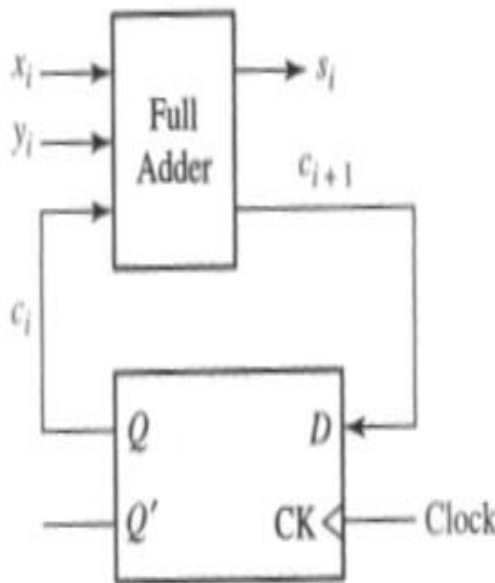

(a) With D flip-flop

x_i	y_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


(b) Truth table

Multiple Inputs/Outputs

- **00,01/00** means if $X_1 = X_2 = 0$ or $X_1 = 0$ and $X_2 = 1$, then $Z_1 = 0$ and $Z_2 = 0$.

TABLE 13-4
A State Table with
Multiple Inputs
and Outputs

Present State	Next State				Present Output (Z_1, Z_2)			
	$X_1 X_2 = 00$	01	10	11	$X_1 X_2 = 00$	01	10	11
S_0	S_3	S_2	S_1	S_0	00	10	11	01
S_1	S_0	S_1	S_2	S_3	10	10	11	11
S_2	S_3	S_0	S_1	S_1	00	10	11	01
S_3	S_2	S_2	S_1	S_0	00	00	01	01

 

Timing Chart

- State change occurs after the falling (rising) edge of the clock.
- Input will normally be stable immediately before and after the active clock edge.
- For a Moore circuit, the output changes only when the state changes.
- For a Mealy circuit, the output can change when the input changes and when the state changes.

Timing Charts (cont.)




- For a Mealy circuit, a false output may occur between the time the state changes and the time the input is changed.
 - If the state has changed to its next value, but the old input is still present, the output may be temporarily incorrect.
 - False outputs are difficult to determine from the state graph.
 - Use signal tracing or
 - Use the state table.

Timing Chart Constructions

- Procedures: using a Mealy state table to construct a timing chart (given an input sequence).
 - For the first input, read the present output and plot it.
 - Read the next state and plot it (following the active edge of the clock).
 - Go to the row in the table which corresponds to the next state and read output under the old input column and plot it. (This may be a false output.)
 - Change to the next input and repeat
- For a Mealy circuit, the best time to read the output is just before the active edge of the clock.

Interpretation of Timing Chart

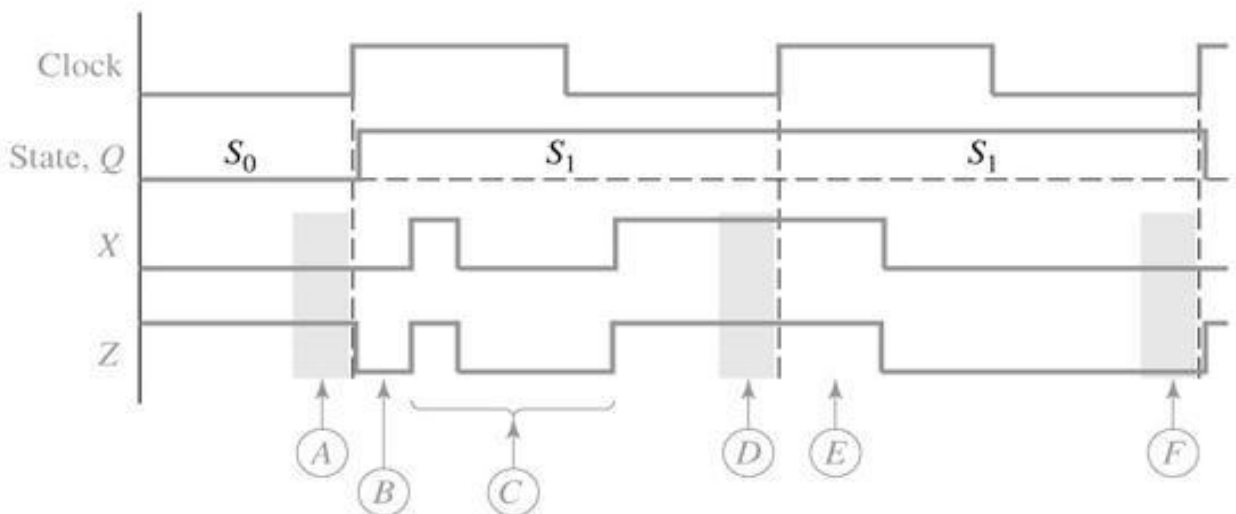  
- Read output before the rising edge of the clock.



Read X and Z in shaded area (before rising edge of clock).

General Model

- Mealy network using D FF

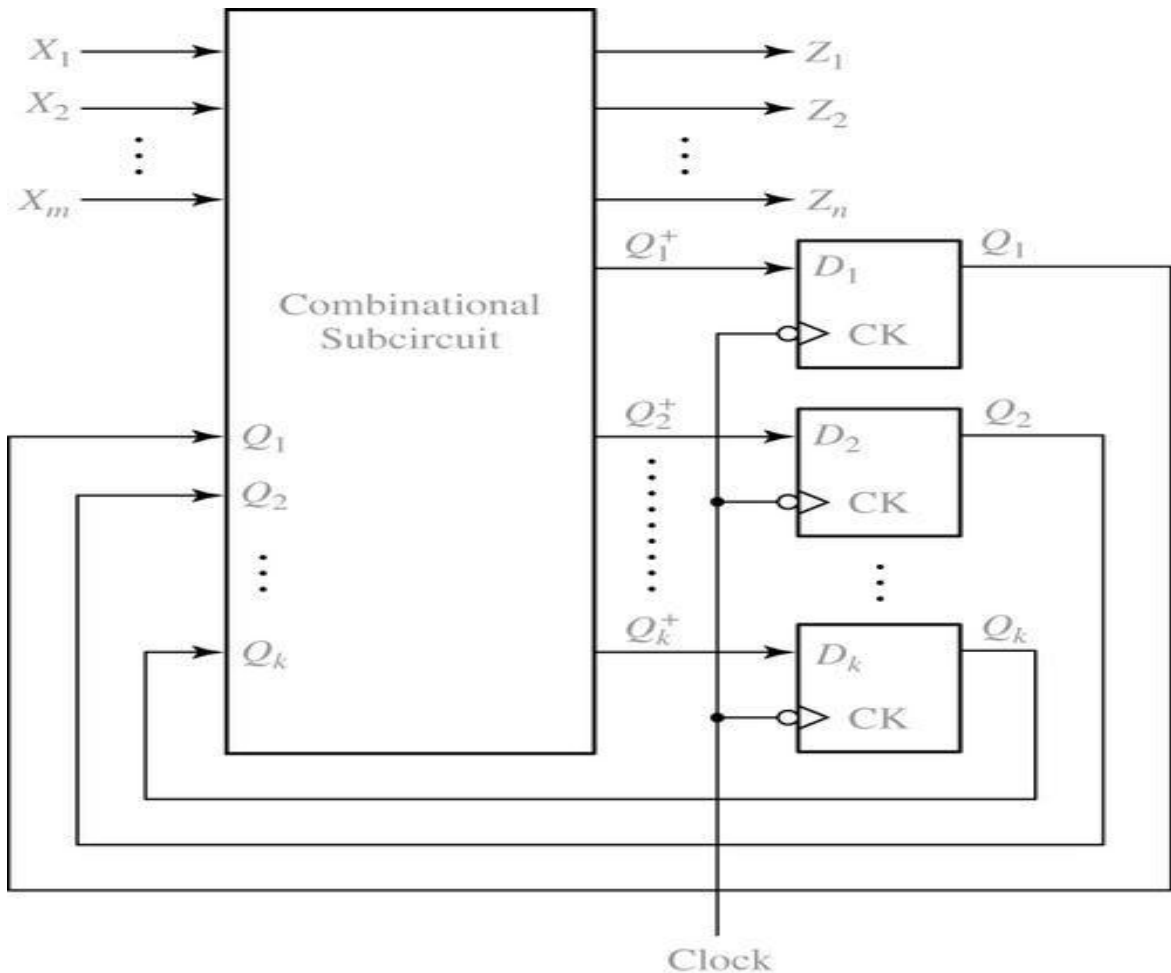


$$\left. \begin{aligned} Z_1 &= f_1(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k) \\ Z_2 &= f_2(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k) \\ &\vdots \\ Z_n &= f_n(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k) \end{aligned} \right\} n \text{ output functions}$$

$$\left. \begin{aligned} Q_1^+ &= D_1 = g_1(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k) \\ Q_2^+ &= D_2 = g_2(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k) \\ &\vdots \\ Q_k^+ &= D_k = g_k(X_1, X_2, \dots, X_m, Q_1, Q_2, \dots, Q_k) \end{aligned} \right\} k \text{ next-state functions}$$

Clock Period

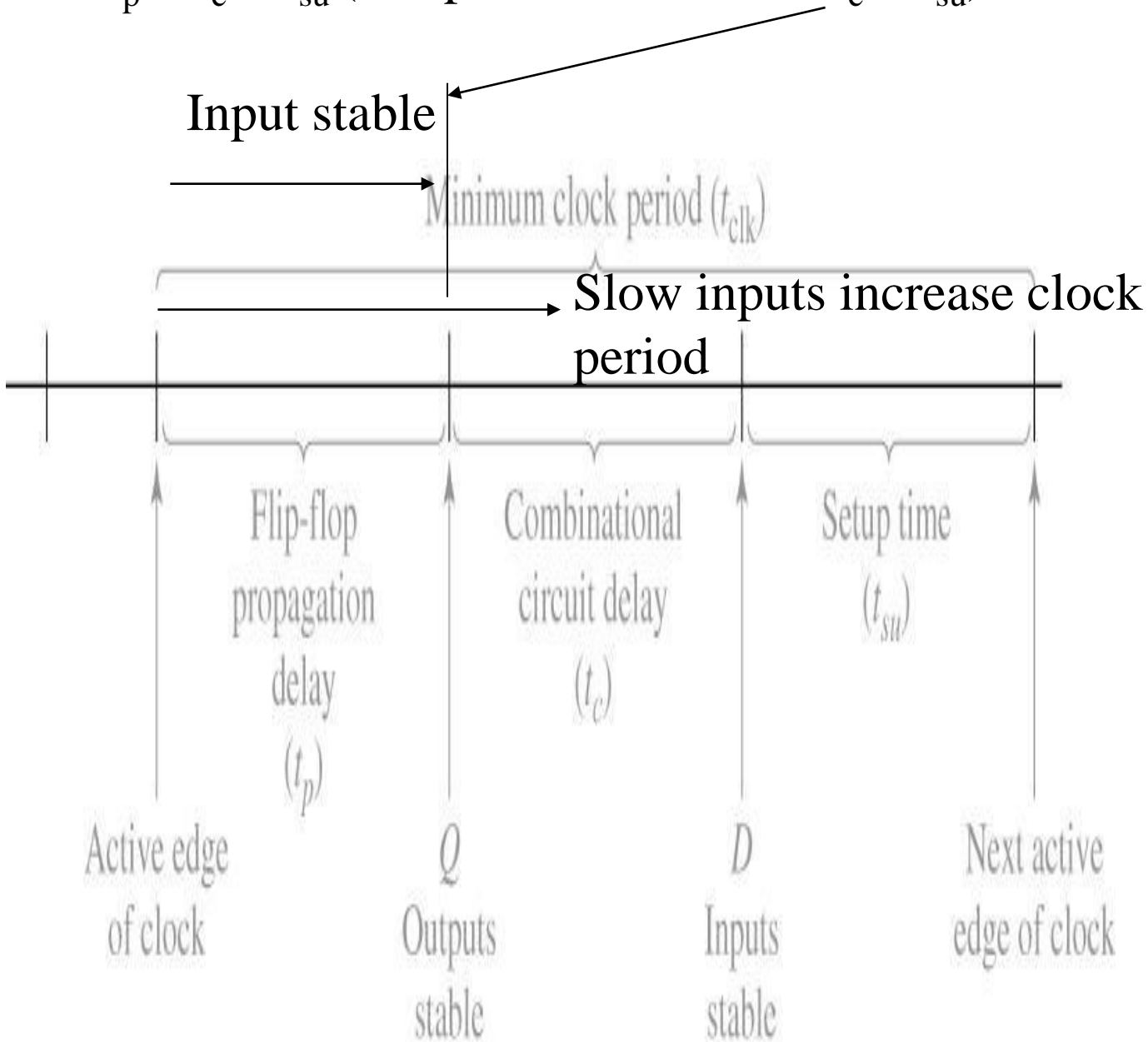- Minimum clock period for Mealy circuit = $t_p + t_c + t_{su}$ (if inputs stable before $t_c + t_{su}$)



General Model

- Moore network using D FF
 - Outputs are only a function of the present state of the FFs and not a function of the inputs.

