


# Lecture 16

## Arithmetic Circuits

- Serial adder
- Parallel multiplier
- Divider
- Control circuit outputs a sequence of control signals that cause arithmetic operation to take place at appropriate times.

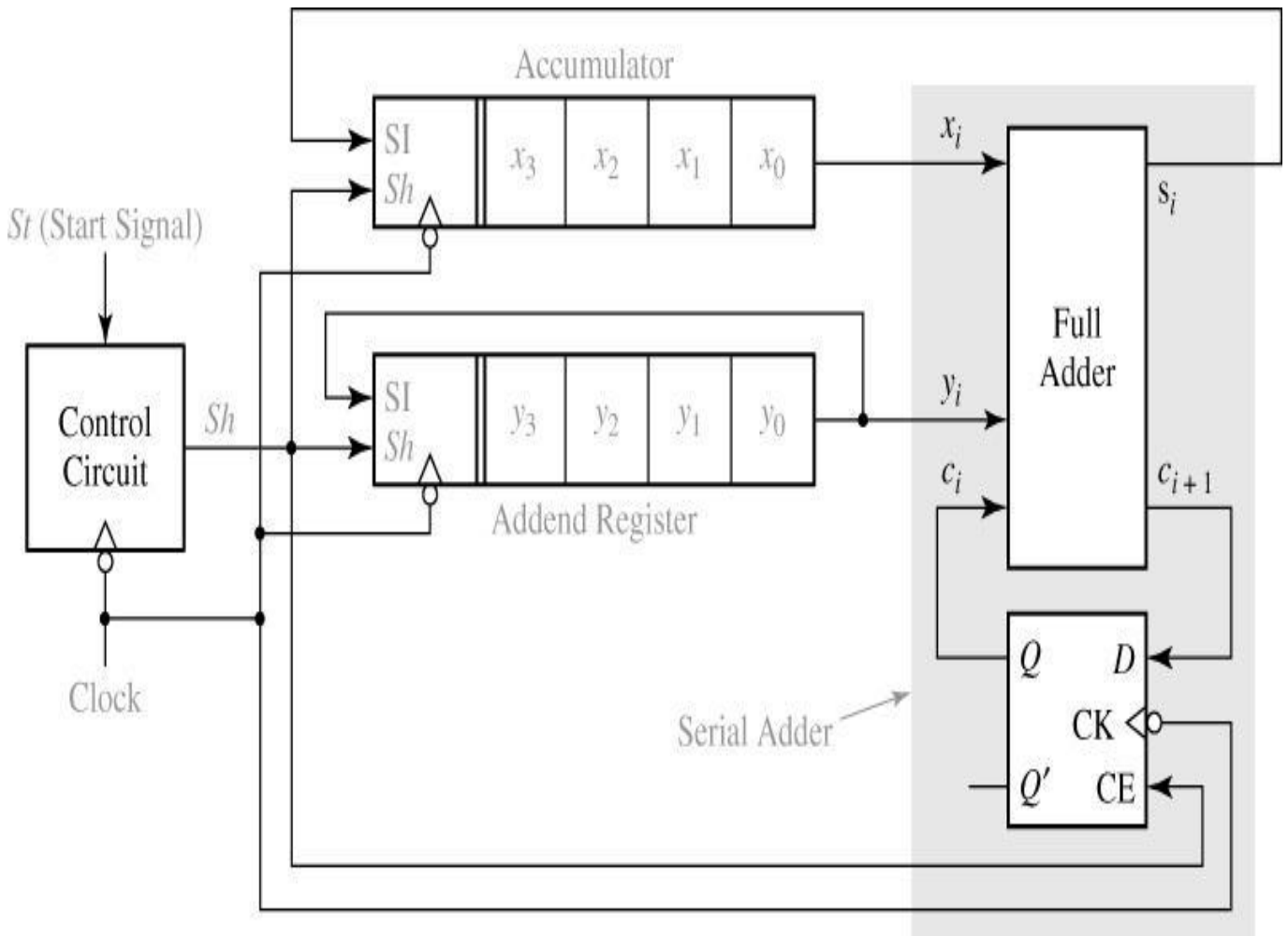
# Serial Adder

- **X register**
  - Accumulator:  $X = X + Y$
- **Y register**
  - Addend register: cyclic shift register
    - after shifting 4 times, it is back in its original state
- Sh: shift signal
- SI: serial input




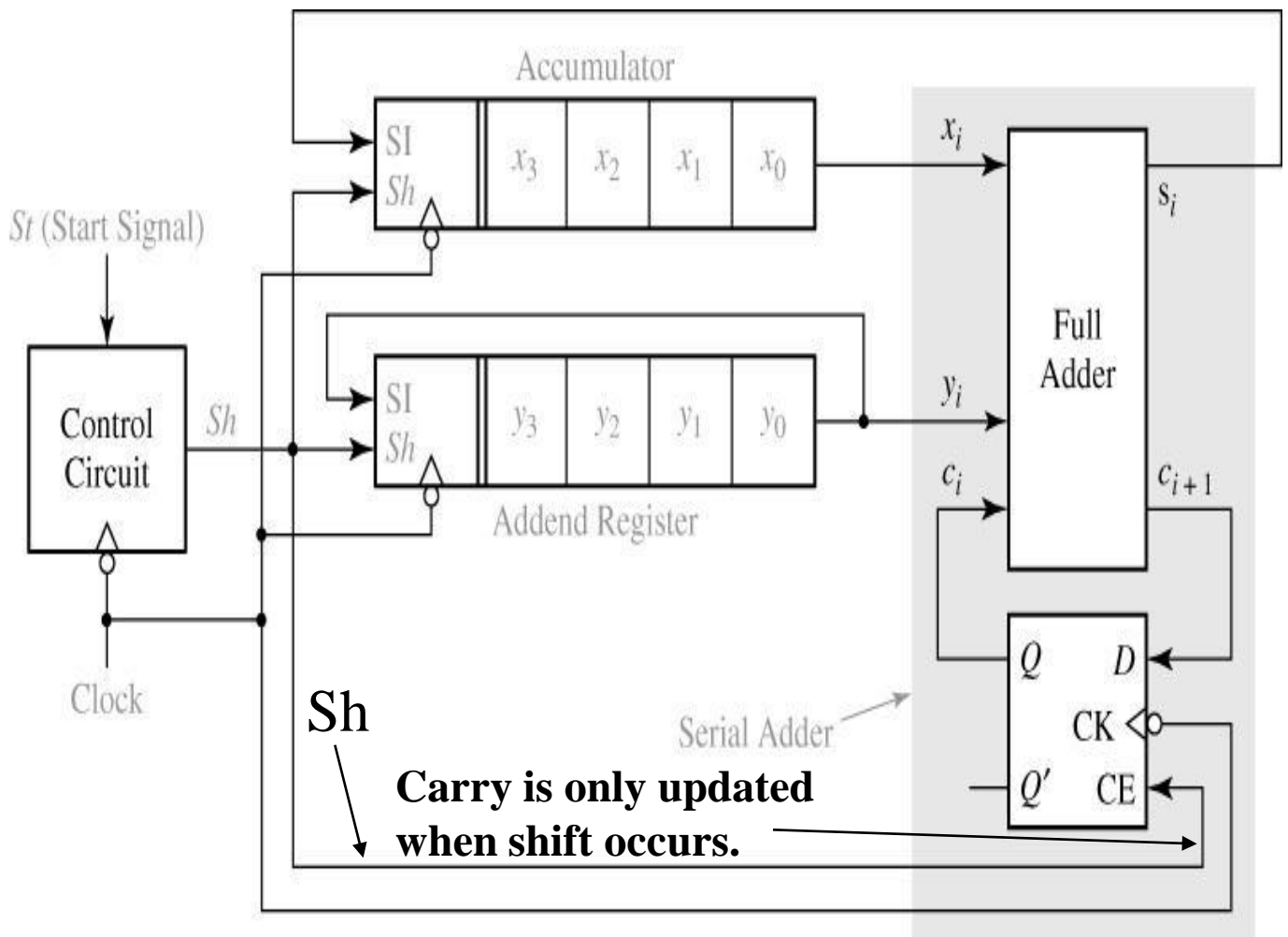
# Serial Adder

- **At the falling clock edge and  $Sh=1$** 
  - $S_i$  (sum  $b_i$ ) is shifted into  $x$
  - Carry bit is stored in the D FF.
  - Register  $y$  is rotated one bit to the right.
  - Initial loading circuit not shown.





# Serial Adder

- At the falling clock edge and  $Sh=1$

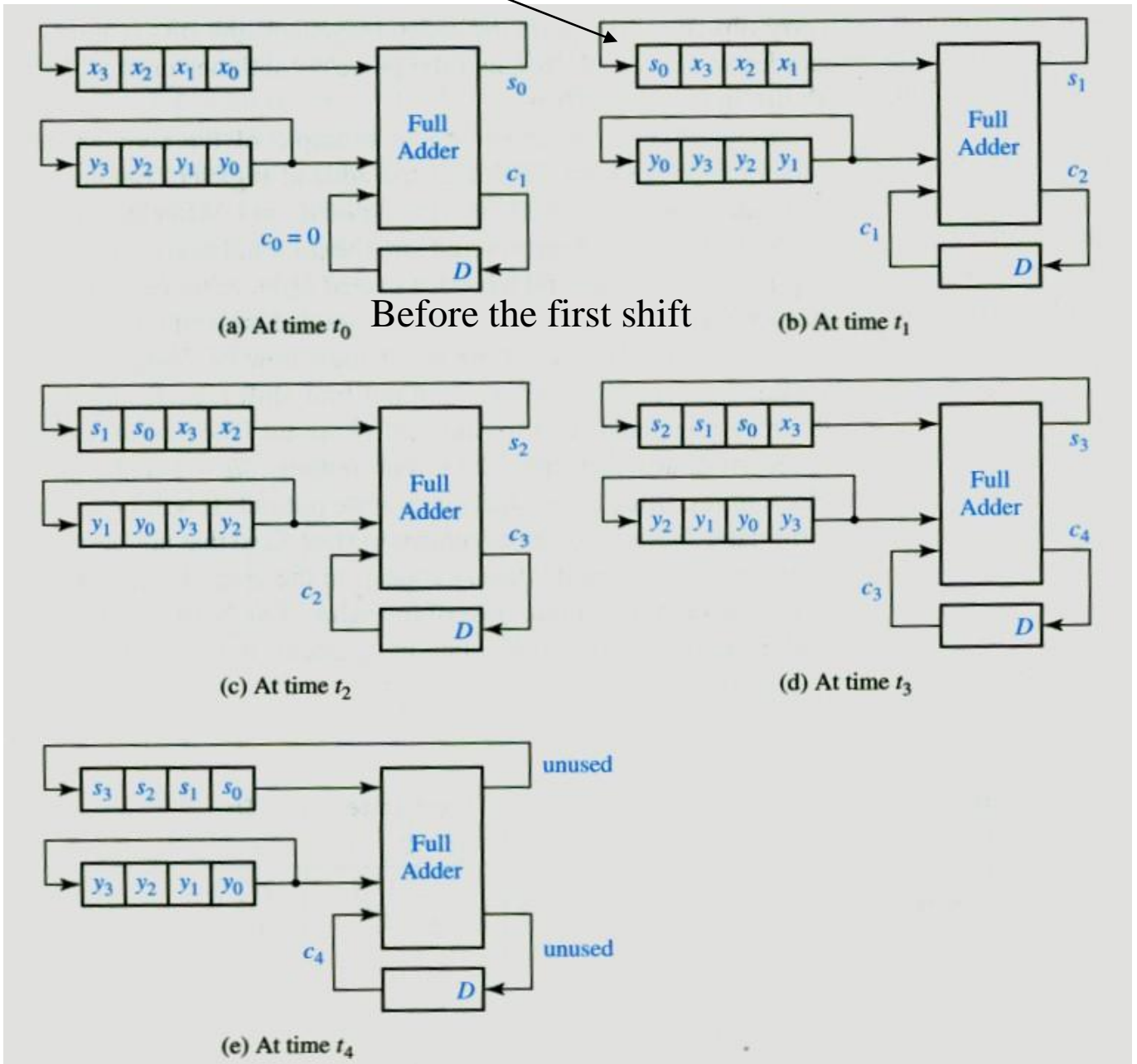 

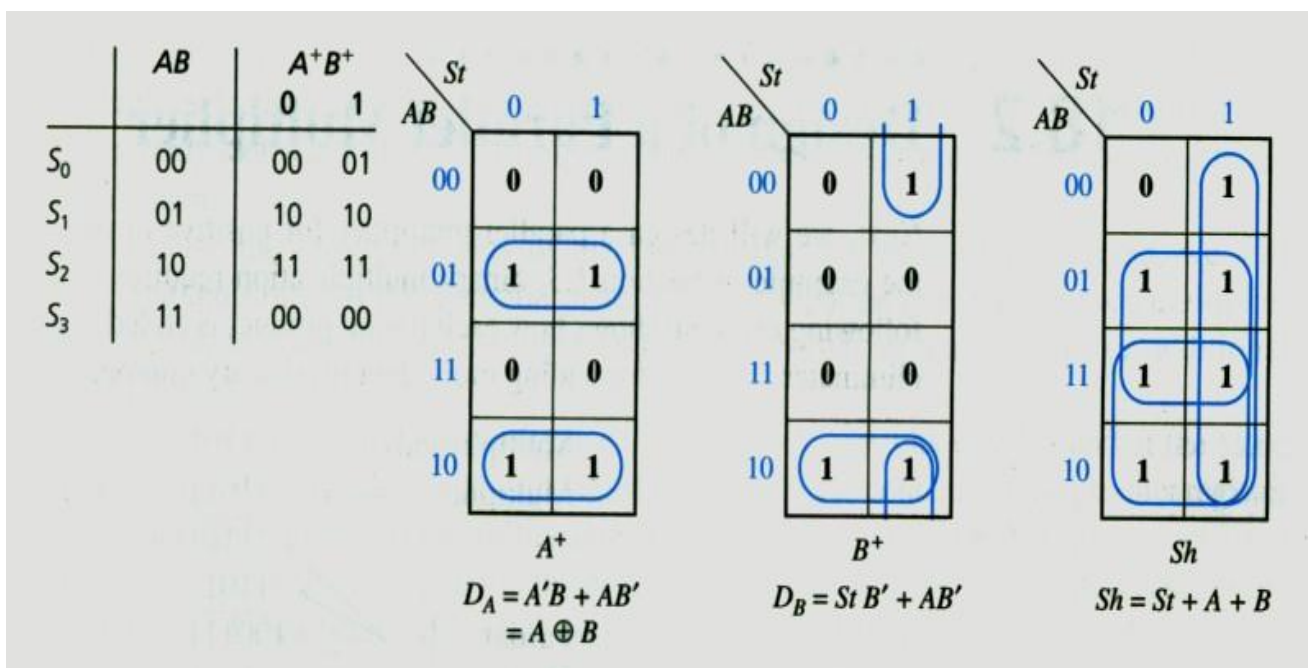 
# Control Unit Realization

- A start signal:  $St$ .
  - If  $St$  is asserted, then the control unit puts out 4 shift signals then stops.



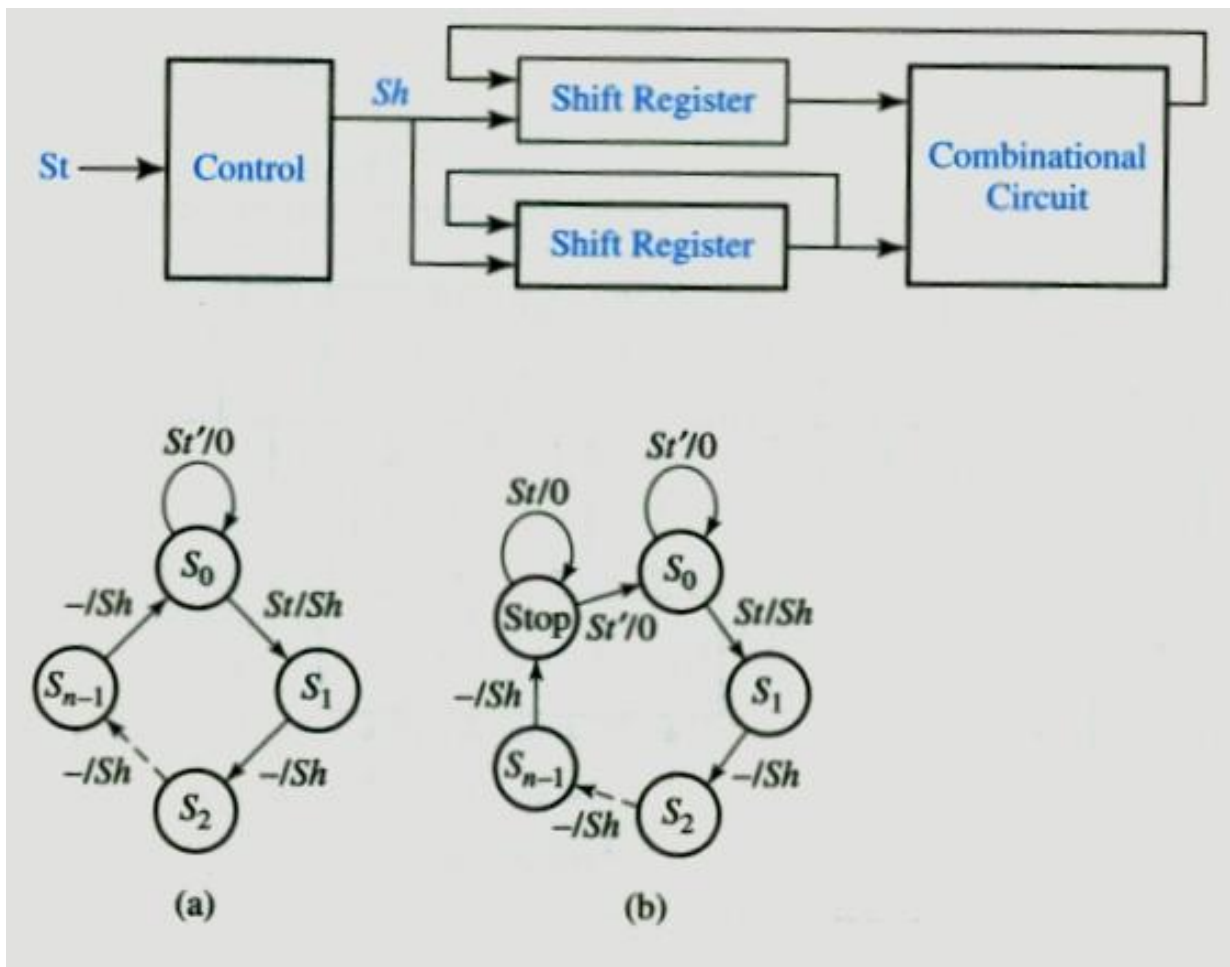
# Serial Processing Unit

- A start signal:  $St$ .
  - If  $St$  is asserted, then the control unit puts out  $n$  shift (Fig. a)  $St = 1$  for only one clock time.
  - If  $St$  remains 1 until the shifting is completed, then a stop state is required. (Fig. b)



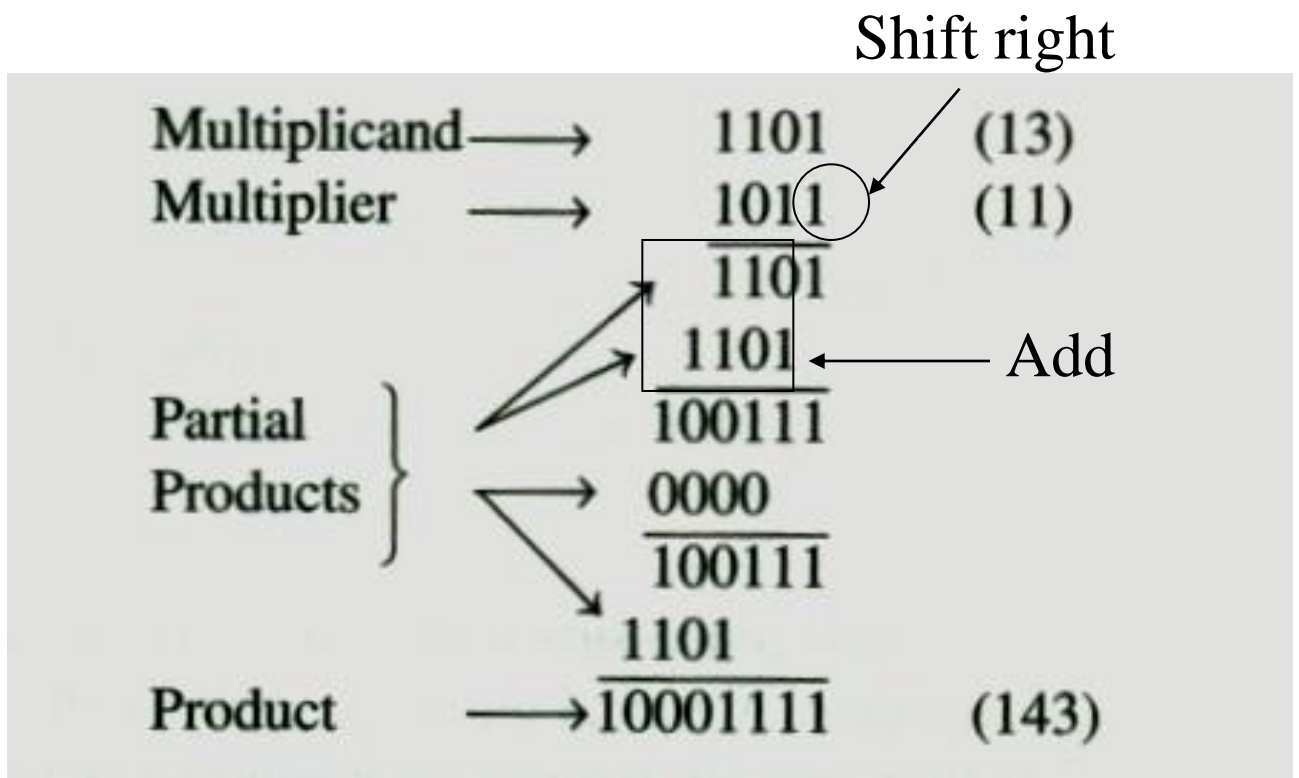
# Multiplier

- Add shift add shift add....
- Check the right most bit of the multiplier.  
1=> add + shift, 0=> shift.


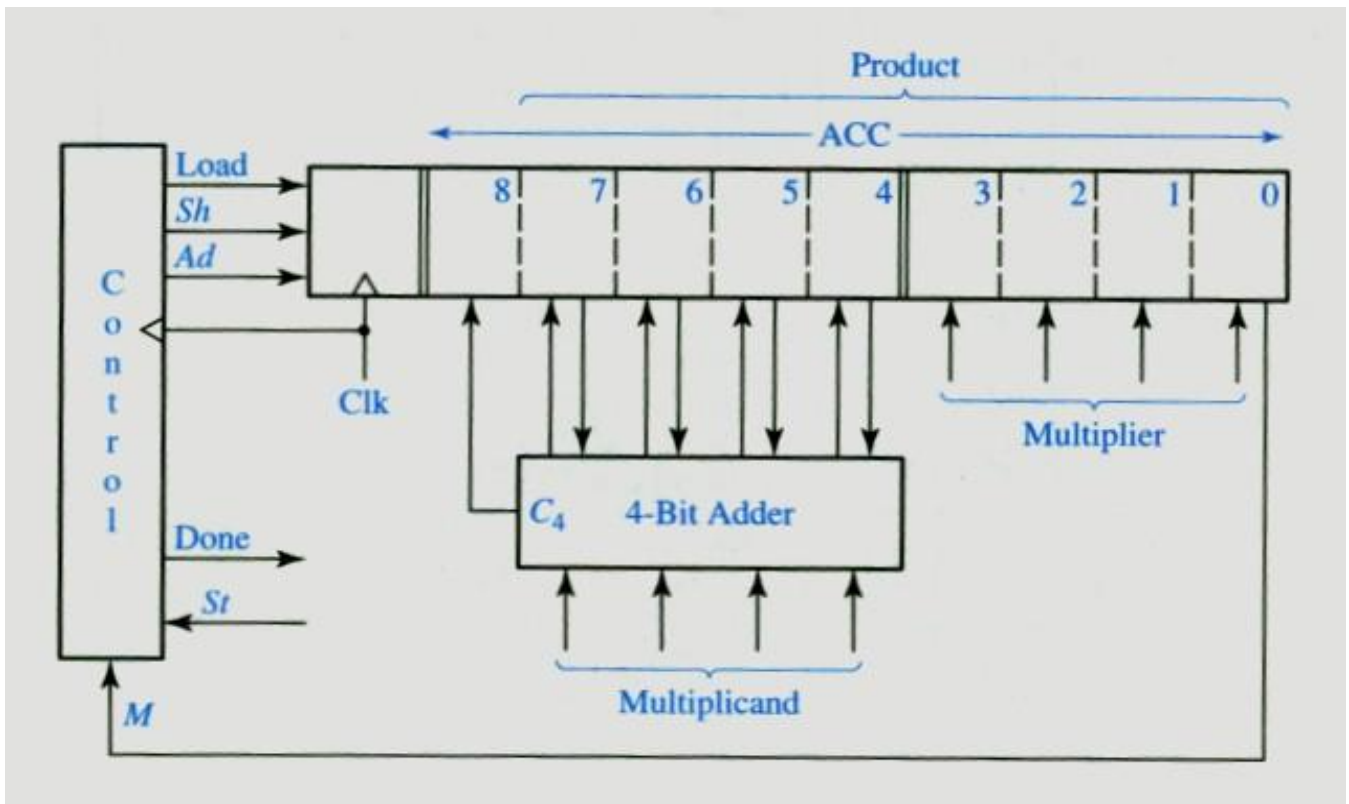
# Multiplier Diagram


- Product register [3:0] = multiplier
- Load: ACC = 00000::multiplier
- Sh: shift ACC 1 bit right.
- St: start signal, start operation.
- M bit: M= 1, add + shift. M = 0, shift.





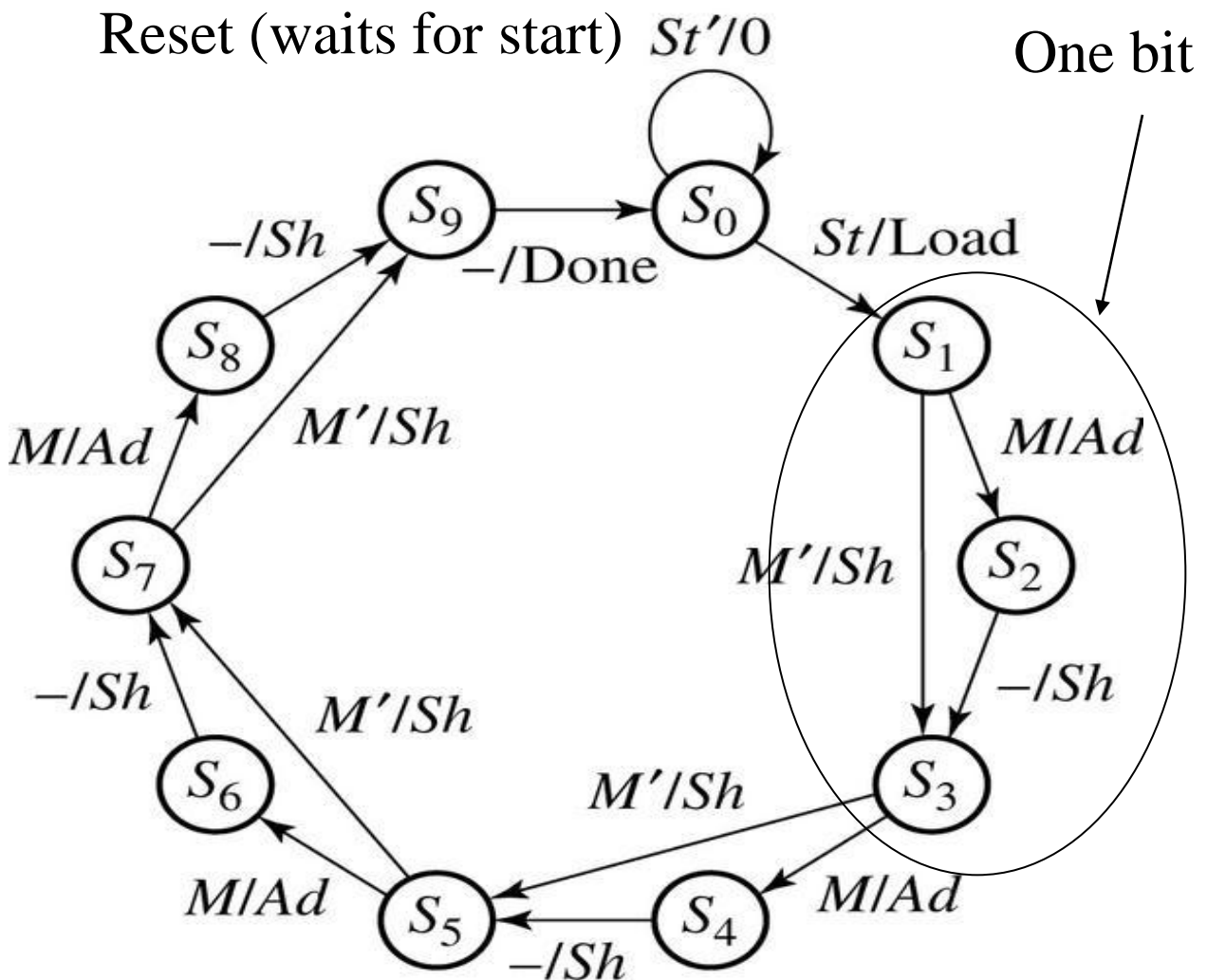
# Multiplier Control

- M/Ad: If  $M = 1$  then  $Ad = 1$ , the rest of outputs is 0.
- How many clocks are required for a multiplication?



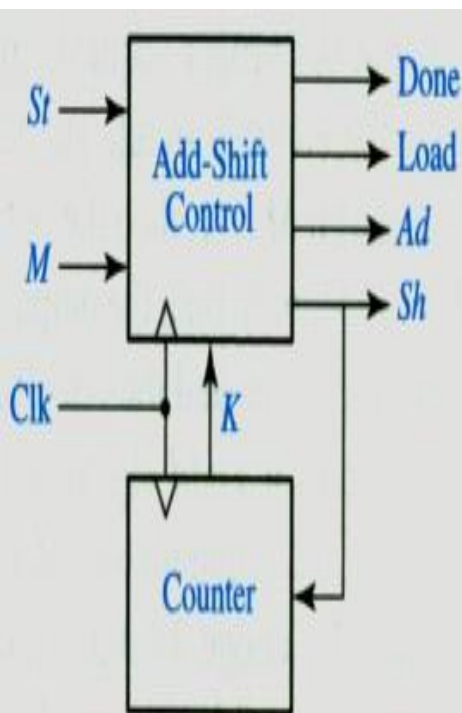
# Multiplier Control


- Multiplication for a large number of bits
- User a counter. When  $n-1$  shifts have occurred,  $K = 1$ . Then go to  $S_3$  for completion (last shift also).



(a) Multiplier control

 

(b) State graph for add-shift control

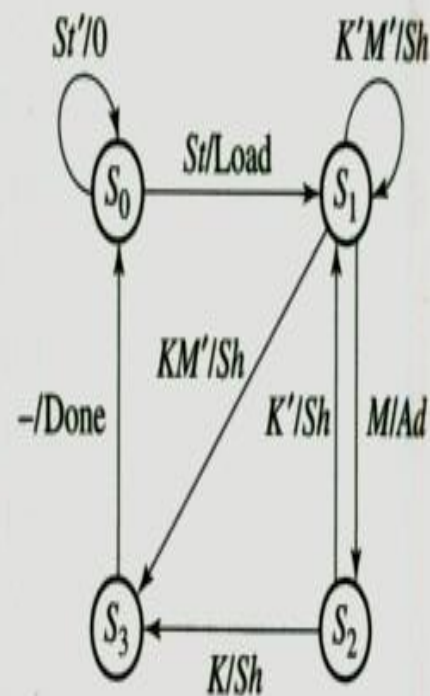

(c) Final state graph for add-shift control

# Division

- Division = subtraction and shift
- 8-bit dividend by a 4-bit divisor to get a 4-bit quotient
- Use a 9-bit dividend register for shifting the dividend left.
- Store quotient bit by bit into the dividend register when shifting left.


	divisor	1101		1010	quotient
				10000111	dividend
				1101	
				0111	
				0000	
				1111	
				1101	
				0101	
				0000	
				0101	remainder

(135 ÷ 13 = 10 with a remainder of 5)

# Binary Division


- Use a 9-bit dividend register for shifting the dividend left.
- Store quotient bit by bit into the dividend register when shifting left.

**FIGURE 18-10**  
Block Diagram for  
Parallel Binary  
Divider

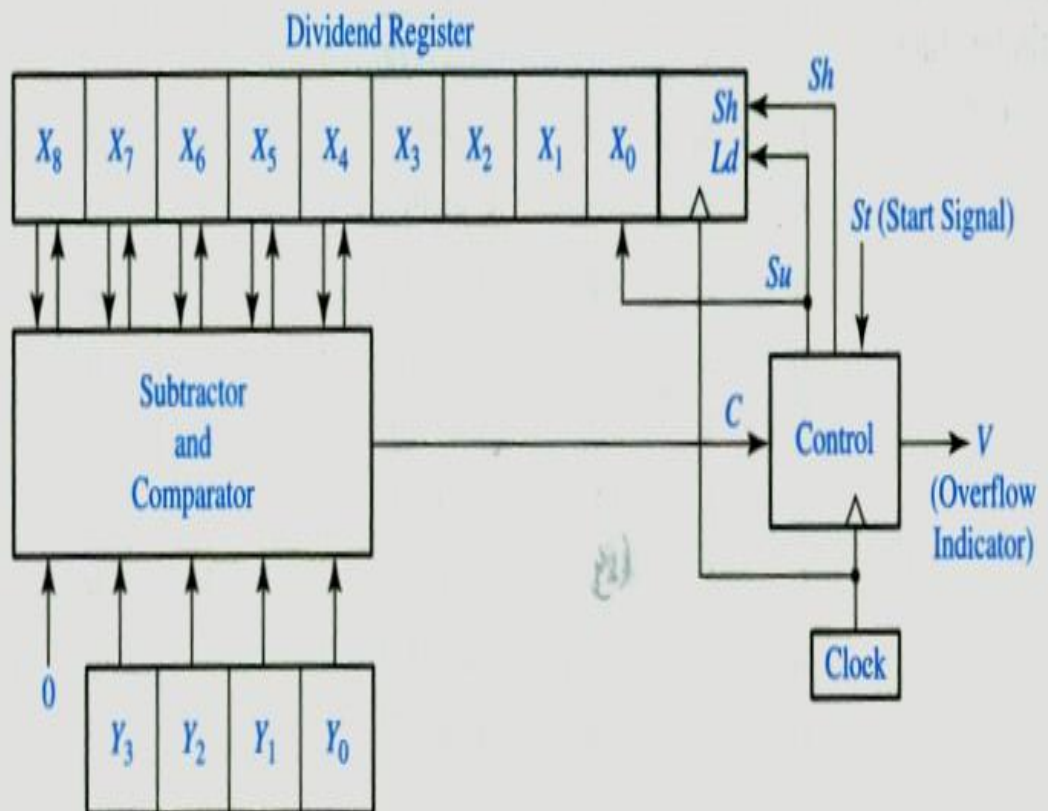

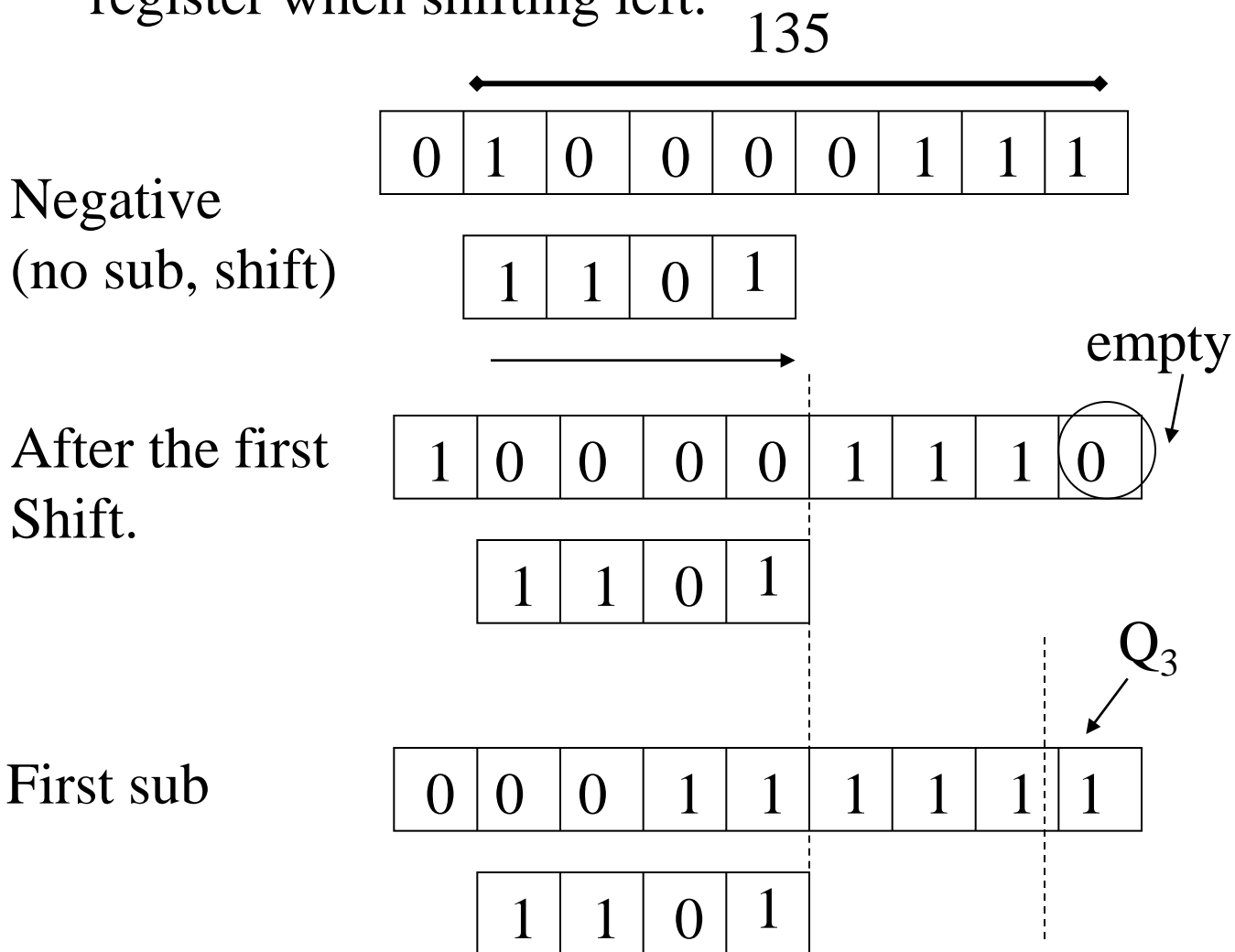
# Binary Division

- Use a 9-bit dividend register for shifting the dividend left.
- Store quotient bit by bit into the dividend register when shifting left.


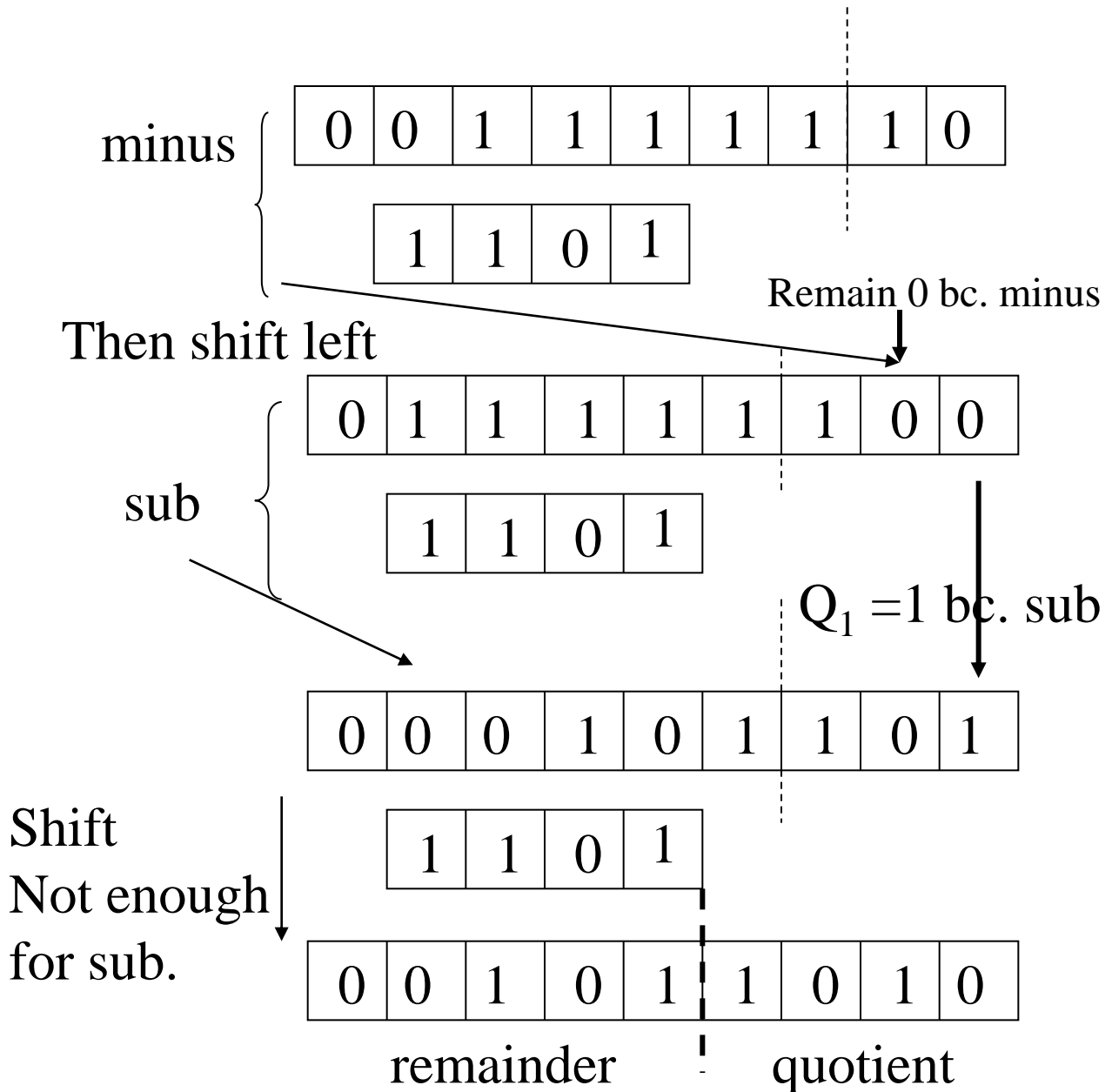
# Binary Division (cont.)

- Use a 9-bit dividend register for shifting the dividend left.




# Binary Division (cont.)

- In this example, if  $Q > 15$ , then overflow occurs.
- If initially  $X_8X_7X_6X_5X_4 \geq Y_3Y_2Y_1Y_0$ , then the quotient will be greater than 15 and overflow occurs.
- Shift signal: Sh
  - Shift the dividend one place to the left on the next rising clock edge.
- Subtract signal: Su
  - Use a subtracter to compute  $X_8X_7X_6X_5X_4 - Y_3Y_2Y_1Y_0$  (this is combinational circuit).
  - Su loads the subtracter output into  $X_8X_7X_6X_5X_4$  and sets the quotient bit to 1 on the next rising edge.
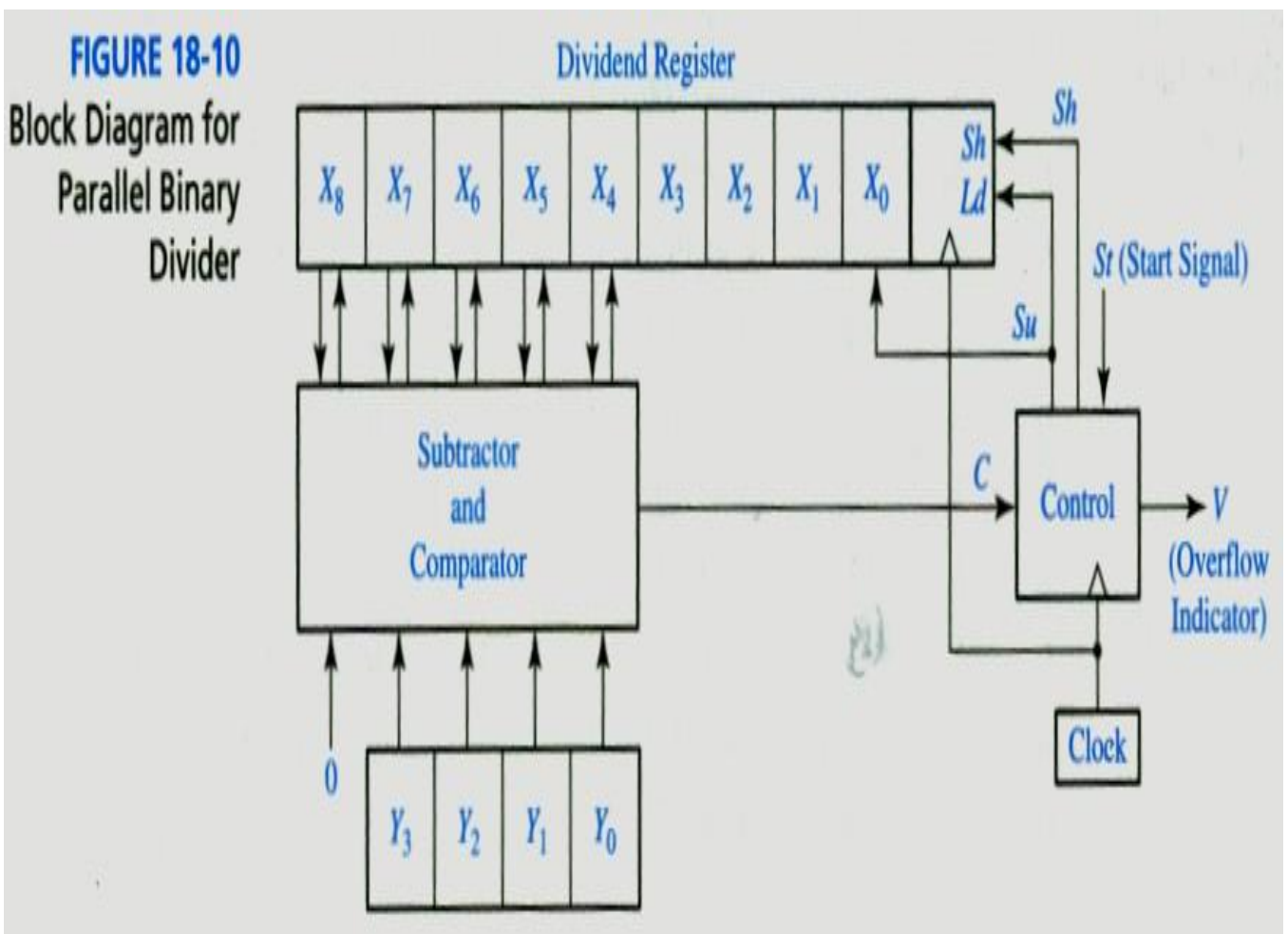
# Binary Division (cont.)


- Sh: shift the dividend register 1 bit left.
- Su: load  $X_8$  to  $X_4$  for the result of subtraction, (Ld). Set  $X_0$  to 1.





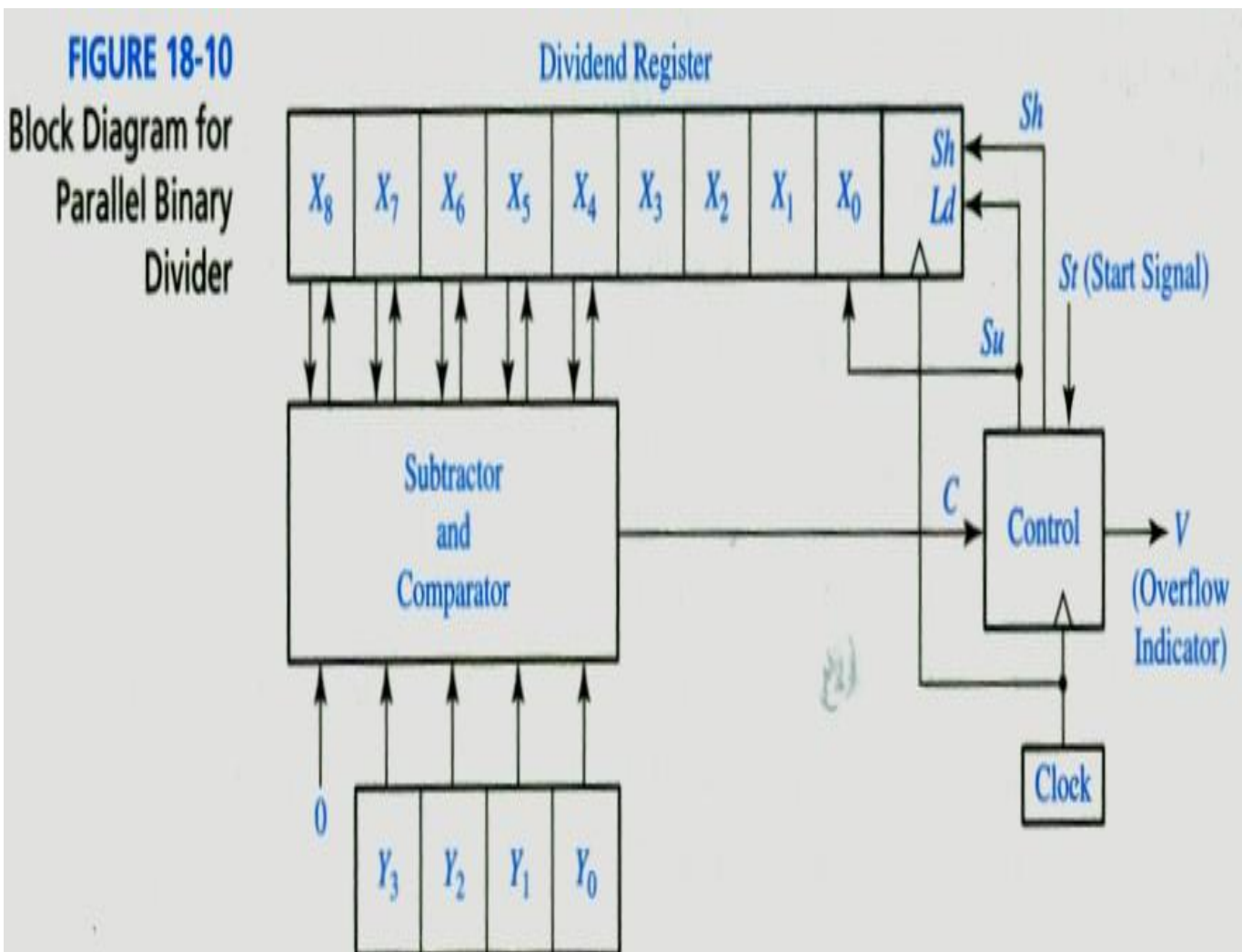
# Binary Division (cont.)

- $C$ : if divisor  $> X_8$  to  $X_4$ ,  $C=0$ . No subtraction, generate shift.  $Sh=1$ .
- Otherwise  $C = 1$ , subtract signal is generated ( $Su = 1$ ),  $Q$  bit is set to 1.



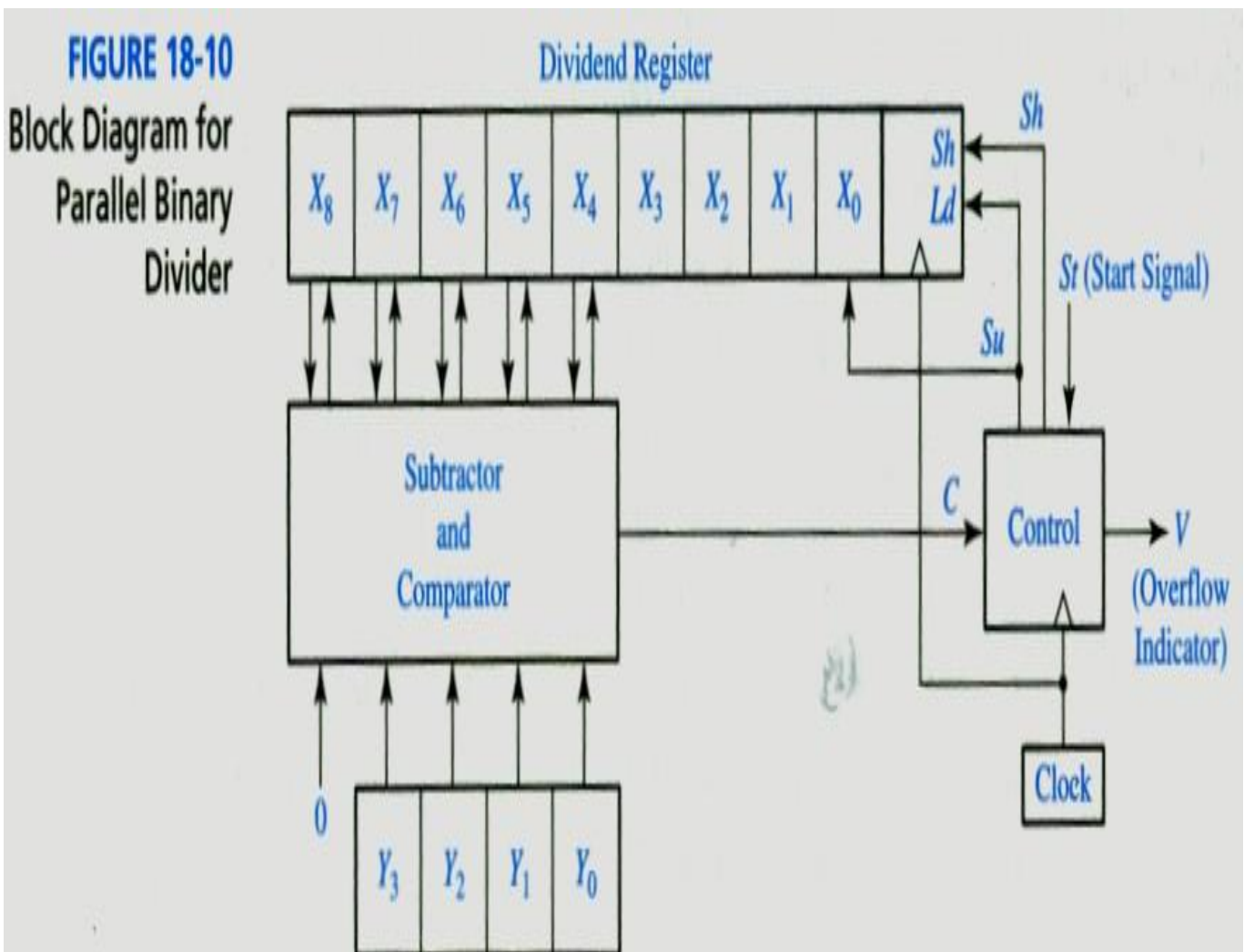
# Binary Division (cont.)

- $St$ : start signal.  $St = 1$ , load 8-bit dividend and 4-bit divisor into registers. If  $C = 1$  at this moment, this is overflow. Set  $V$  flag.


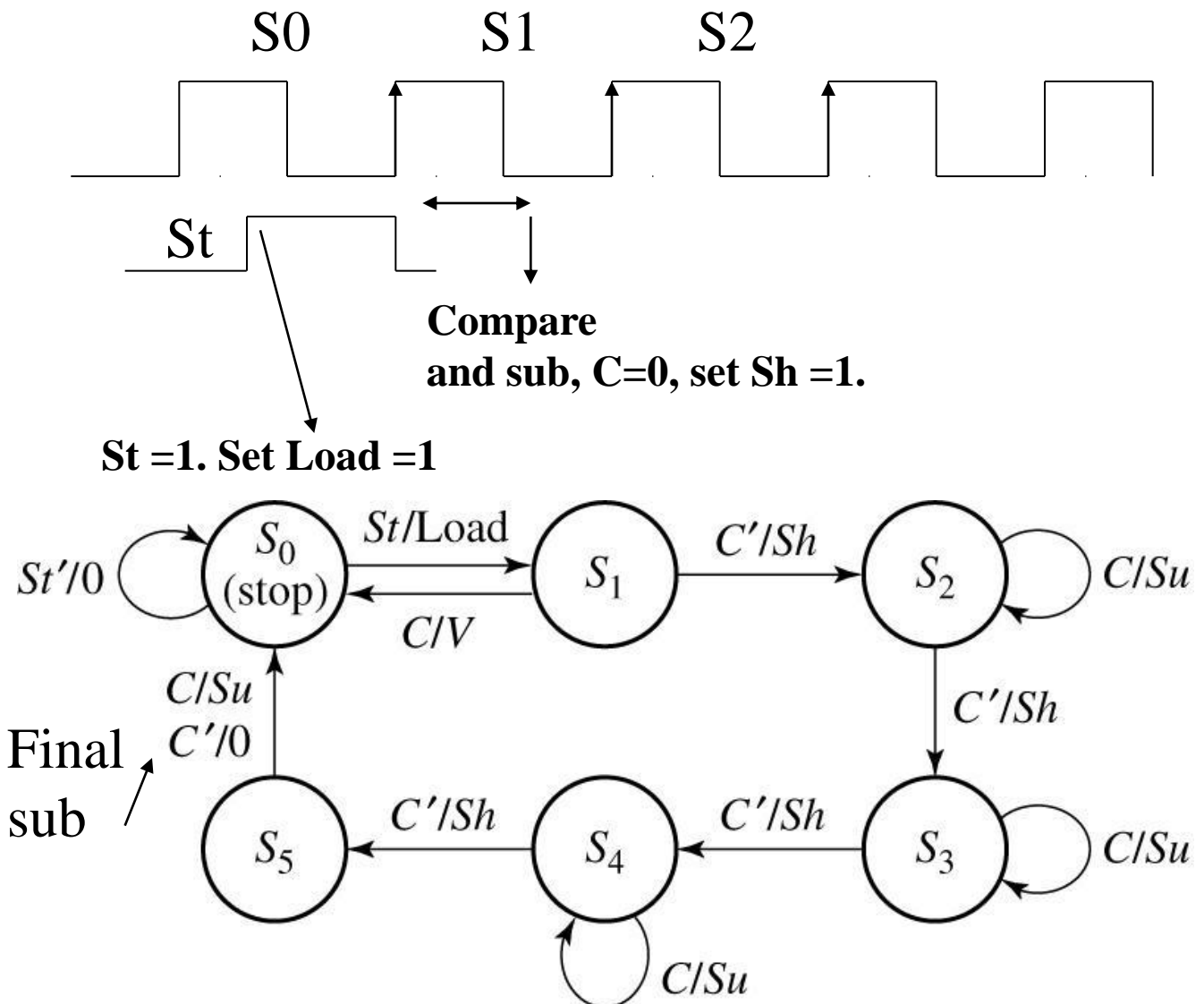
# Binary Division (cont.)

- $St$ : start signal.  $St = 1$ , load 8-bit dividend and 4-bit divisor into registers. If  $C = 1$  at this moment, this is overflow. Set  $V$  flag.
- Normally,  $C = 0$  at first.
- After  $C=1$  (do sub), then  $C$  will always be 0.



# Binary Division (cont.)

- One-hot assignment

$$Q_0^+ = St'Q_0 + CQ_1 + Q_5$$

$$Q_2^+ = C'Q_1 + CQ_2$$

$$Q_4^+ = C'Q_3 + CQ_4$$

$$Load = StQ_0$$

$$Sh = C'(Q_1 + Q_2 + Q_3 + Q_4) = C'(Q_0 + Q_5)'$$


$$Su = C(Q_2 + Q_3 + Q_4 + Q_5) = C(Q_0 + Q_1)'$$

$$Q_1^+ = StQ_0$$

$$Q_3^+ = C'Q_2 + CQ_3$$

$$Q_5^+ = C'Q_4$$

$$V = CQ_1$$

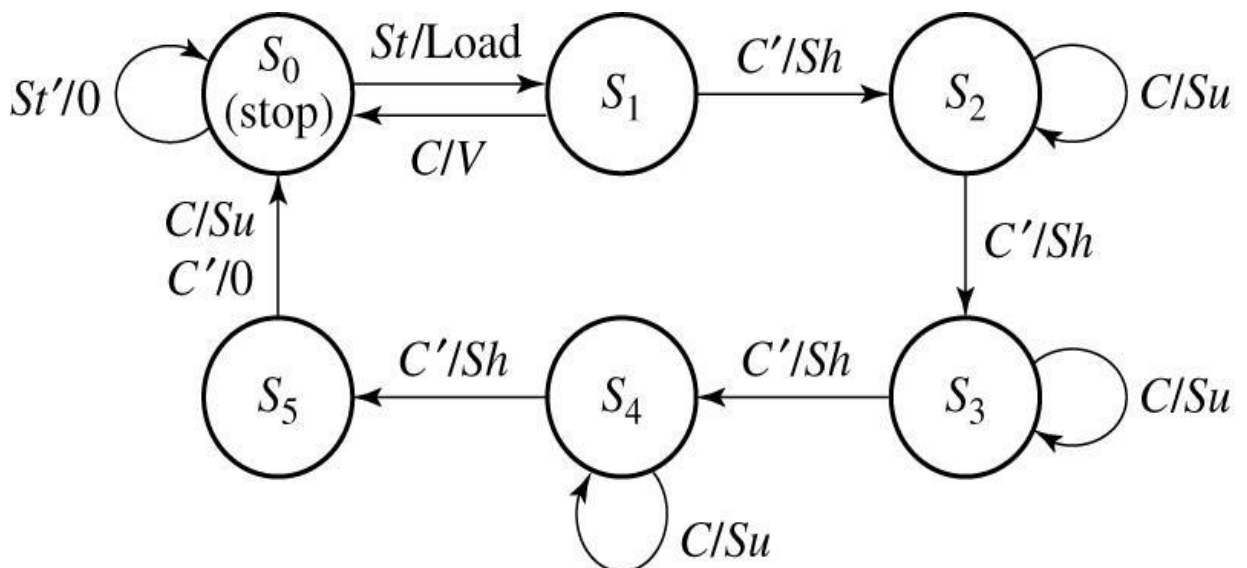

# Binary Division (cont.)

- Complete circuit

**FIGURE 18-13**  
Block Diagram for  
Divider Using Bus  
Notation

