


Lecture 2

Boolean Algebra Basic

- Algebra
 - An algebra A is a mathematics theory involving a set of elements S and a set of operations O that act on the members of S .
 - The smallest Boolean algebra contains two values, 0 and 1.
 - If X is a Boolean variable, then either $X = 0$ or $X = 1$.
 - 1 can mean high voltage or True while 0 might correspond to low voltage or False.

Basic Operations

- NOT (Complement, inversion)


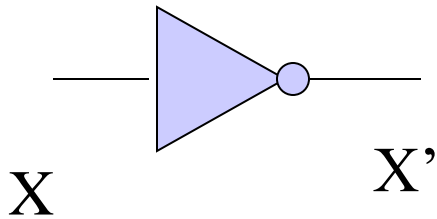


X	X'
0	1
1	0

Truth table

Basic Operations-cont.

- AND (Boolean multiplication)

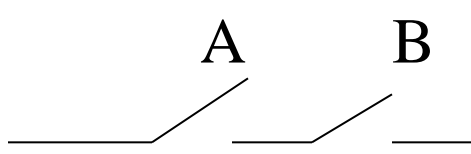
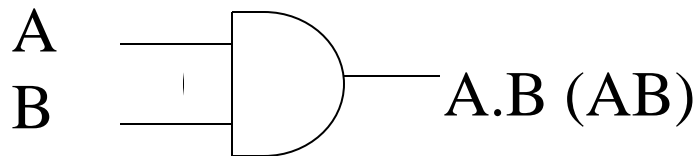


Open: 0
Close: 1

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

Basic Operations-cont.

- OR (Boolean addition, inclusive OR)

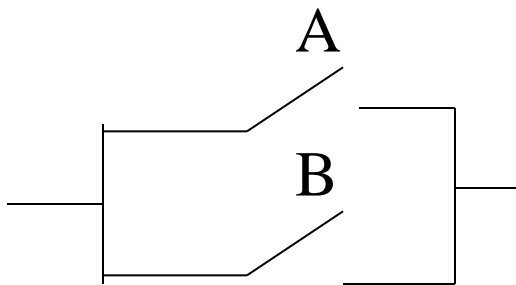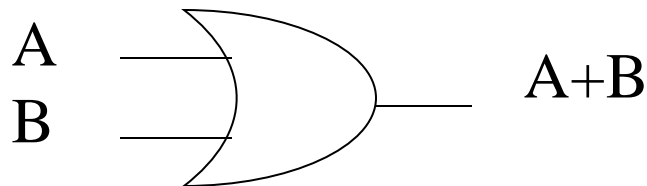

A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

Open: 0

Close: 1

Boolean Expressions

- Expressions
- Examples:


$$AB' + C \quad (1)$$

$$[A(C + D)]' + BC \quad (2)$$

- Each expression corresponds to a network of logic gates.
 - Exercise: Draw the logic gate network for (1) and (2).
- In (2), there are 4 variables and 5 literals.
- Operation order:
 - Parenthesis, NOT-> AND-> OR

Literals and Truth Table

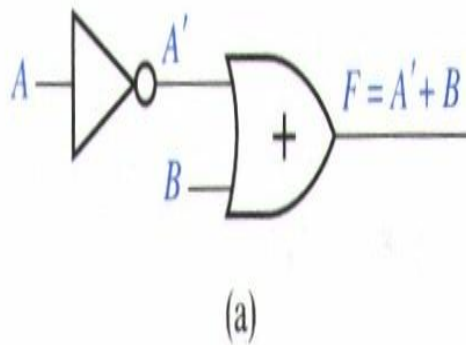- Literals
 - When an expression is realized using logic gates, each literal in the expression corresponds to a gate input.



A	B	A'	$F = A' + B$
0	0	1	1
0	1	1	1
1	0	0	0
1	1	0	1

(b)

2-input Network and Truth Table

Literals and Truth Table

- Truth table
 - Specify the values of the variables in the expression.
 - n variables have 2^n different combinations of values of the variables.

A	B	C	B'	AB'	$AB' + C$	$A + C$	$B' + C$	$(A + C)(B' + C)$
0	0	0	1	0	0	0	1	0
0	0	1	1	0	1	1	1	1
0	1	0	0	0	0	0	0	0
0	1	1	0	0	1	1	1	1
1	0	0	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1
1	1	0	0	0	0	1	0	0
1	1	1	0	0	1	1	1	1

Basic Theorems

- Operation with 0 and 1

$$X + 0 = X$$

$$X + 1 = 1$$

$$X \cdot 1 = X$$

$$X \cdot 0 = 0$$

- Idempotent laws

$$X + X = X$$

$$X \cdot X = X$$

- Involution law

$$(X')' = X$$

- Laws of complementarity

$$X + X' = 1$$

$$X \cdot X' = 0$$

Basic Theorems-cont.

- Commutative laws

$$X + Y = Y + X$$

$$XY = YX$$

- Associative laws

$$(X+Y) + Z = X + (Y + Z) = X + Y + Z$$

$$(XY)Z = X(YZ) = XYZ$$

- Distributive laws

$$X(Y + Z) = XY + XZ$$

$$X + YZ = (X+Y)(X+Z)$$

Basic Theorems-cont.

- Simplification theorems

$$XY + XY' = X$$

$$\checkmark (X+Y)(X+Y') = X$$


$$X + XY = X$$

$$\checkmark X(X+Y) = X$$

$$(X+Y')Y = XY$$

$$\checkmark XY' + Y = X + Y$$

Example: Simplification

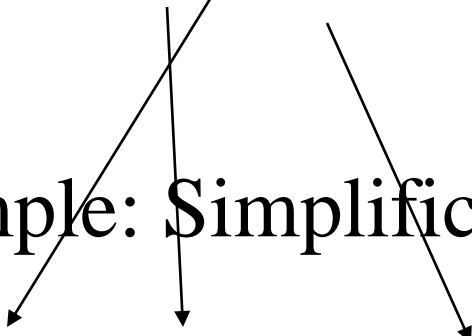
$$Z = (AB+C)(B'D+C'E') + (AB+C)' = (AB+C)' + B'D+C'E'$$

Basic Theorems-cont.

- Theorem for multiplying out and factoring
 - Use distributive law.

$$\checkmark (X+Y)(X+Z) = X + YZ$$



Example: $(A+BC)(A+D+E)$

$$= A + BC(D+E) = A + BCD + BCE.$$

Proof of Theorem or Law

- Using truth table
 - Associative law
 - $(A+B) + C = A + B + C$
 - What is the difference?
 - # of fan-in
 - Potential speedup
- Using algebra manipulation
 - $A + A = A$
- Using Principal of Duality
 - ✓ Principal of duality: Any theorem or identity in switching algebra remains true if 0 and 1 are swapped and, \cdot and $+$ are swapped.
 - ✓ Example: If $X + XY = X \cdot 1$, then $X \cdot (X+Y) = X + 0 = X$

Some Properties

- In Boolean algebra, AND (OR) operation distributes over OR(AND).

$$\checkmark X(Y+Z) = XY + XZ$$

$$\checkmark A+BC = (A+B)(A+C)$$

- Application of simplification

Example: $(A + B'C + D + EF)(A+B'C+ (D+EF)')$;

□ View $A+B'C = X$, $D + EF = Y$;
so this is $(X+Y)(X+Y') = X$

SOP

- An expression is said to be in **sum of products** form when all products are products of single variables only. Use frequently.

- Example

$$A'B + CD'E + AC'E' \quad \text{Yes.}$$

$$(A+B)CD + EF \quad \text{No.}$$

$$ACD + BCD + EF \quad \text{Yes.}$$

- Use Multiplying out to get SOP

$$(A+BC)(A+D+E) =$$

$$A + BC(D+E) = A + BCD + DCE.$$

- Using $(X+Y)(X+Z) = X + YZ$

POS

- An expression is said to be in **product of sums** form when all sums are sums of a single variable. Not use as often as SOP form in industry.

- Example

$$(A+B')(C+D'+E) \quad \text{Yes.}$$

$$(A+B')(C+D'+E)F \quad \text{Yes.}$$

$$(A+B)(C+D) + EF \quad \text{No.}$$

- Use Factoring to get POS

$$A + B'CD = (A + B')(A + CD);$$

first factoring.

$$= (A+B')(A+C)(A+D);$$

second factoring.