

Lecture 5

Karnaugh Maps

- Algebraic procedures:
 - Difficult to apply in a systematic way.
 - Difficult to tell when you have arrived at a minimum solution.
- Karnaugh map (K-map) can be used to minimize functions of up to 6 variables.
 - K-map is directly applied to two-level networks composed of AND and OR gates.
 - Sum-of-products, (SOP)
 - Product-of-sum, (POS).

Minimum SOP

- It has a minimum no. of terms.
 - That is, it has a minimum number of gates.
- It has a minimum no. of gate inputs.
 - That is, minimum no. of literals.
 - Each term in the minimum SOP is a prime implicant, i.e., it cannot be combined with others.
- It may not be unique.
 - Depend on the order in which terms are combined or eliminated.

Minimum SOP

- Example: vertical input scheme

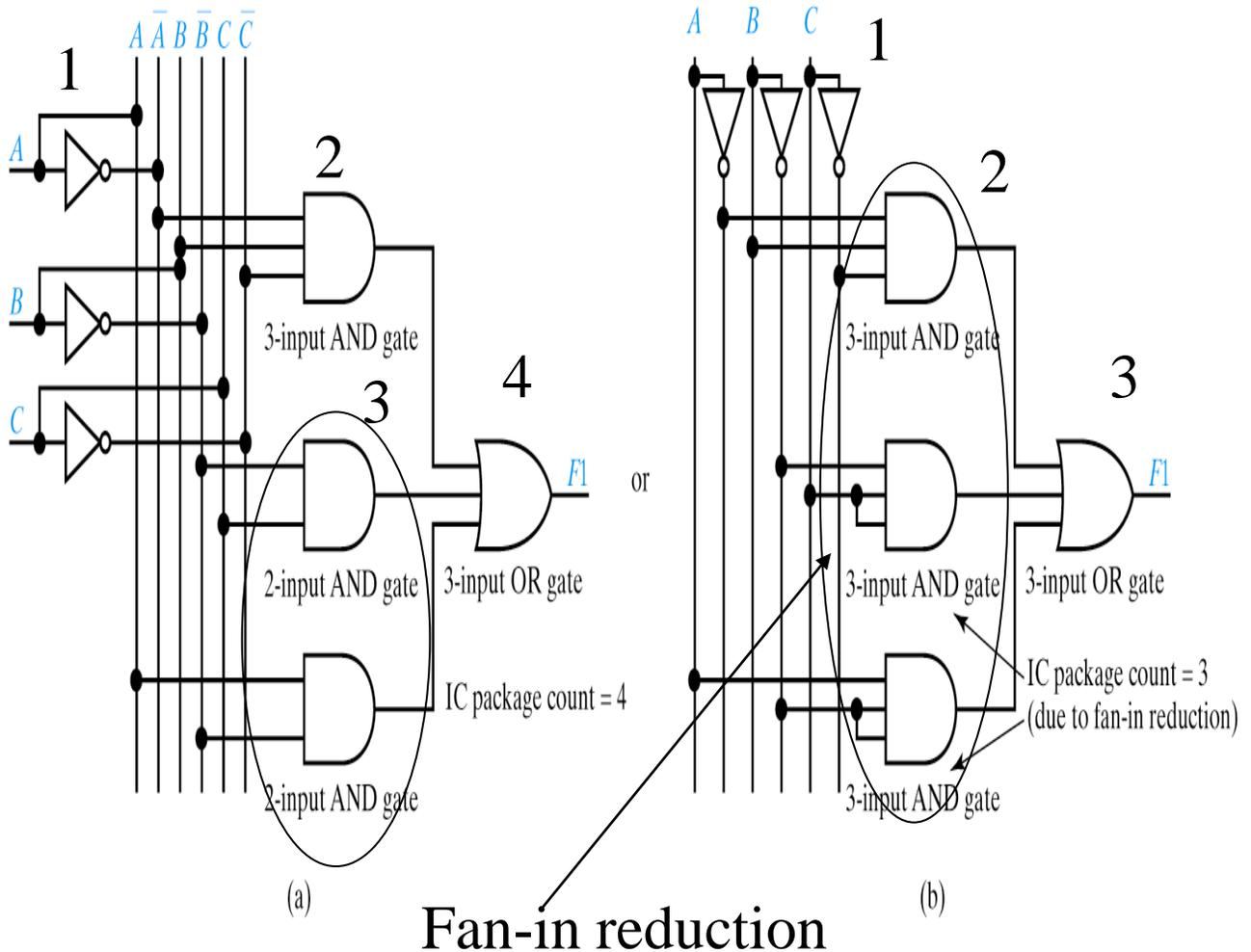


Figure 3.2.5 IC logic circuit designs for a minimum SOP form of a function using a vertical input scheme: (a) without fan-in reduction, (b) with fan-in reduction.

Minimum POS

- It has a minimum no. factors.
- It has a minimum no. of literals.
- It may not be unique.
 - Use $(X+Y) (X+Y')$ = X
 - Use $(X +C) (X' + D)(C+D) = (X+C)(X'+D)$ to eliminate term.

Minimum POS

- Example: Vertical input scheme


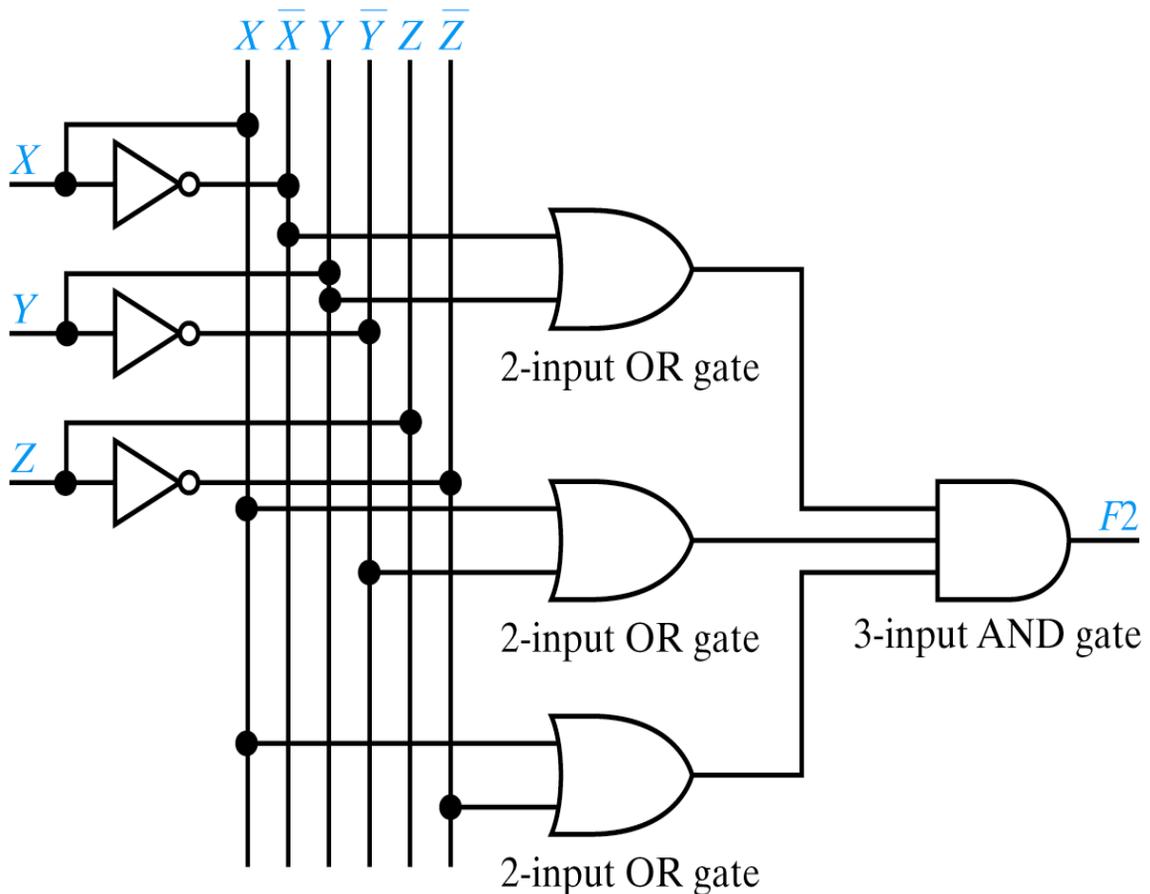


Figure 3.2.7 IC logic circuit design for a minimum POS form of a function using a vertical input scheme.


2-Variable K-map

- Place 1s and 0s from the truth table in the K-map.
- Each square of 1s = minterms.
- Minterms in adjacent squares can be combined since they differ in only one variable. Use $XY' + XY = X$.

A	B	F
0	0	1
0	1	1
1	0	0
1	1	0

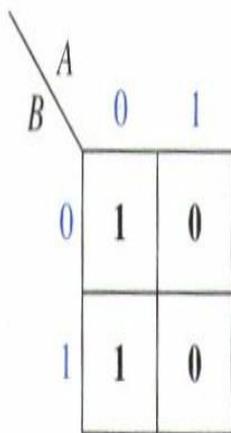


(a)

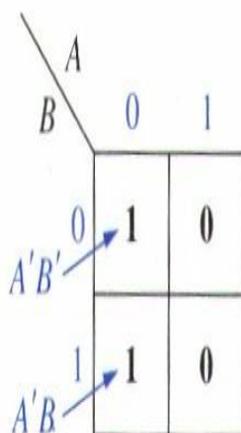

$$F = A'B' + A'B$$

(c)

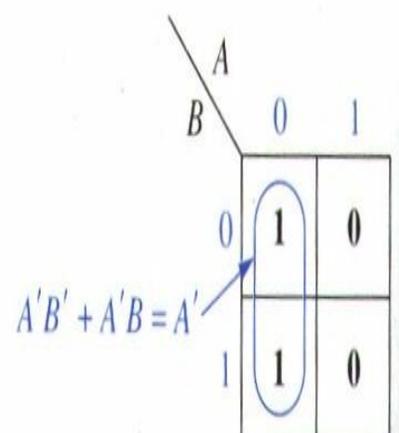

$$F = A'$$


(d)

3-Variable K-map

- Note BC is listed in the order of 00, 01, 11, 10. (Gray code)
- Minterms in adjacent squares that differ in only one variable can be combined using $XY' + XY = X$.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

(a)

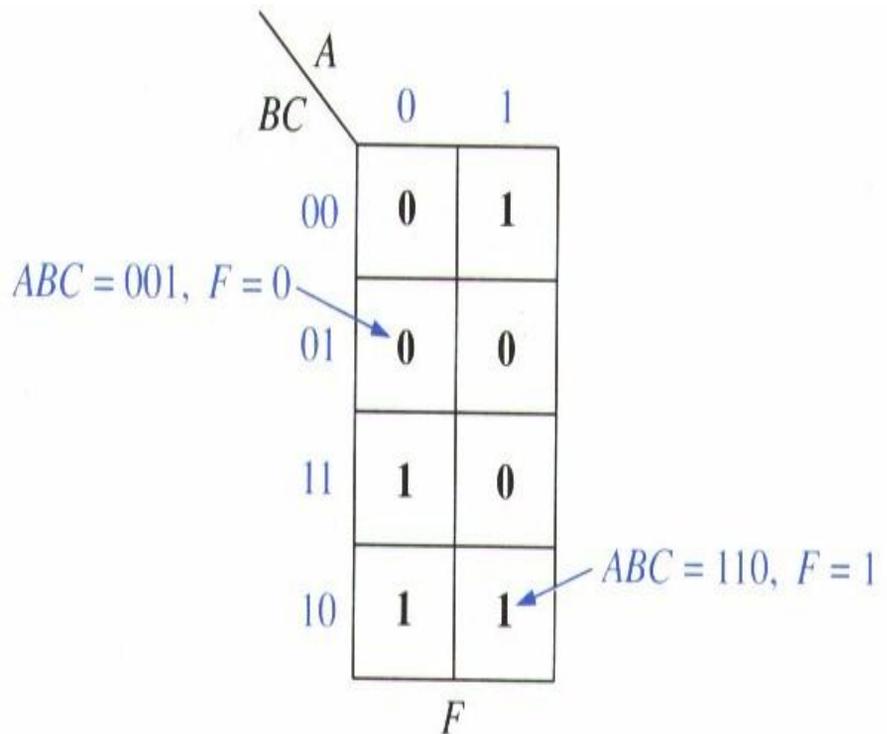

(b)

Location of Minterms

- Adjacent terms in 3-variable K map.

A 3-variable Karnaugh map in binary notation. The vertical axis is labeled 'a' with values 00, 01, 11, 10. The horizontal axis is labeled 'bc' with values 0 and 1. The cells contain the following binary values:

a \ bc	0	1
00	000	100
01	001	101
11	011	111
10	010	110

Blue arrows indicate adjacencies: a vertical arrow between 001 and 011, a horizontal arrow between 011 and 111, a vertical arrow between 011 and 010, and a blue line connecting 100 and 110. A text label states: "100 is adjacent to 110".

(a) Binary notation

A 3-variable Karnaugh map in decimal notation. The vertical axis is labeled 'a' with values 00, 01, 11, 10. The horizontal axis is labeled 'bc' with values 0 and 1. The cells contain the following decimal values:

a \ bc	0	1
00	0	4
01	1	5
11	3	7
10	2	6

(b) Decimal notation

K Map Example

- K-map of $F(a,b,c) = \sum m(1,3,5)$
 $= \prod M(0,2,4,6,7)$

A Karnaugh Map for a three-variable function F(a,b,c). The map is a 4x2 grid. The vertical axis is labeled 'a' and has values 00, 01, 11, 10. The horizontal axis is labeled 'bc' and has values 0 and 1. The cells contain the following values: (00,0)=0, (00,1)=0, (01,0)=1, (01,1)=1, (11,0)=1, (11,1)=0, (10,0)=0, (10,1)=0. Small numbers 0, 1, 2, 3, 4, 5, 6, 7 are placed in the bottom-right corner of each cell to indicate the minterm index.


a \ bc	0	1
00	0 0	0 4
01	1 1	1 5
11	1 3	0 7
10	0 2	0 6

Karnaugh Map of

$$F(a, b, c) = \sum m(1, 3, 5) = \prod M(0, 2, 4, 6, 7)$$

Place Product Terms on K Map

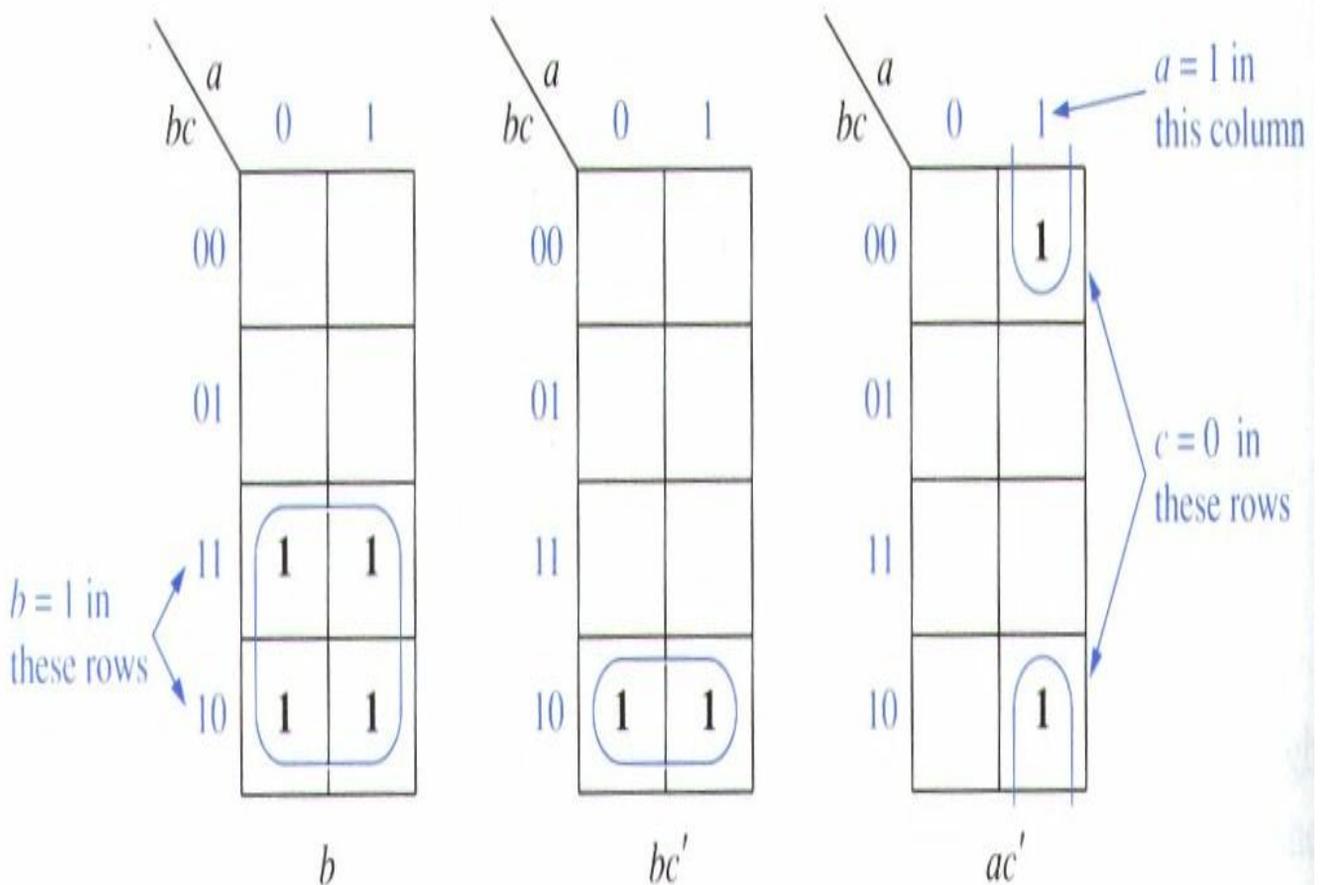- Example
 - Place b , bc' and ac' in the 3-variable K map.




More Example

- Exercise. Plot $f(a, b, c) = abc' + b'c + a'$ into the K-map.

$$f(a, b, c) = abc' + b'c + a'$$

we would plot the map as follows:

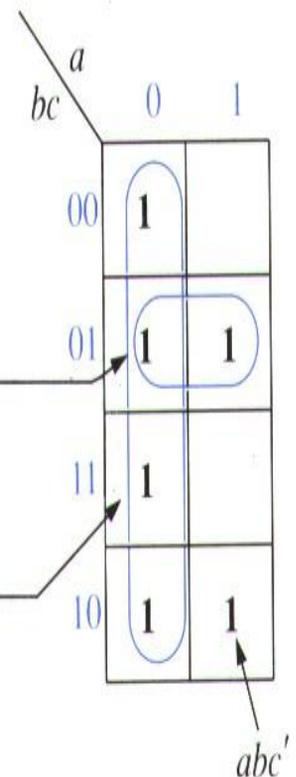1. The term abc' is 1 when $a = 1$ and $bc = 10$, so we place a 1 in the square which corresponds to the $a = 1$ column and the $bc = 10$ row of the map.
 2. The term $b'c$ is 1 when $bc = 01$, so we place 1's in both squares of the $bc = 01$ row of the map.
 3. The term a' is 1 when $a = 0$, so we place 1's in all the squares of the $a = 0$ column of the map.
- (Note: since there already is a 1 in the $abc = 001$ square, we do not have to place a second 1 there because $x + x = x$.)



Simplification Example

- Exercise. Simplify: $F(a,b,c) = \sum m(1,3,5)$
 - Procedure: place minterms into map.
 - Select adjacent 1's in group of two 1's or four 1's etc.
 - Kick off x and x' .

	<i>a</i>	0	1
<i>bc</i>			
00			
01		1	1
11		1	
10			

$$F = \sum m(1, 3, 5)$$

(a) Plot of minterms

	<i>a</i>	0	1
<i>bc</i>			
00			
01		1	1
11		1	
10			

$$T_1 = a'b'c + a'bc = a'c$$


$$T_2 = a'b'c + ab'c = b'c$$

$$F = a'c + b'c$$

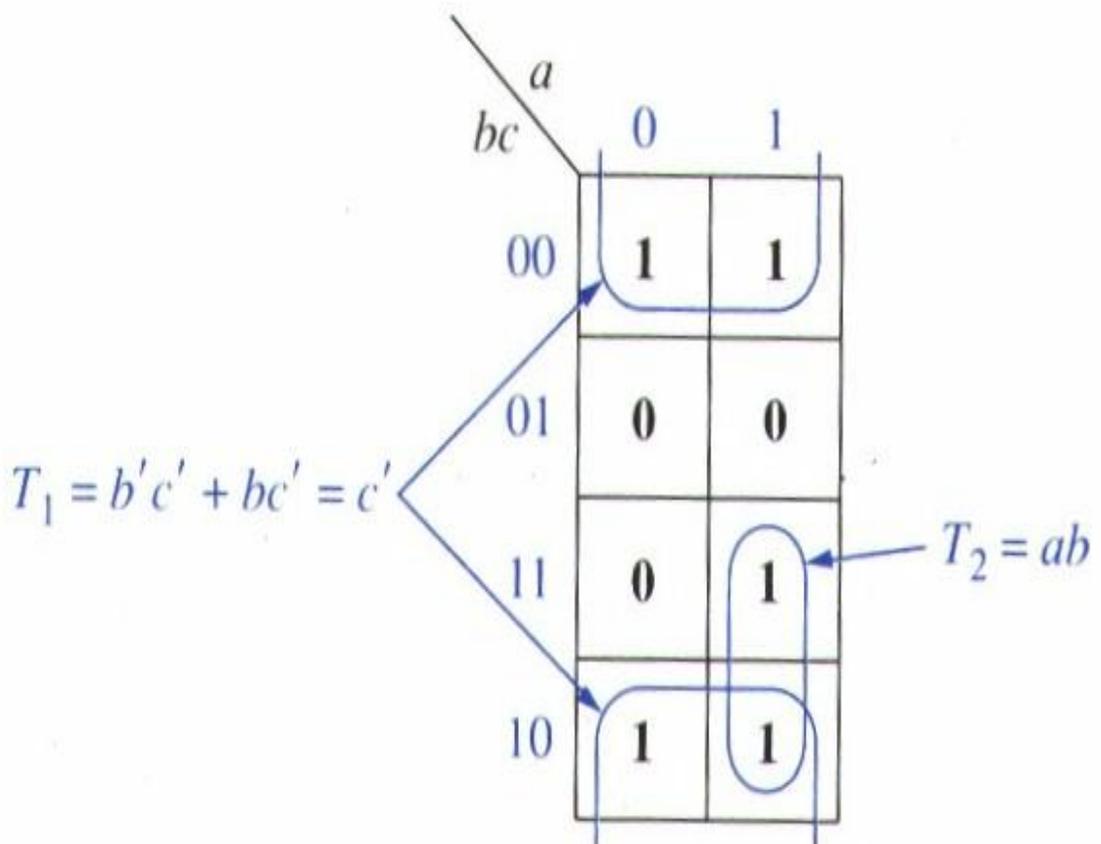(b) Simplified form of F


More Example

- The complement of F
 - Using four 1's to eliminate two variables.




Redundant Terms

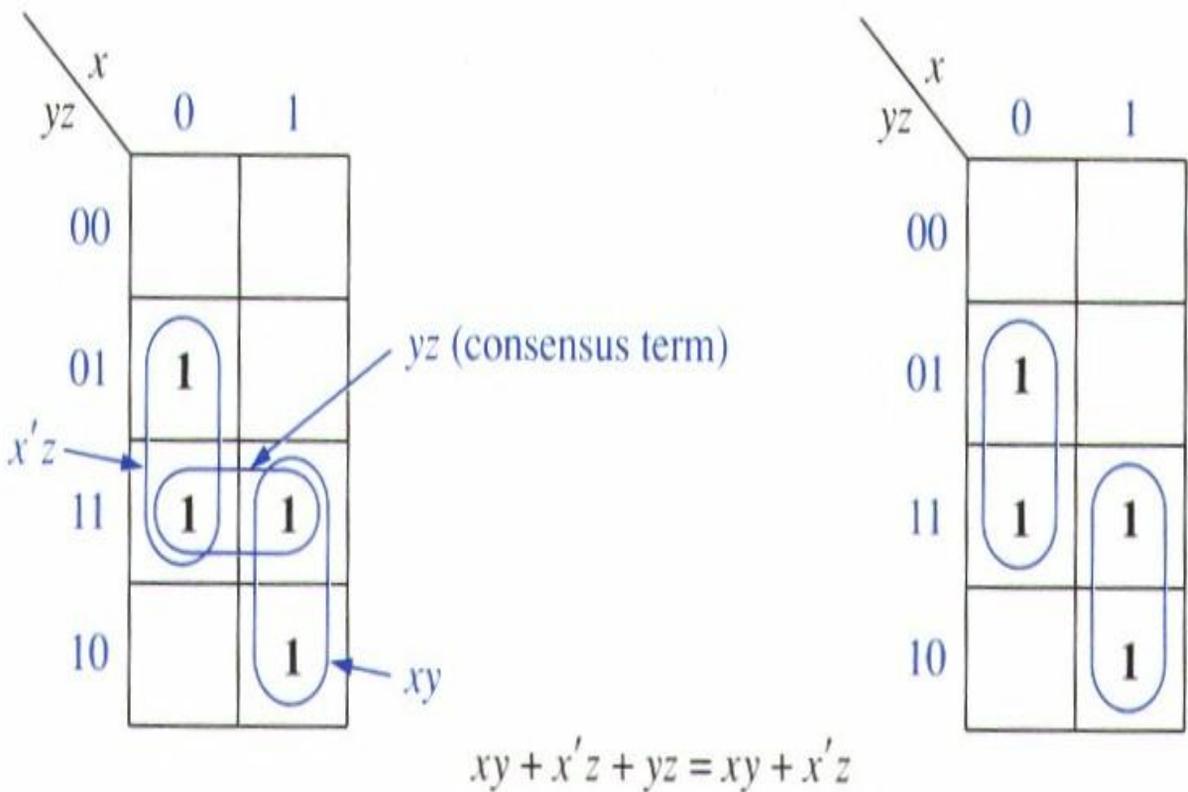- If a term is covered by two other terms, that term is redundant. That is, it is a consensus term.
- Example: yz is the redundant.




More Than Two Minimum Solutions

- $F = \sum m(0,1,2,5,6,7)$

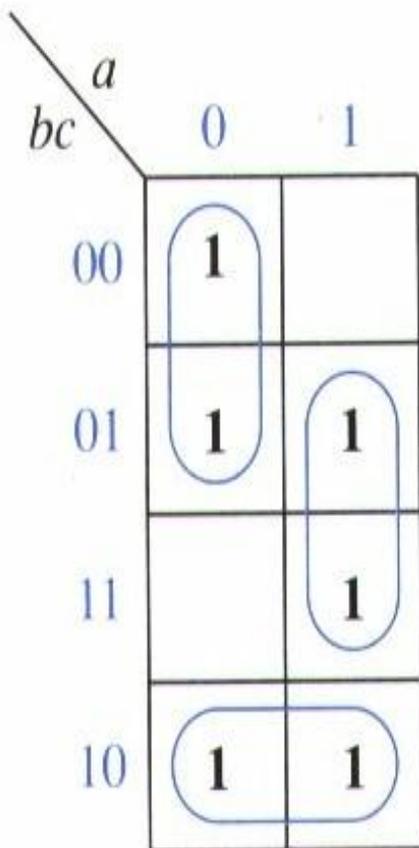

$$F = a'b' + bc' + ac$$

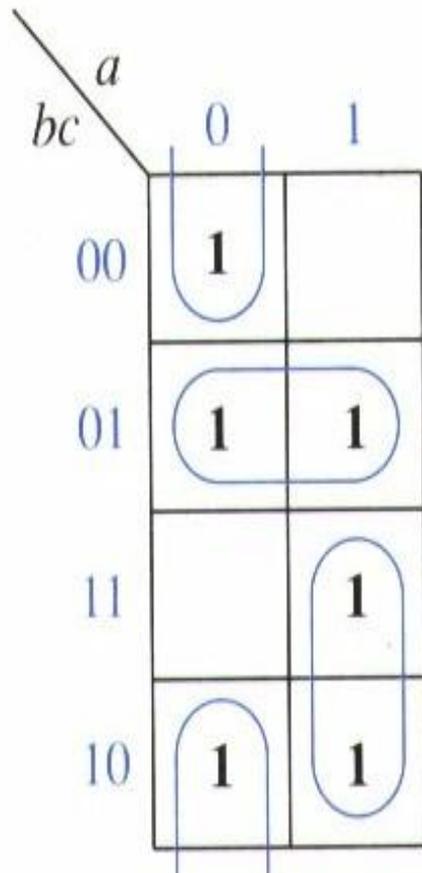

$$F = a'c' + b'c + ab$$


4-Variable K Map

- Each minterm is adjacent to 4 terms with which it can combine.
 - 0, 8 are adjacent squares
 - 0, 2 are adjacent squares, etc.
 - 1, 4, 13, 7 are adjacent to 5.

<i>CD</i> \ <i>AB</i>	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10


Plot a 4-variable Expression

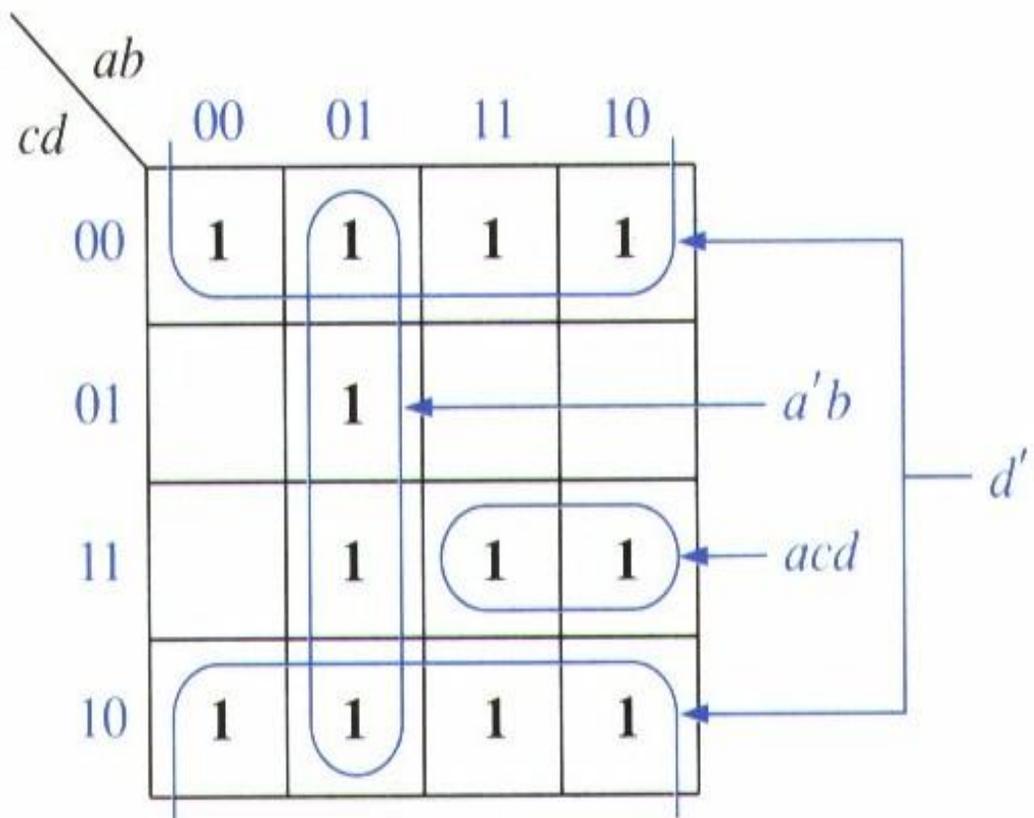- $F(a,b,c,d) = acd + a'b + d'$
 $acd = 1$ if $a=1, c=1, d=1$



Simplification Example

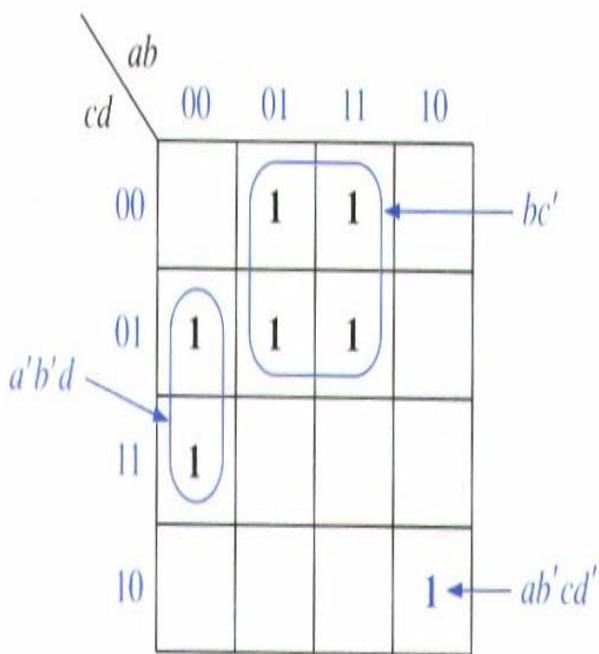
- Minterms are combined in groups of 2, 4, or 8 to eliminate 1, 2, 3 variables.
- Corner terms.



$$f_1 = \sum m(1, 3, 4, 5, 10, 12, 13)$$

$$= bc' + a'b'd + ab'cd'$$

(a)

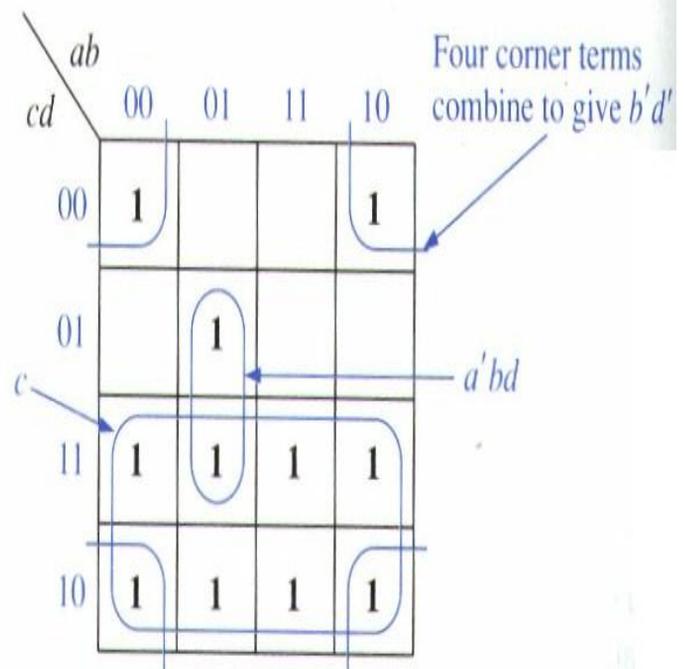

$$f_2 = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15)$$

$$= c + b'd' + a'bd$$

(b)

Simplification with Don't Care

- Don't care “x” is covered if it helps. Otherwise leave it along.

<i>cd</i> \ <i>ab</i>	00	01	11	10
00			x	
01	1	1	x	1
11	1	1		
10		x		

$$f = \Sigma m(1, 3, 5, 7, 9) + \Sigma d(6, 12, 13)$$
$$= a'd + c'd$$

Get a Minimum POS Using K Map

- Cover 0's to get simplified POS.
 - We want 0 in each term.

$$f = x'z' + wyz + w'y'z' + x'y$$

First, the 1's of f are plotted in Fig. 5-14. Then, from the 0's,

$$f' = y'z + wxz' + w'xy$$

and the minimum product of sums for f is

$$f = (y + z')(w' + x' + z)(w + x' + y')$$


		wx			
		00	01	11	10
yz	00	1	1	0	1
	01	0	0	0	0
	11	1	0	1	1
	10	1	0	0	1

Determination of Minimum Expressions Using Essential Prime Implicants

- Definitions:
 - **Implicants:** An implicant of a function F is a single element of the on set (1) or any group of elements that can be combined together in a K-map.
 - **Prime Implicants:** An implicant that cannot be combined with another to eliminate a literal.
 - **Essential Prime Implicants:** If a particular element of the on-set is covered by a single prime implicant. That implicant is called an essential prime implicant.
- All essential primes must be part of the minimized expression.


Implicant of F

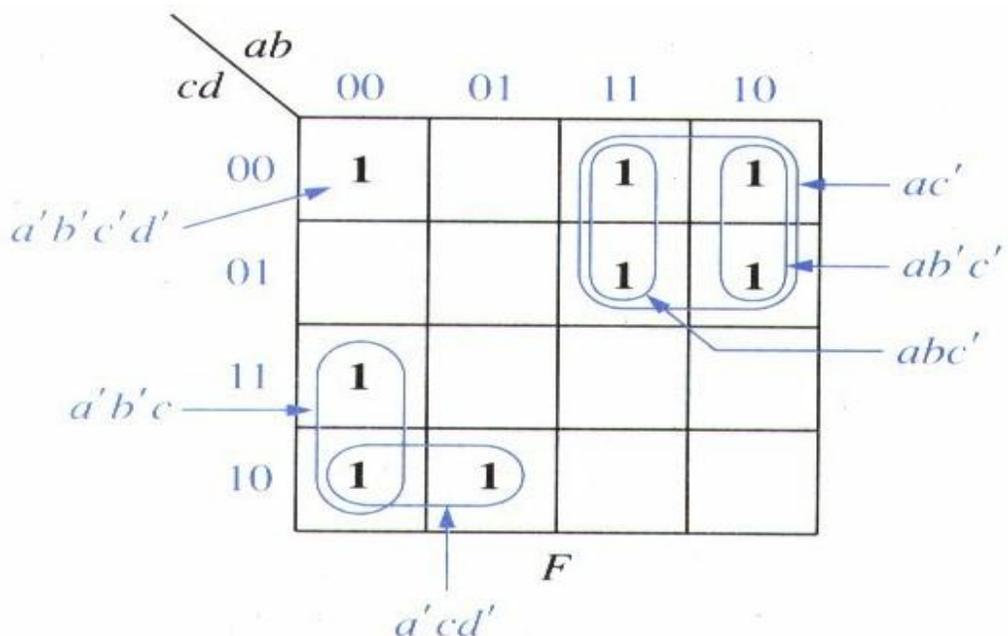- Implicant
 - Any single 1 or any group of 1's
- Prime implicant
 - An implicant that can not be combined with another term to eliminate a variable.
 - $a'b'c$, $a'cd'$, ac' are prime implicant.
 - $a'b'c'd'$ is not (combined with $a'b'cd'$).
 - abc' and $ab'c'$ are not.




Prime Implicant

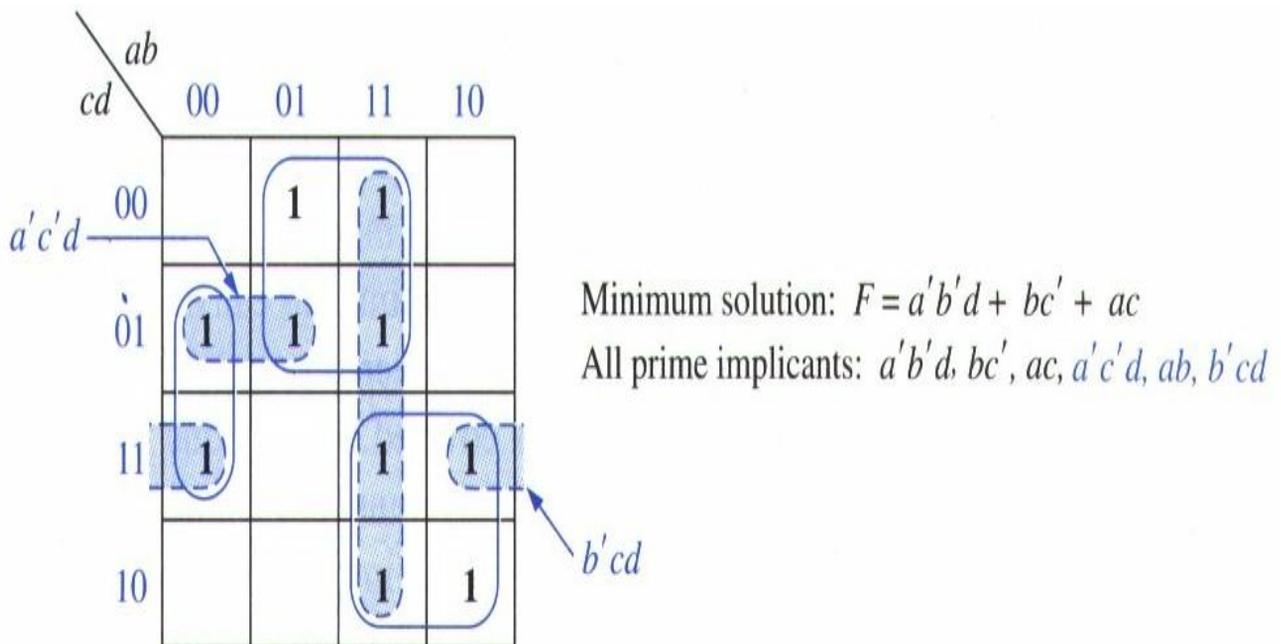- A single 1 which is not adjacent to any other 1's.
- Two adjacent 1's which are not contained in a group of four 1's. And so on.
 - Shaded loops are also prime implicants, but not part of the minimum solution.
 - $a'c'd$ and $b'cd$ are already covered by other group. So we do not need them.




Essential Prime Implicants for Minimum SOP

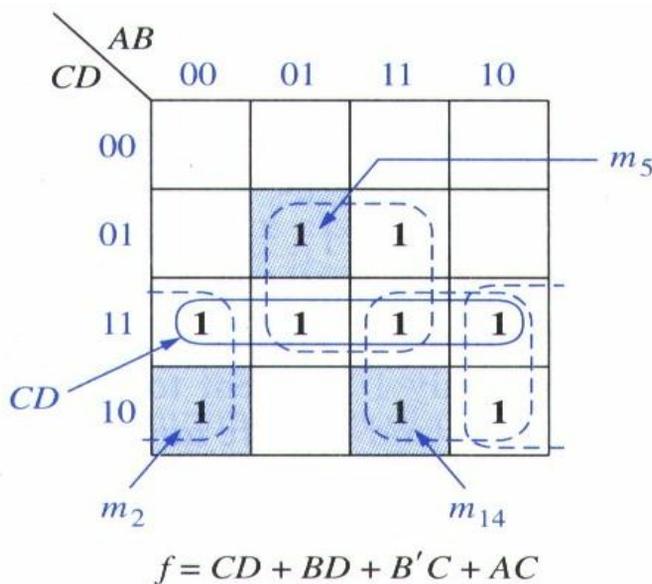- If CD is chosen first, then f has 4 terms. We don't need CD since it is covered by other group. CD is not a essential prime implicant.
- m2 is essential prime implicant since it is covered only by one prime implicant. So does m5, and m14. We need them in the answer.




(a)

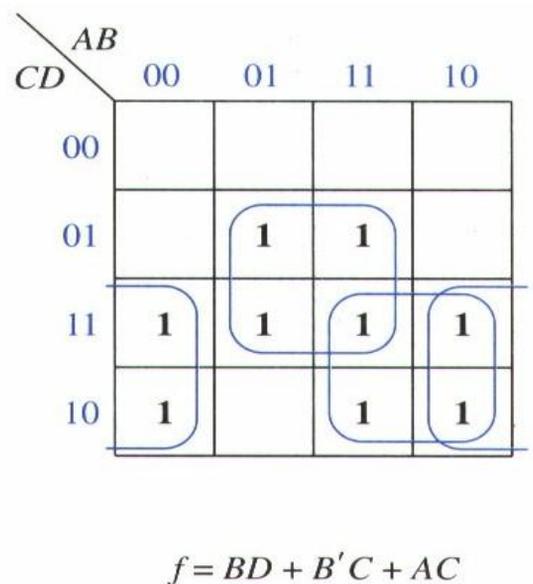


(b)

Rule of Thumb

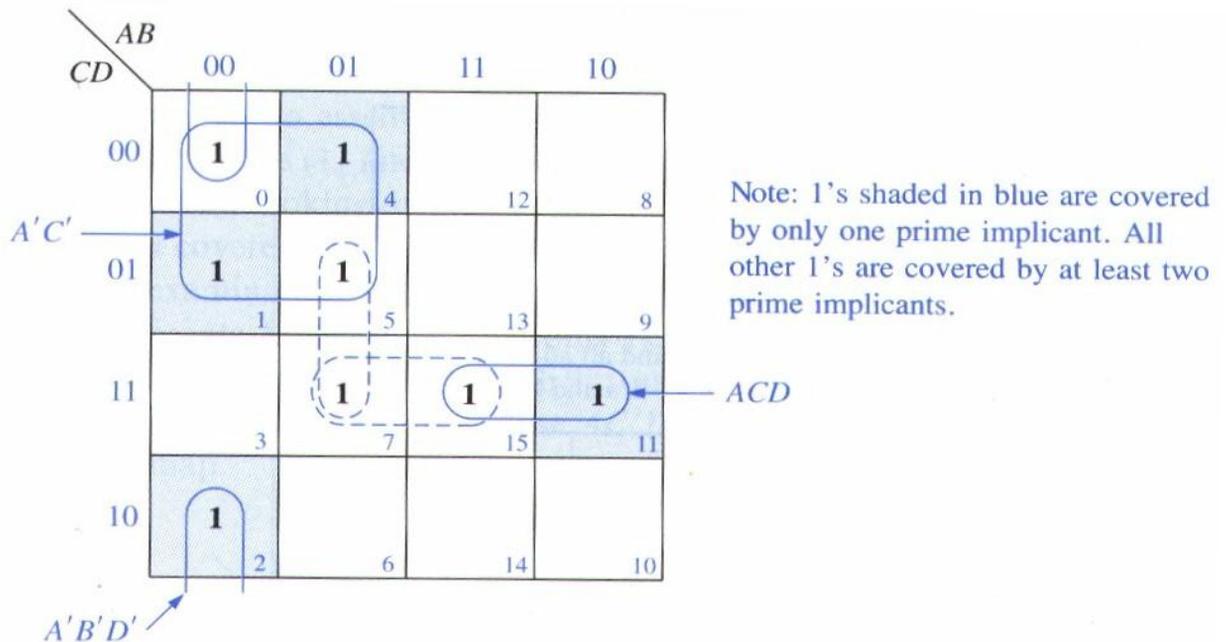- Look at all squares adjacent to a minterm.
 - If the given minterm and all of the 1's adjacent to it are covered by a single term, then that term is an essential prime implicant
 - But if it is covered by more than two prime implicant, we can not tell whether this term is essential or not.
 - The solution is $A'C' + A'B'D' + ACD + (A'BD \text{ or } BCD)$.



Flow Chart

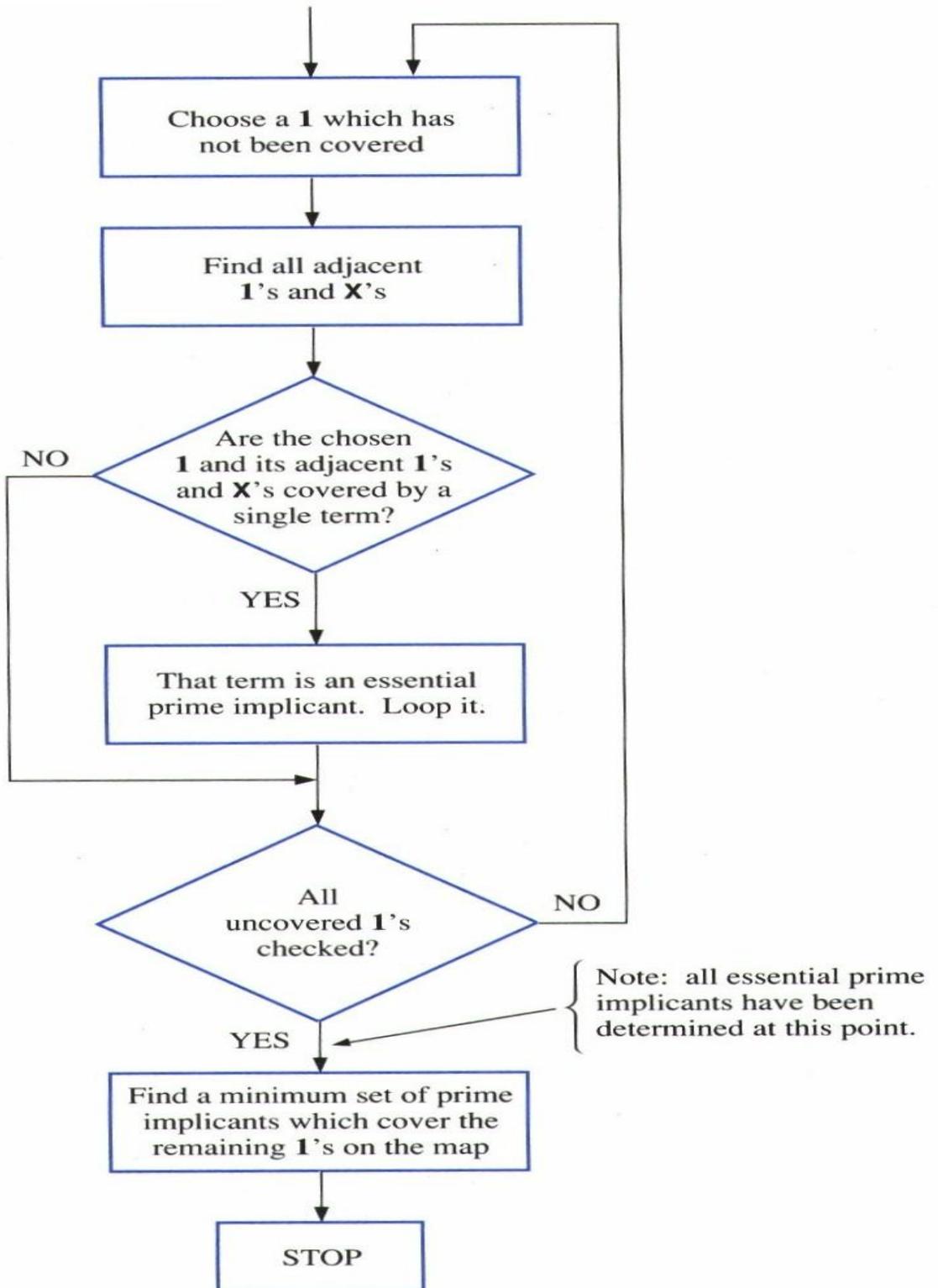

Example

- Find the 1 that is covered by only one term first (Do not share with other circle).

$CD \backslash AB$	00	01	11	10
00	x_0	1 ₄		1 ₈
01		1 ₅	1 ₁₃	1 ₉
11		x_7	x_{15}	
10		1 ₆		1 ₁₀


Shaded 1's are covered by only one prime implicant

5-Variable K Map

– Use two 4-variable map to form a 5-variable K map ($16 + 16 = 32$)


(A,B,C,D,E)

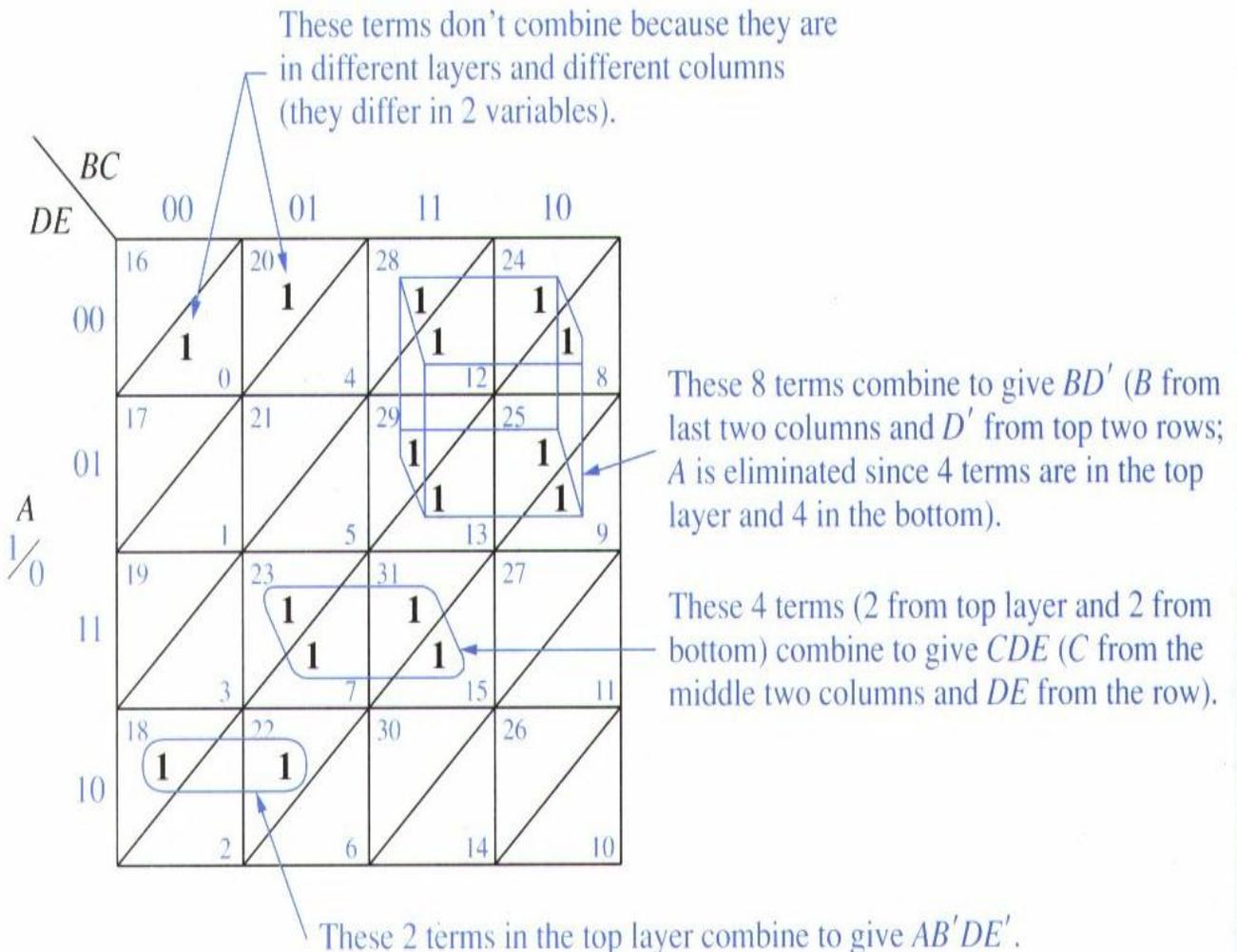- A' in the bottom layer
- A in the top layer.




5 Neighbors

- Same plane and above or under

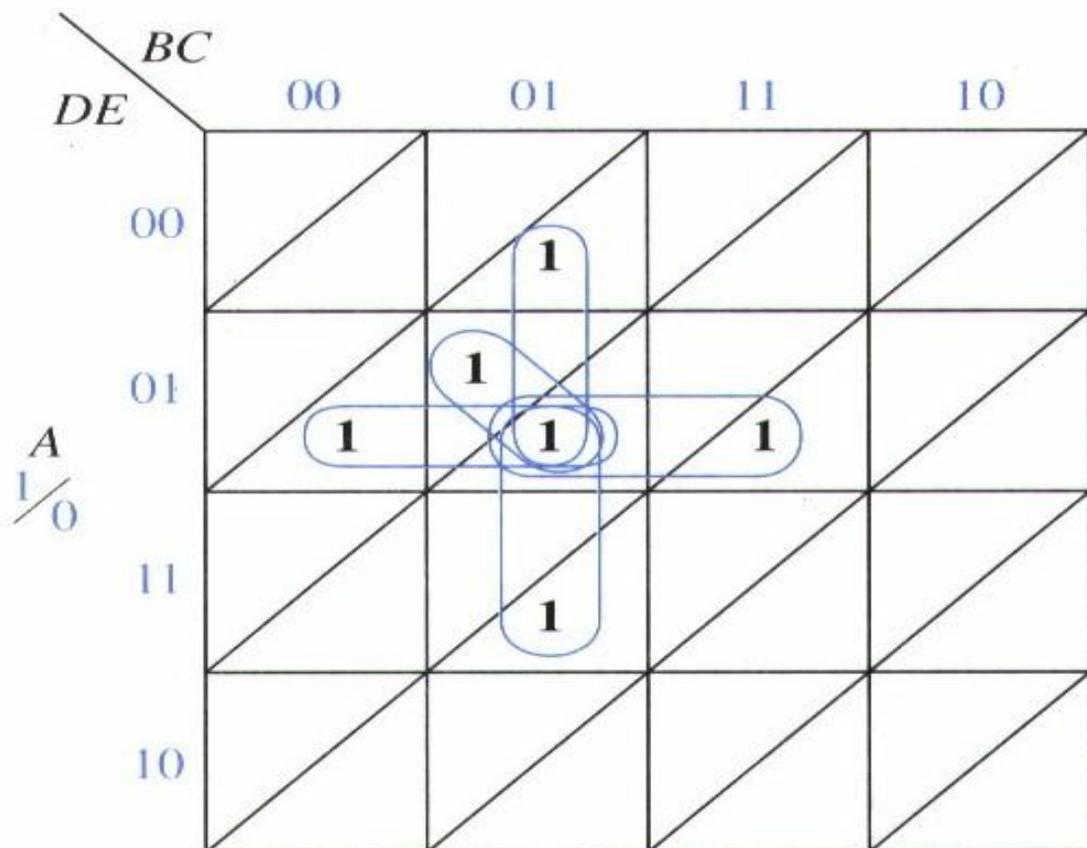

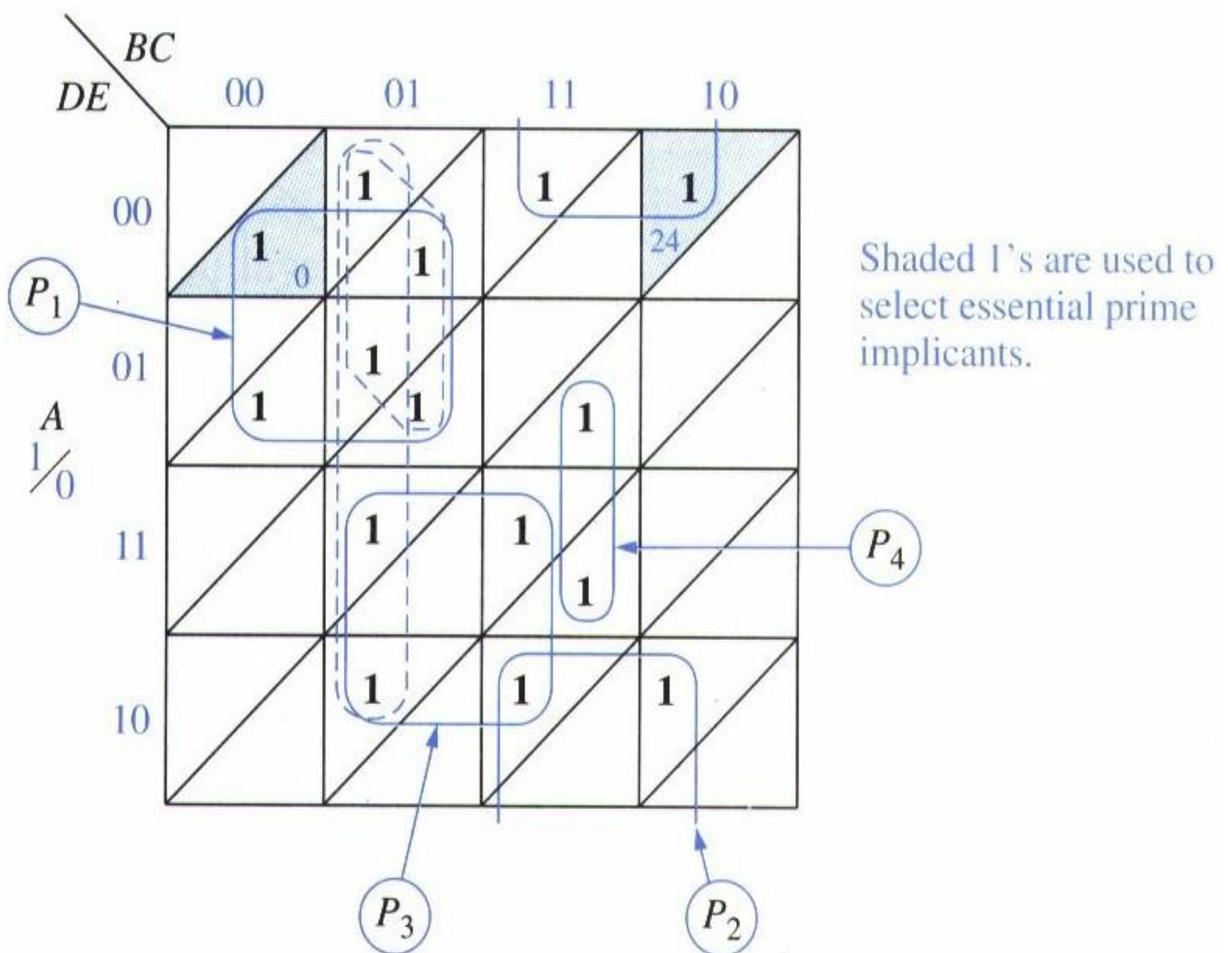
Example: 5-variables

- Ans: $F = A'B'D' + ABE' + ACD + A'BCE + \{AB'C \text{ or } B'CD'\}$
 $- P_1 + P_2 + P_3 + P_4 + AB'C \text{ or } B'CD'$



One More

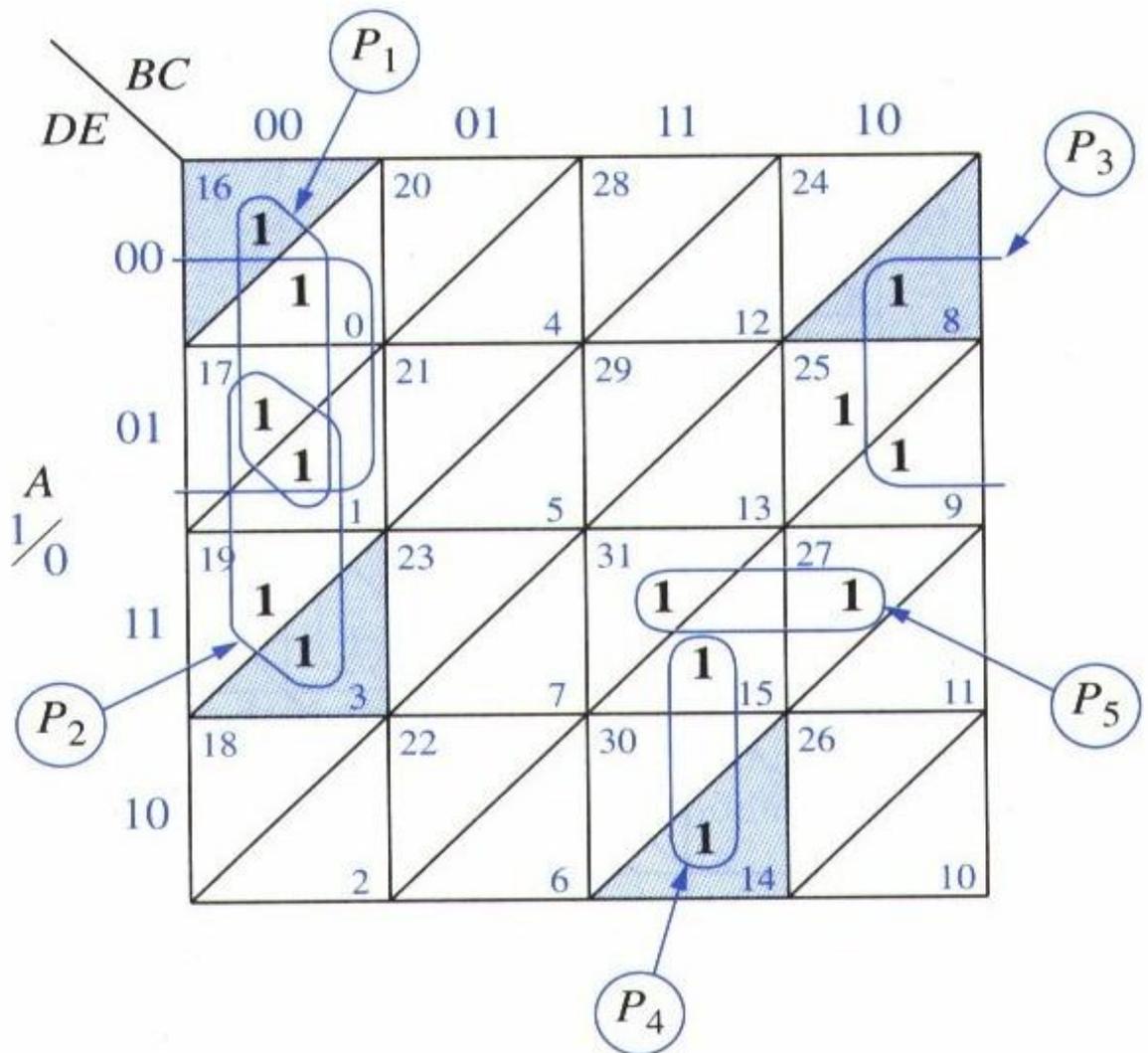- $F = B'C'D' + B'C'E + A'C'D' + A'BCD + ABDE + \{C'D'E \text{ or } AC'E\}$
- $(17,19,25,27 = AC'E), (1,9,17,25 = C'D'E)$



Simplification Using Map-Entered Variables

- Extend K-map for more variables.
 - When E appears in a square, if E = 1, then the corresponding minterm is present in the function G.
 - $G(A,B,C,D,E,F) = m_0 + m_2 + m_3 + Em_5 + Em_7 + Fm_9 + m_{11} + m_{15} + (\text{don't care terms})$

	AB			
CD	00	01	11	10
00	1			
01	X	E	X	F
11	1	E	1	1
10	1			X

G

(a)

	AB			
CD	00	01	11	10
00	1			
01	X		X	
11	1		1	1
10	1			X

$E = F = 0$

$$MS_0 = A'B' + ACD$$

(b)

	AB			
CD	00	01	11	10
00	X			
01	X	1	X	
11	X	1	X	X
10	X			X

$E = 1, F = 0$

$$MS_1 = A'D$$

(c)

	AB			
CD	00	01	11	10
00	X			
01	X		X	1
11	X		X	X
10	X			X

$E = 0, F = 1$

$$MS_2 = AD$$

(d)

Map-Entered Variable

- $F(A,B,C,D) = A'B'C + A'BC + A'BC'D + ABCD + (AB'C)$, (don't care)
 - Choose D as a map-entered variable.
 - When $D = 0$, $F = A'C$ (Fig. a)
 - When $D = 1$, $F = C + A'B$ (Fig. b)
 - two 1's are changed to x's since they are covered in Fig. a.
- $F = A'C + D(C+A'B) = A'C + CD + A'BD$

	<i>A</i>		
<i>BC</i>		0	1
00			
01		1	X
11		1	<i>D</i>
10		<i>D</i>	

(a)

	<i>A</i>		
<i>BC</i>		0	1
00			
01		X	X
11		X	1
10		1	

(b)

	<i>DA</i>				
<i>BC</i>		00	01	11	10
00					
01		1	X	X	1
11		1		1	1
10					1

(c)

General View for Map-Entered Variable Method

- Given a map with variables P1, P2 etc, entered into some of the squares, the minimum SOP form of F is as follows:
- $F = MS_0 + P_1 MS_1 + P_2 MS_2 + \dots$
where
 - MS₀ is minimum sum obtained by setting $P_1 = P_2 \dots = 0$
 - MS₁ is minimum sum obtained by setting $P_1 = 1$, $P_j = 0$ ($j \neq 1$), and replacing all 1's on the map with don't cares.
 - Previously, $G = A'B' + ACD + EA'D + FAD$.