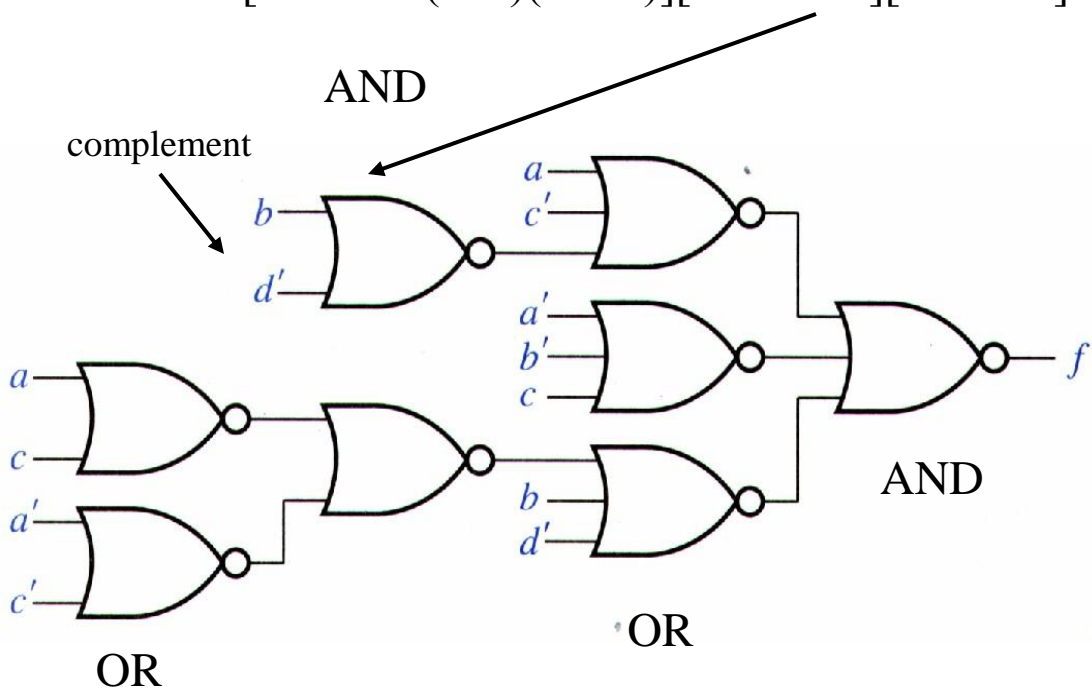


Lecture 8 Combinational Network Design and Issues

- Limited gate fan-in
 - Using 3-input NOR gates.
- **Example** : $f(a,b,c,d) = \Sigma m(0,3,4,5,8,9,10,14,15)$
 - $f = a'b'c'd + ab'cd + abc' + a'bc + a'cd'$ (2 4-input, 1 5-input)
 - $f = b'd(a'c' + ac) + a'c(b + d') + abc'$ (use common terms)
 - $f = [b + d' + (a+c)(a'+c')][a+c'+b'd][a'+b'+c]$



Multiple-Output With Limited Fan-In

- Using only 2-input NAND.

$$f_1 = b'c' + ab' + a'b$$

$$f_2 = b'c' + bc + a'b$$

$$f_3 = a'b'c + ab + bc'$$

- 3-input OR-gate

$$f_1 = b'(a+c') + a'b$$

$$f_2 = b(a'+c) + b'c' \text{ or } \underline{(b'+c)(b+c')} + a'b$$



↙ Choose this because of common term

$$f_3 = a'b'c + b(a+c') = a'(b+c')' + b(a+c')$$

↘ 3 inputs ↗ 2 inputs



Gate Delay

- Propagation delay
- Timing diagram

  

Network Delay

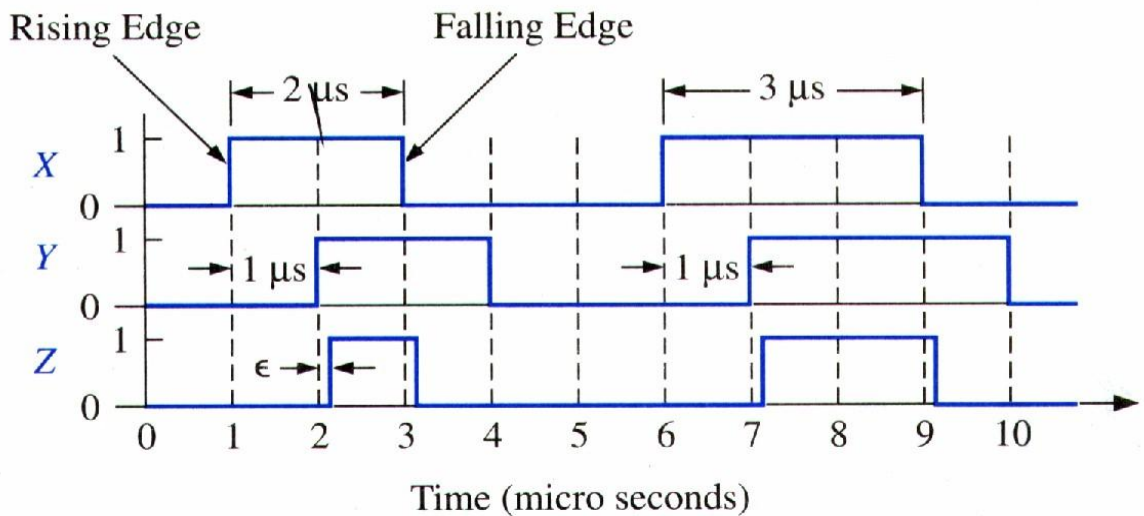 - Delay element
 - Extra logic circuit, capacitance.




Hazards

- Uncertain delays in logic circuits have the ability to introduce temporary or transient signal pulse where none are supposed to exist.
 - The spurious pulses or noise signals are referred to as **glitches**.
 - A **glitch** is a momentary error condition on the output of a circuit due to unequal signal delay paths in the circuit.
 - A glitch is identified as an additional pulse or pulses on output.
 - The circuit conditions that allow such signals to appear are called **hazards**.
 - A circuit with a hazard may or may not produce glitches, depending on the input patterns and the electrical characteristics of the circuit.

An Example of Hazard

- Propagation delays result in output transients.
 - When x_2 1 \rightarrow 0, the output should remain to 1.
 - But if G1 goes to 1 first, then (11) for G3 results in 0 output. Suppose that G2 has a longer delay, then (1,0) causes the output back to 1.

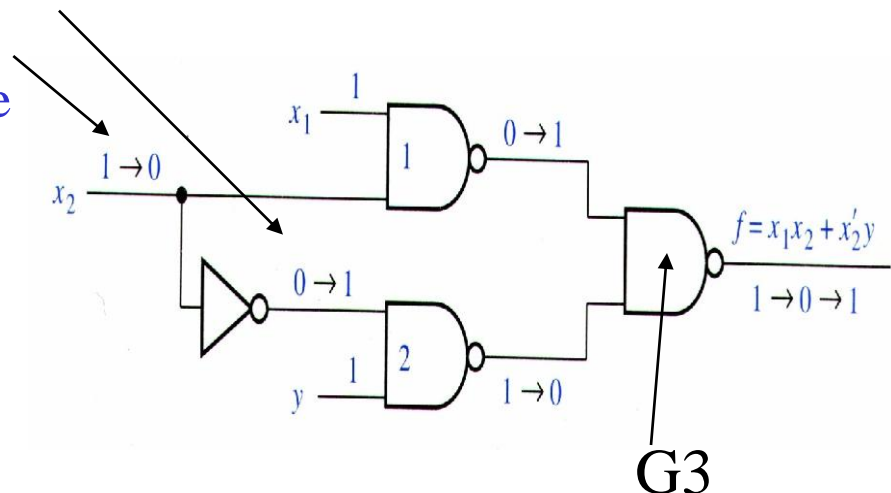
x_2 and x_2' have the same value for a short time.




Static and Dynamic Hazard

– Hazard

 
- In a combinational part of a sequential network, hazard can cause the sequential network to malfunction.
- Hazard in an output network can cause a problem if the output serves as the input to another asynchronous network.



(a) Static 1-hazard

 

(b) Static 0-hazard

 


(c) Dynamic hazards

Glitch Eliminations


- If the glitches are narrow in width, they might be filtered out by the **inertial property of physical gates**.
- Hazard controls are only feasible to fairly small circuits that operate under restrictive conditions.
 - Avoid multiple simultaneous input changes. (Restriction)

Hazard Detection

- 1-hazard

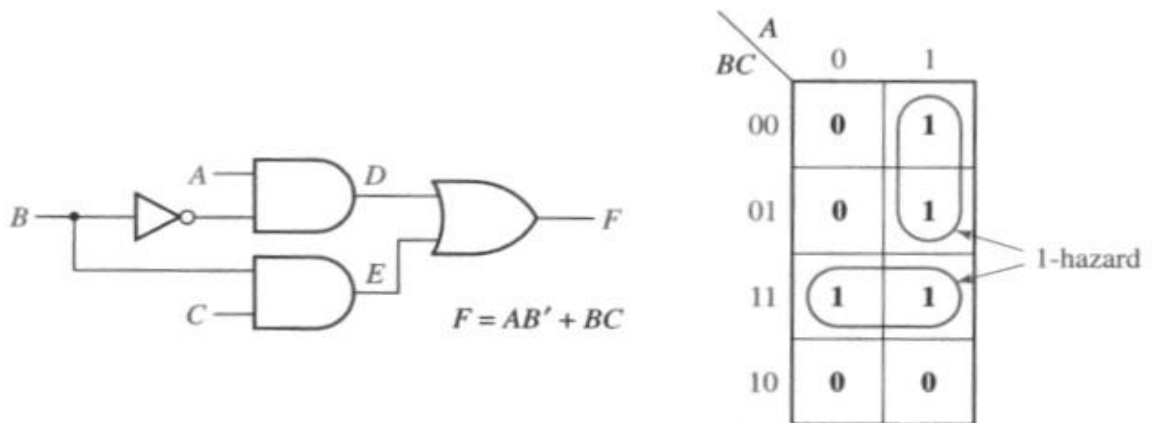


(a) Circuit with a static 1-hazard

 

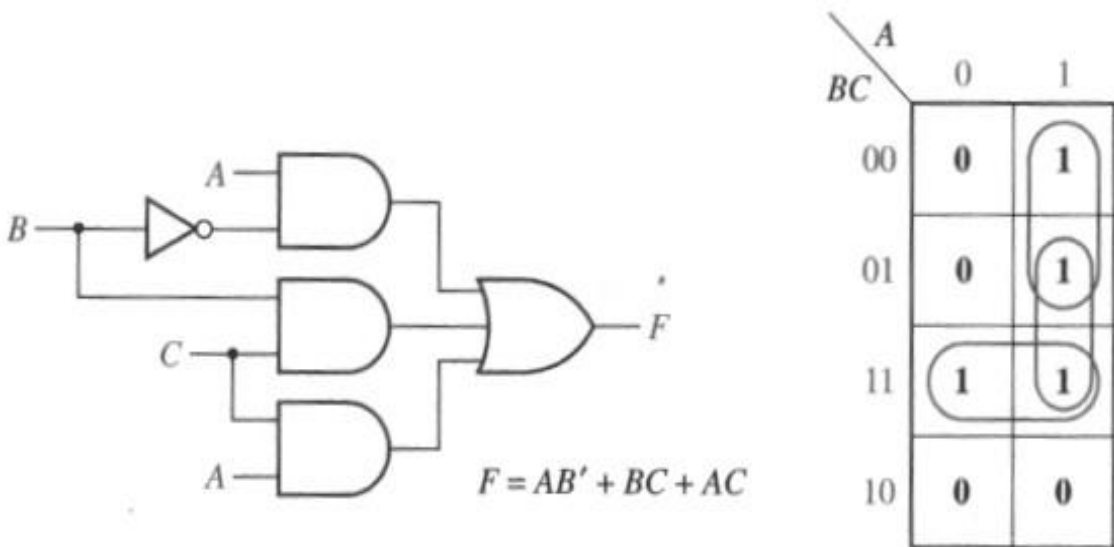(b) Timing chart


Remove the Hazard

- Add a redundant gate to remove the hazard.




Hazard Detection (cont.)


- Static 0-hazard

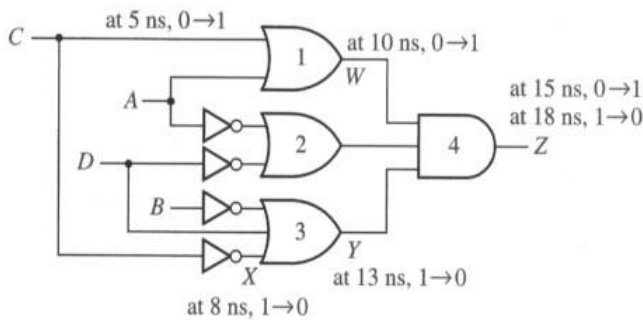

(a) Circuit with a static 0-hazard

 


(b) Karnaugh map for circuit of (a)

 

 (c) Timing diagram illustrating 0-hazard of (a)

Remove Hazard

- Looping additional prime implicants that cover the adjacent 0's that are not already covered by a common loop.



Possible Causes for Errors

- Incorrect design
- Gate connected wrong
- Wrong inputs to the network
- Defective gates
- Defective wires

stuck at zero

stuck at one