

# Lab 8

## Verilog – Sequential Design(3)

Johnson Liu



Department of Electrical Engineering  
National Cheng Kung University

# Outline

1. Finite-State Machine (FSM)
  - Moore Machine
  - Mealy Machine
2. Traffic Light
3. TA Checking & Laboratory Report
4. Reference

# Recall: Blocking vs. Non-Blocking

Name	Blocking	Non-Blocking
Symbol	=	<=
Ordering	Order Sensitive	Order Independent
Always Block Type	Combinational Block	Sequential Block
LHS Synthesize Result	Wire	Register (Memory element)

# Recall: Blocking vs. Non-Blocking

## 1. Blocking

initial  
begin

...  
A = 1;  
B = 0;

...  
A = B;  
B = A;

B = 0 is used  
A = 0 is used

initial  
begin

...  
A = 1;  
B = 0;

...  
B = A;  
A = B;

A = 1 is used  
B = 1 is used

## 2. Non-Blocking

initial  
begin

...  
A <= 1;  
B <= 0;

...  
A <= B;  
B <= A;

B = 0 is used  
A = 1 is used

initial  
begin

...  
A <= 1;  
B <= 0;


...  
B <= A;  
A <= B;

A = 1 is used  
B = 0 is used

# Finite-State Machine (FSM)

 
# Finite-State Machine(FSM)

- 在進行控制電路(Controller)的設計時，可以使用FSM的方式設計。
- 將電路的行為切分為數個state，並定義每個state的行為以及state間轉換的條件。
- 可分為Moore & Mealy 兩種machine。




# Moore vs Mealy

- Moore machine : Output只由當前的state決定。

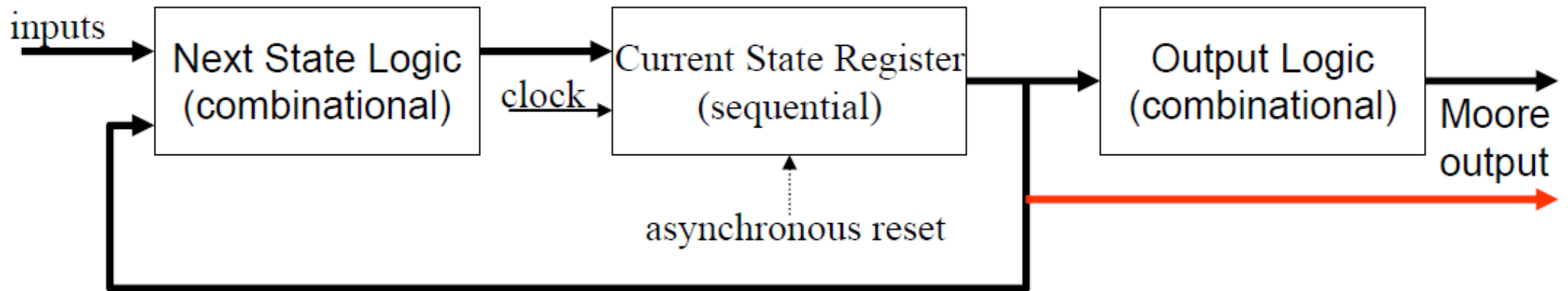
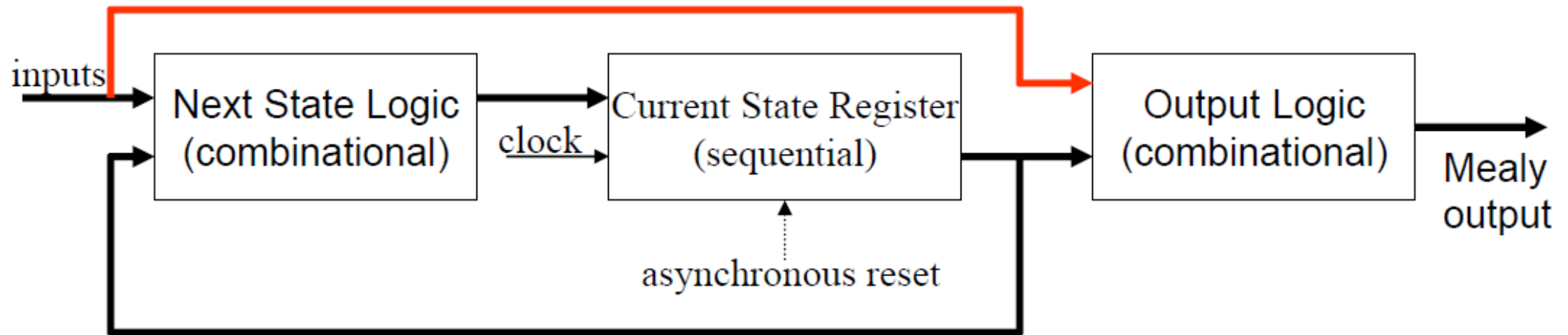
# Moore vs Mealy

- Mealy machine : Output由當前的state和input決定。






- **Verilog Example**

# Moore Machine


- Moore machine is a finite-state machine whose output values are determined only by its current state.
- Moore machine:  $S \rightarrow O$  (  $S$  : state,  $O$ : output )

Present State	Next State		Output	
	I=0	I=1	I=0	I=1
$S_0$	$S_0$	$S_2$	0	0
$S_1$	$S_0$	$S_2$	1	1
$S_2$	$S_2$	$S_3$	1	1
$S_3$	$S_3$	$S_1$	0	0

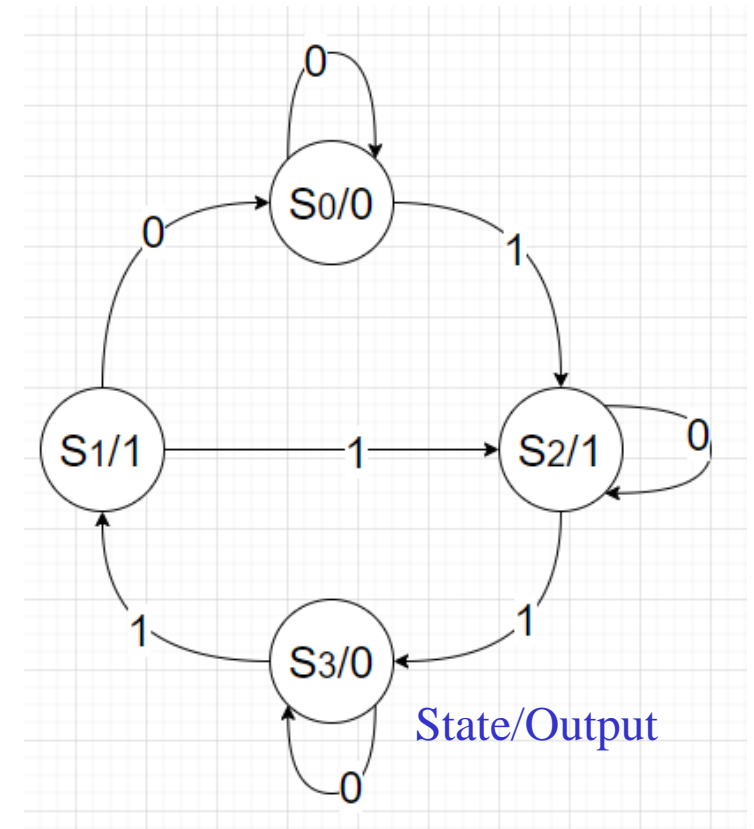
 
# Moore - State Register (Sequential)


```
module moore(clk, rst, In_Data, Out_Data);
  input clk, rst, In_Data;
  output [1:0] Out_Data;
  reg [1:0] Out_Data;
  reg [1:0] State, NextState;
  parameter S0 = 2'b00, S1 = 2'b01,
            S2 = 2'b10, S3 = 2'b11;
  // State Register (Flip-Flops)
  always @(posedge clk or posedge rst)
  begin
    if(rst)
      State <= S0;
    else
      State <= NextState;
  end
end
```


 
# Moore - Next State Logic (Combinational)


```
// Next State Logic
always @(In_Data or State)
begin
  case(State)
    S0:
    begin
      if(In_Data == 1)
        NextState = S2;
      else
        NextState = S0;
    end
    S1:
    begin
      if(In_Data == 1)
        NextState = S2;
      else
        NextState = S0;
    end
  endcase
end
```

```
S2:
begin
  if(In_Data == 1)
    NextState = S3;
  else
    NextState = S2;
end
S3:
begin
  if(In_Data == 1)
    NextState = S1;
  else
    NextState = S3;
end
endcase
```


 
# Moore - Output Logic (Combinational)

```
// Output Logic
always @(State)
begin
    case(State)
        S0:Out_Data = 0;
        S1:Out_Data = 1;
        S2:Out_Data = 1;
        S3:Out_Data = 0;
    endcase
end
endmodule
```



# Moore - Bad Example (All Sequential)

```

module moore_bad(clk, rst, In_Data, Out_Data);
  input clk, rst, In_Data;
  output [1:0] Out_Data;
  reg [1:0] Out_Data;
  reg [1:0] State;
  parameter S0 = 2'b00, S1 = 2'b01,
            S2 = 2'b10, S3 = 2'b11;
  always @(posedge clk)
  begin
    if(rst)
      case(State)
        S0:
          State <= S0;
      end
    else
      begin
        Out_Data <= 0;
        if(In_Data == 1)
          State <= S2;
        else
          State <= S0;
        end
      end
    end
  end
end

```

```


S1:
begin
  Out_Data <= 1;
  if(In_Data == 1)
    State <= S2;
  else
    State <= S0;
  end
S2:
begin
  Out_Data <= 1;
  if(In_Data == 1)
    State <= S3;
  else
    State <= S2;
  end
end

```


```

S3:
begin
  Out_Data <= 0;
  if(In_Data == 1)
    State <= S1;
  else
    State <= S3;
  end
end


```

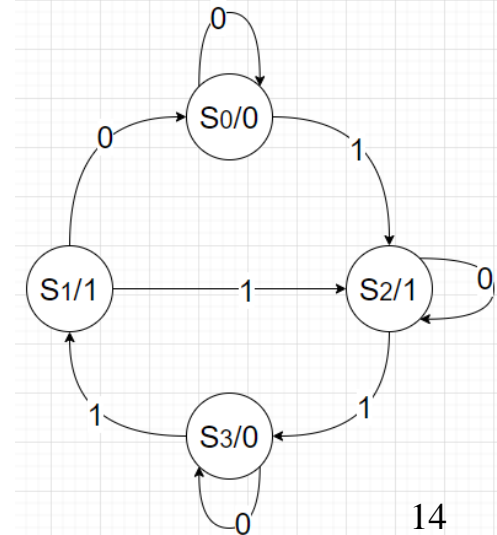


# Moore Waveform

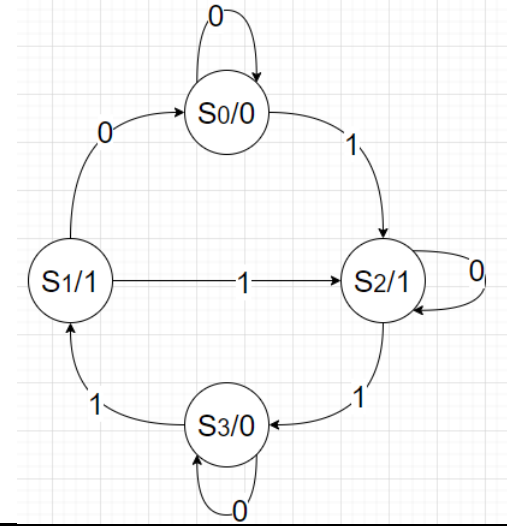

- Good Moore

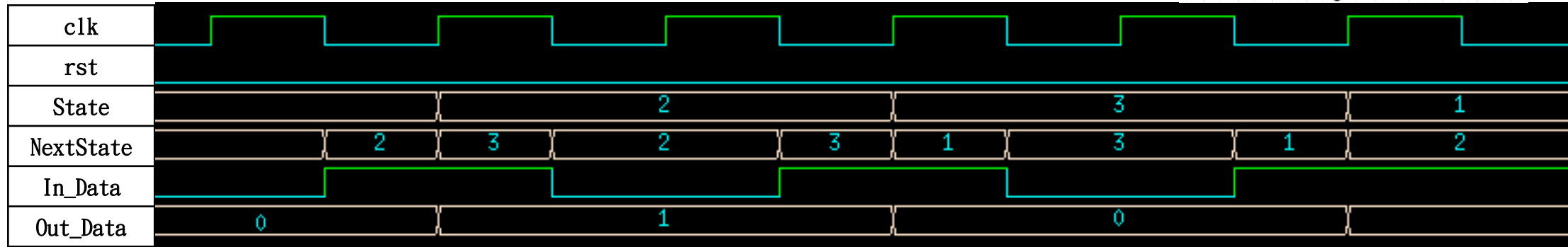

- Bad Moore Output delay 了 1個cycle

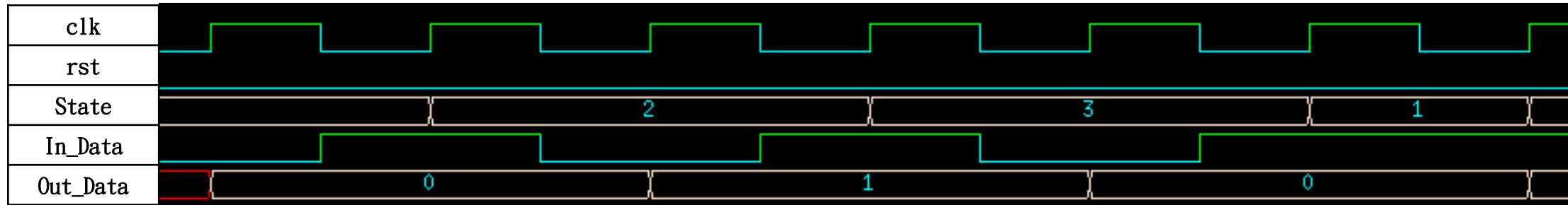

- **Mealy Machine**




# Mealy Machine

- Mealy machine is a finite-state machine whose output values are determined both by its current state and the current inputs.
- Mealy machine:  $S \times I \rightarrow O$  (S : state, I: Input, O: output )

Present State	Next State		Output	
	I=0	I=1	I=0	I=1
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0	1
S <sub>1</sub>	S <sub>1</sub>	S <sub>2</sub>	1	0
S <sub>2</sub>	S <sub>2</sub>	S <sub>0</sub>	0	1
S <sub>3</sub>	S <sub>3</sub>	S <sub>1</sub>	0	1

Four states: S<sub>0</sub>, S<sub>1</sub>, S<sub>2</sub>, S<sub>3</sub>

Input/Output

 


# Mealy - State Register (Sequential)

```

module mealy(clk, rst, In_Data, Out_Data);
  input clk, rst, In_Data;
  output [1:0] Out_Data;
  reg [1:0] Out_Data;
  reg [1:0] State, NextState;
  parameter S0 = 2'b00, S1 = 2'b01,
            S2 = 2'b10, S3 = 2'b11;
  // State Register (Flip-Flops)
  always @(posedge clk or posedge rst)
  begin
    if(rst)
      State <= S3;
    else
      State <= NextState;
  end
end

```

 Four states:  $S_0, S_1, S_2, S_3$   
Input/Output



# Mealy - Next State Logic (Combinational)

```
// Next State Logic
always @(In_Data or State)
begin
```

```
  case(State)
```

```
    S0:
```

```
    begin
```

```
      if(In_Data == 1)
```

```
        NextState = S1;
```

```
      else
```

```
        NextState = S0;
```

```
    end
```

```
    S1:
```

```
    begin
```

```
      if(In_Data == 1)
```

```
        NextState = S2;
```

```
      else
```

```
        NextState = S1;
```

```
    end
```

```
    S2:
```

```
    begin
```

```
      if(In_Data == 1)
```

```
        NextState = S0;
```

```
      else
```

```
        NextState = S2;
```

```
    end
```

```
    S3:
```

```
    begin
```

```
      if(In_Data == 1)
```

```
        NextState = S1;
```

```
      else
```


```
        NextState = S3;
```

```
    end
```

```
  endcase
```

Four states:  $S_0, S_1, S_2, S_3$

Input/Output

 


# Mealy - Output Logic (Combinational)

```
// Output Logic
always @(In_Data or State)
begin
  case(State)
    S0:
      begin
        if(In_Data == 1)
          Out_Data = 1;
        else
          Out_Data = 0;
      end
    S1:
      begin
        if(In_Data == 1)
          Out_Data = 0;
        else
          Out_Data = 1;
      end
  endcase
end
```

```
S2:
begin
  if(In_Data == 1)
    Out_Data = 1;
  else
    Out_Data = 0;
end
S3:
begin
  if(In_Data == 1)
    Out_Data = 1;
  else
    Out_Data = 0;
end
endcase
```

 Four states:  $S_0, S_1, S_2, S_3$   
Input/Output




# Mealy Waveform

clk												
rst												
State	3	1		2			0		1		2	
NextState	1	2	1	2	0	2	0	1	0	1	2	
In_Data	1		0			1		0		1		
Out_Data	1	0	1	0	1	0	1	0	1	0	1	


Four states:  $S_0, S_1, S_2, S_3$

Input/Output

 


# Example : Traffic Light

# Traffic Light Circuit

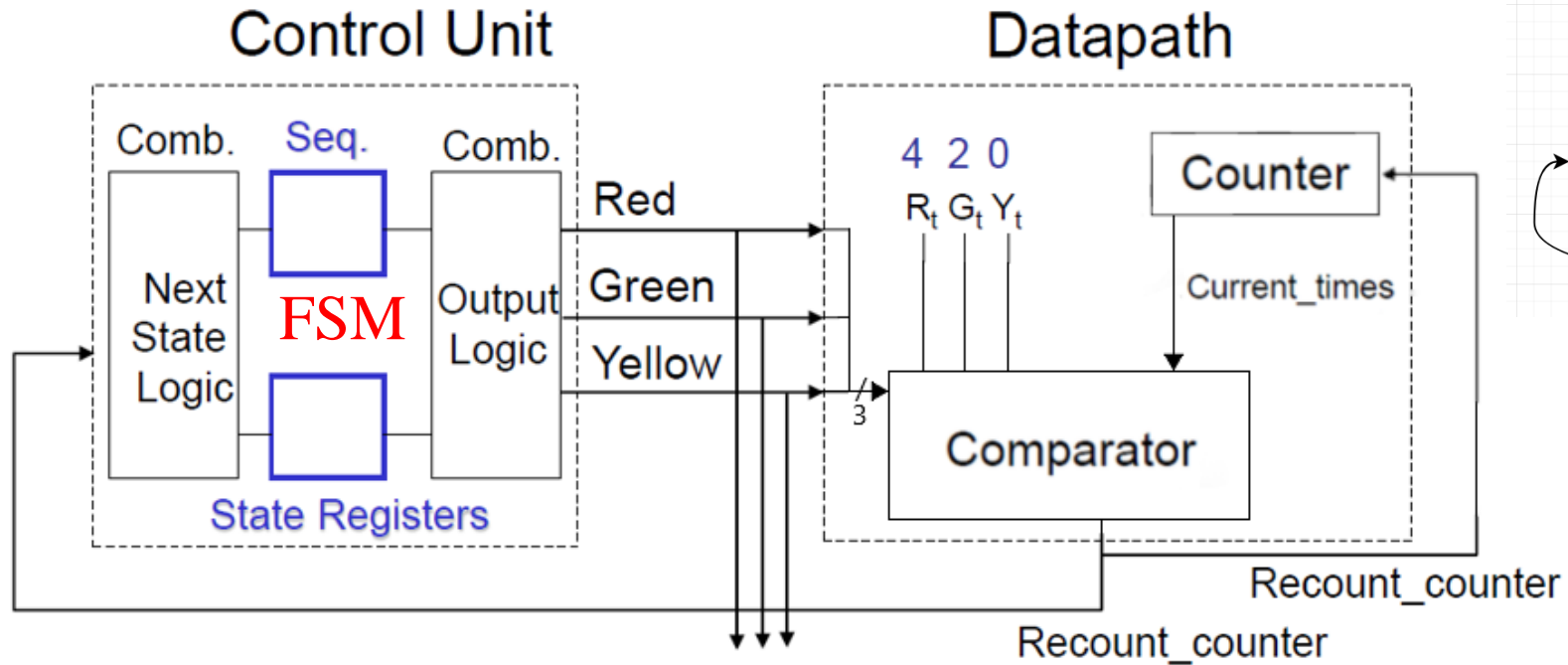


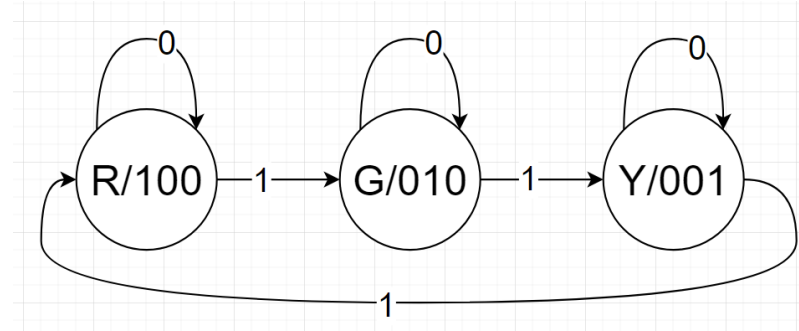R\_time:  $4+1=5$  cycles  
 G\_time:  $2+1=3$  cycles  
 Y\_time:  $0+1=1$  cycles


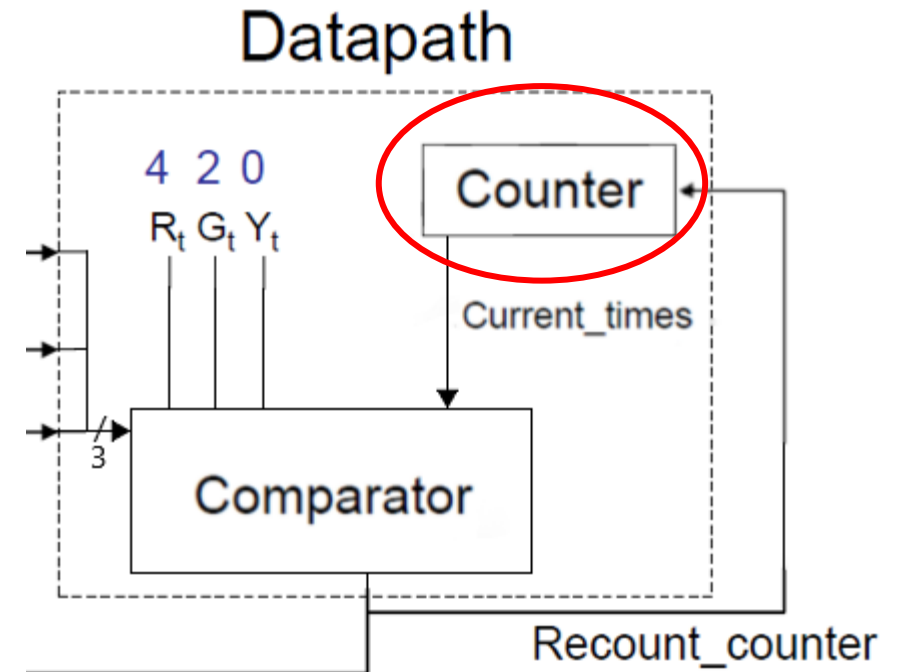
# Datapath – Counter (Sequential)

```
module Counter(clk, rst, Recount_Counter, Count_Out);  
  input clk, rst, Recount_Counter;  
  output [3:0] Count_Out;  
  reg [3:0] Count_Out;  
  always @(posedge clk)  
  begin  
    if(rst)  
    begin  
      Count_Out <= 0;  
    end  
    else  
    begin  
      if(Recount_Counter)  
        Count_Out <= 0;  
      else  
        Count_Out <= Count_Out + 1;  
    end  
  end  
end
```






# Datapath – Comparator (Combinational)

```

module Compare(current_times, RGY, Recount_counter);
  input [2:0] RGY;
  input [3:0] current_times;
  output Recount_counter;
  reg Recount_counter;
  parameter R_times = 4,
            G_times = 2,
            Y_times = 0;

  always @(*)
  begin
    case(RGY)
      3'b100:
        begin
          if(current_times == R_times)
            Recount_counter = 1;
          else
            Recount_counter = 0;
        end
    end
  end
end

```

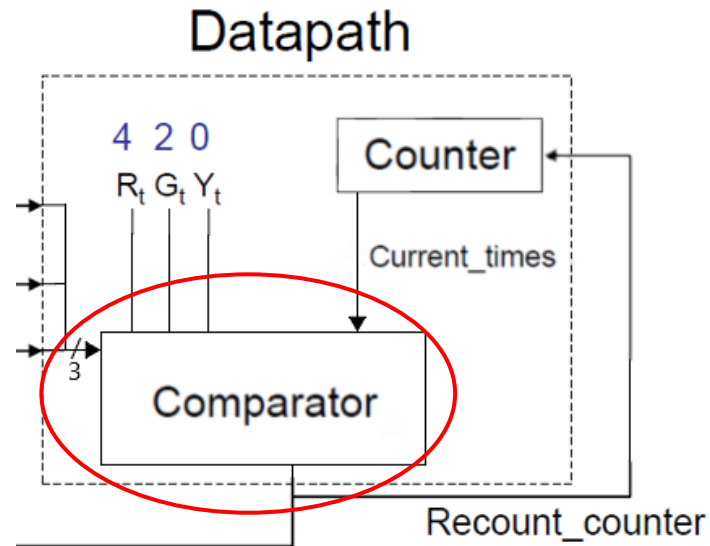

```

3'b001:
  begin
    if(current_times == Y_times)
      Recount_counter = 1;
    else
      Recount_counter = 0;
  end
3'b010:
  begin
    if(current_times == G_times)
      Recount_counter = 1;
    else
      Recount_counter = 0;
  end
default:
  Recount_counter = 1;
endcase


```

# Datapath

```


module Datapath(clk, rst, RGY, Recount);
  input clk, rst;
  input [2:0] RGY;
  output Recount;
  wire [3:0] Current_times;
  // Module
  Compare compare
  (
    .current_times(Current_times),
    .RGY(RGY),
    .Recount_counter(Recount)
  );
  Counter counter
  (
    .clk(clk),
    .rst(rst),
    .Recount_Counter(Recount),
    .Count_Out(Current_times)
  );
endmodule

```

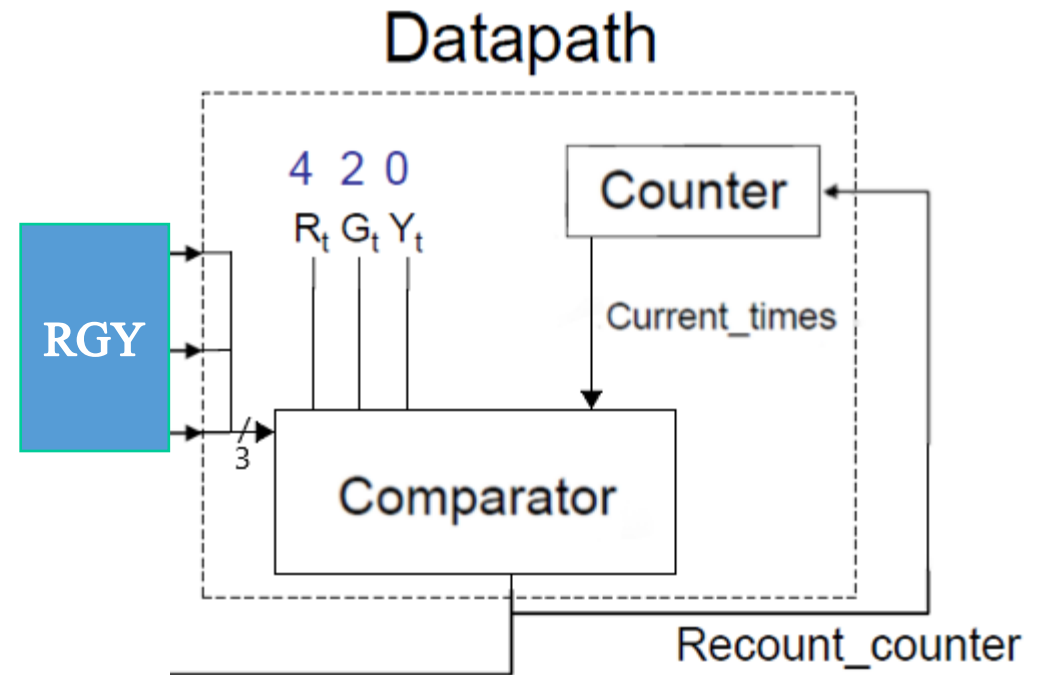

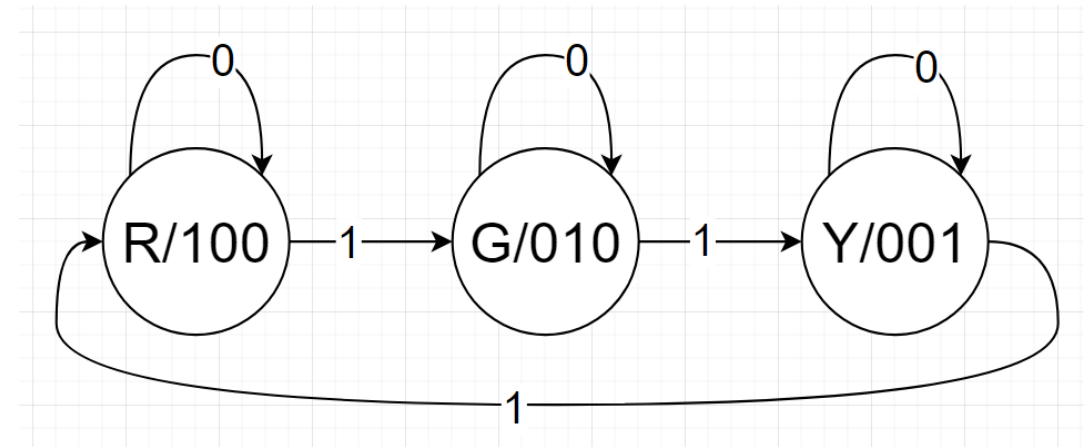
# Control Unit—State Register (Sequential)

```
module Traffic_Control (clk, rst, Recount_Counter, Red, Green, Yellow);  
  input clk, rst, Recount_Counter;  
  output Red, Green, Yellow;  
  reg Red, Green, Yellow;  
  reg [1:0] currentstate, nextstate;  
  parameter [1:0] Red_Light = 0,  
                Green_Light = 1,  
                Yellow_Light = 2;  
  // State Register (Flip-Flops)  
  always @(posedge clk)  
  begin  
    if(rst)  
      currentstate <= Red_Light;  
    else  
      currentstate <= nextstate;  
  end
```



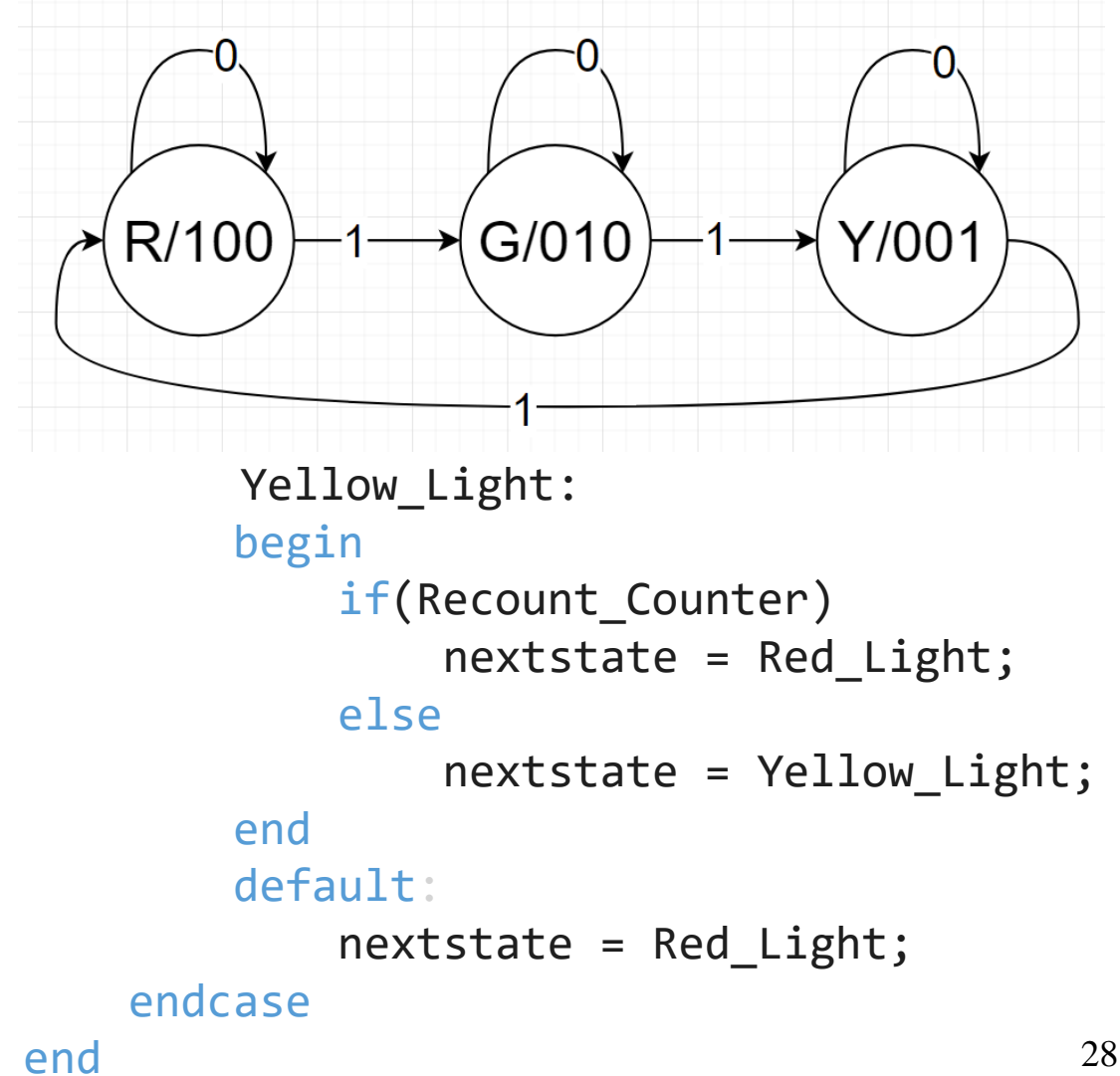
# Control Unit—Next State Logic (Combinational)

```
// Next State Logic
always @(*)
begin
  case(currentstate)
    Red_Light:
    begin
      if(Recount_Counter)
        nextstate = Green_Light;
      else
        nextstate = Red_Light;
    end
    Green_Light:
    begin
      if(Recount_Counter)
        nextstate = Yellow_Light;
      else
        nextstate = Green_Light;
    end
  end
end
```


 
# Control Unit—Output Logic (Combinational)

```
// Output Logic
always @(currentstate)
begin
    case(currentstate)
        Red_Light:
        begin
            Red = 1'b1;
            Green = 1'b0;
            Yellow = 1'b0;
        end
        Green_Light:
        begin
            Red = 1'b0;
            Green = 1'b1;
            Yellow = 1'b0;
        end
        Yellow_Light:
        begin
            Red = 1'b0;
            Green = 1'b0;
            Yellow = 1'b1;
        end
        default:
        begin
            Red = 1'b0;
            Green = 1'b0;
            Yellow = 1'b0;
        end
    endcase
end
```




# Combine Control Unit & Datapath

```

module traffic(clk, rst, Red, Green, Yellow);
  input clk, rst;
  output Red, Green, Yellow;
  wire Recount_counter;
  // Module
  Traffic_Control controller
  (
    .clk(clk),
    .rst(rst),
    .Recount_Counter(Recount_counter),
    .Red(Red),
    .Green(Green),
    .Yellow(Yellow)
  );

```

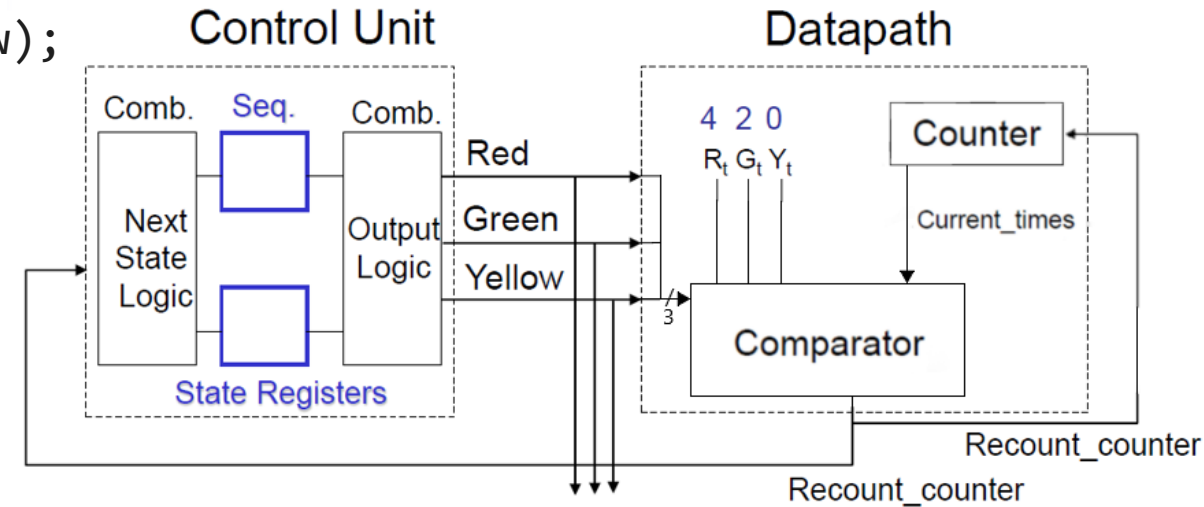

Datapath datapath


```

(
  .clk(clk),
  .rst(rst),
  .RGY({Red,Green,Yellow}),
  .Recount(Recount_counter)
);
endmodule


```

# Traffic Light Waveform

- Traffic Light

 

- Comparator

 

# Implementation(1)

## Microwave Oven



# Microwave Oven


- A microwave oven is an electric oven that heats and cooks food by exposing it to electromagnetic radiation in the microwave frequency range.
- This induces polar molecules such as water in the food to rotate and produce thermal energy in a process known as electronic heating.
- The first microwave oven was created by Percy Spencer who was hired by Raytheon in 1945. He was at that time one of the world's leading experts in radar tube design. When he was working on powered radar set, he noticed that a chocolate bar that he had in his pocket was melting.
- Mechanisms  
Heat the food by microwave within the fixed time.



# Implement Microwave Oven by State Machine

- Create a 10-bit register to store Count Down Time.
- **Only one button work each time.** If more than one button been activated, the button with **highest priority** will be chosen.
- Try to use following 4 States Moore Machine Template to create your own Finite State Machine. (**By adding new transition to the template**)
- 6 buttons on the control panel

Button Name	Priority
10 Minutes	1
1 Minute	2
10 Seconds	3
1 Second	4
Start	5
Pause	6

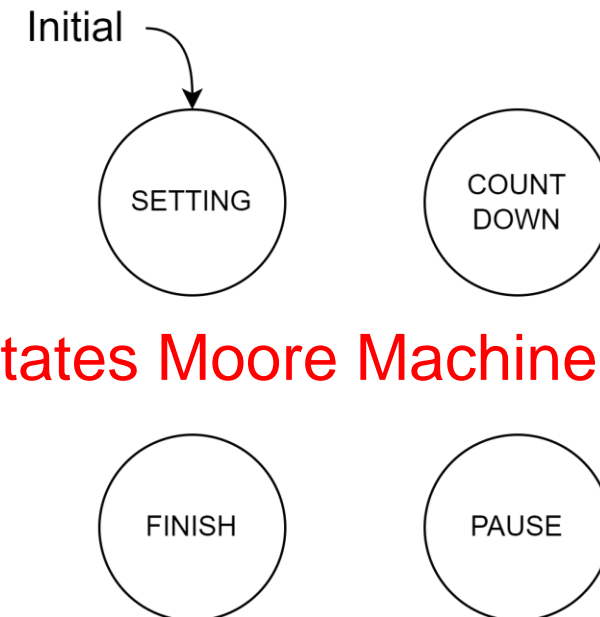

- **4 States Moore Machine Template**

# Implement Microwave Oven by State Machine

- *Setting*  
Set Count Down Time by Press **10 Minutes**, **1 Minute**, **10 Seconds**, or **1 Second** Button. Press **Pause** Button to reset Count Down Time to 0. Press **Start** Button to start microwave food and count down. **It is not necessary to microwave food and count down, if the Count Down Time is 0.**
- *Count Down*  
Microwave food and count down one second each cycle. Press **Pause** to pause count down. **It is not necessary to pause count down, if the Count Down Time is 0.**
- *Pause*  
Pause count down. Press **Pause** to stop microwave and reset Count Down Time to 0. Press **Start** to resume microwave food and count down.
- *Finish*  
Notify user microwave has finished by one cycle, then resume setting.


# Implement Microwave Oven by State Machine

- I/O Interface of Module Microwave in Microwave.v

Name	I/O	Width	Description
clk	I	1	System clock signal. This system is synchronized with the <b>positive edge</b> of the clock.
rst	I	1	Active-high <b>asynchronous</b> reset signal.
tenMinutes	I	1	High when 10 Minutes Button is pressed.
minute	I	1	High when 1 Minute Button is pressed.
tenSeconds	I	1	High when 10 Seconds Button is pressed.
second	I	1	High when 1 Second Button is pressed.
pause	I	1	High when Pause Button is pressed.
start	I	1	High when Start Button is pressed.
countDown	O	10	Show the Count Down Time.
finish	O	1	Show microwave has finished.

# Implement Microwave Oven by State Machine

- Waveform of Microwave Oven

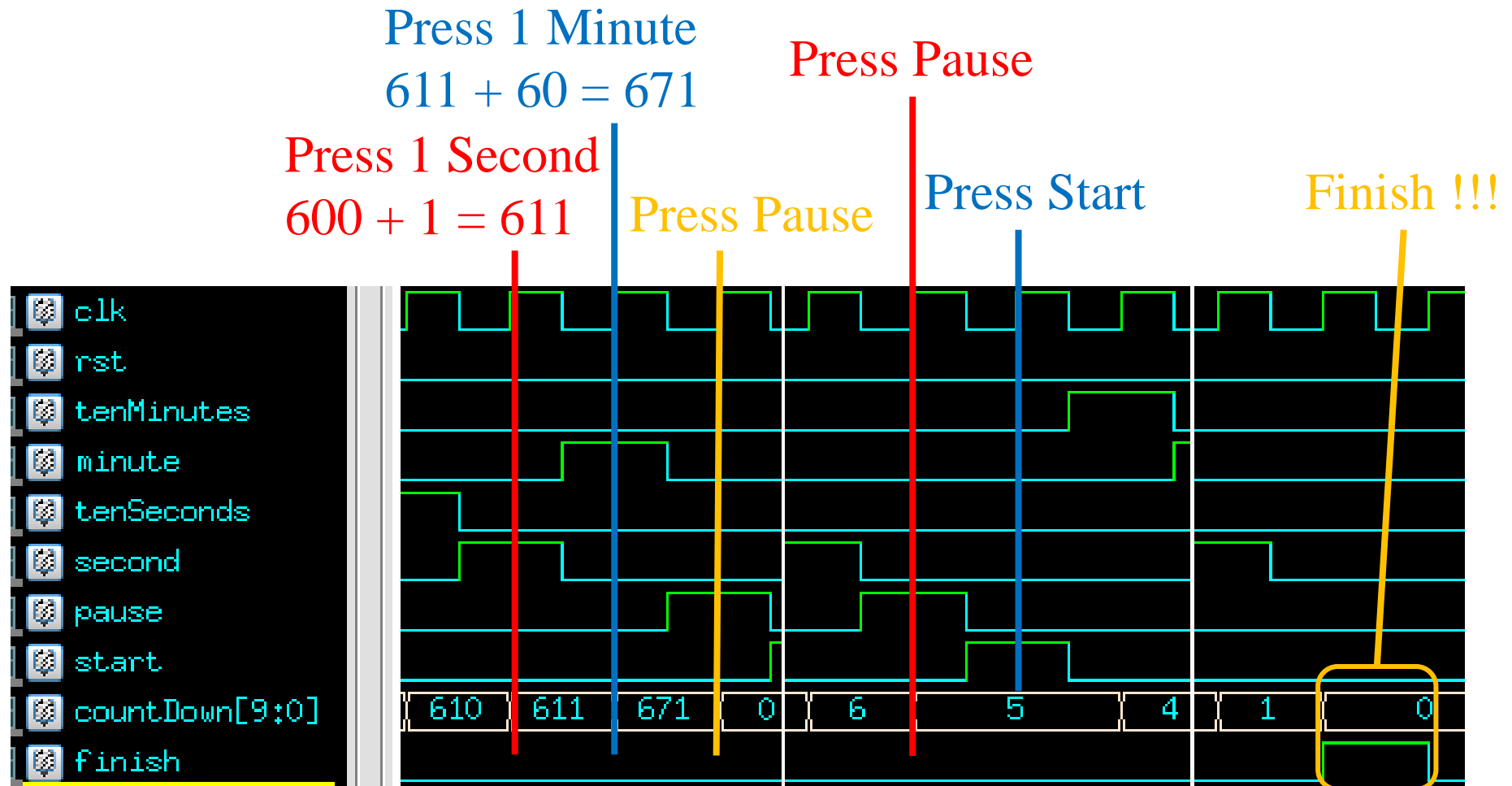

# Hint.

- 使用講義的state registers, next-state logic, output logic的範例進行改寫。(Moore machine)
- 使用if-else來設定按鈕的priority.
- 在setting state按下pause會reset倒數，在count down state按下則會暫停。

# **Implementation(2): Microwave Oven with Door**

# Implement Microwave Oven with Door

- Microwave Oven without door is very dangerous, because user would be microwaved and get burned.
- **Microwave Oven with Door inherits Implementation(1)'s functions.**
- Try to reuse Finite State Machine you created in Implementation(1), and add some constraints to transition.
- Setting  
**The *Start* Button is valid only when the *Door* is closed.**
- Count Down  
**Microwave food and count down can only proceed with the *Door* being closed.** If the ***Door*** is opened, the microwave oven will be forced to pause.
- Pause  
**The *Start* Button is valid only when the *Door* is closed.**




# Implement Microwave Oven with Door

- I/O Interface of Module Microwave in Microwave.v

Name	I/O	Width	Description
clk	I	1	System clock signal. This system is synchronized with the <b>positive edge</b> of the clock.
rst	I	1	Active-high <b>asynchronous</b> reset signal.
tenMinutes	I	1	High when 10 Minutes Button is pressed.
minute	I	1	High when 1 Minute Button is pressed.
tenSeconds	I	1	High when 10 Seconds Button is pressed.
second	I	1	High when 1 Second Button is pressed.
pause	I	1	High when Pause Button is pressed.
start	I	1	High when Start Button is pressed.
door	I	1	High when Door is closed.
countDown	O	10	Show the Count Down Time.
finish	O	1	Show microwave has finished.

# Implement Microwave Oven with Door

- Waveform of Microwave Oven

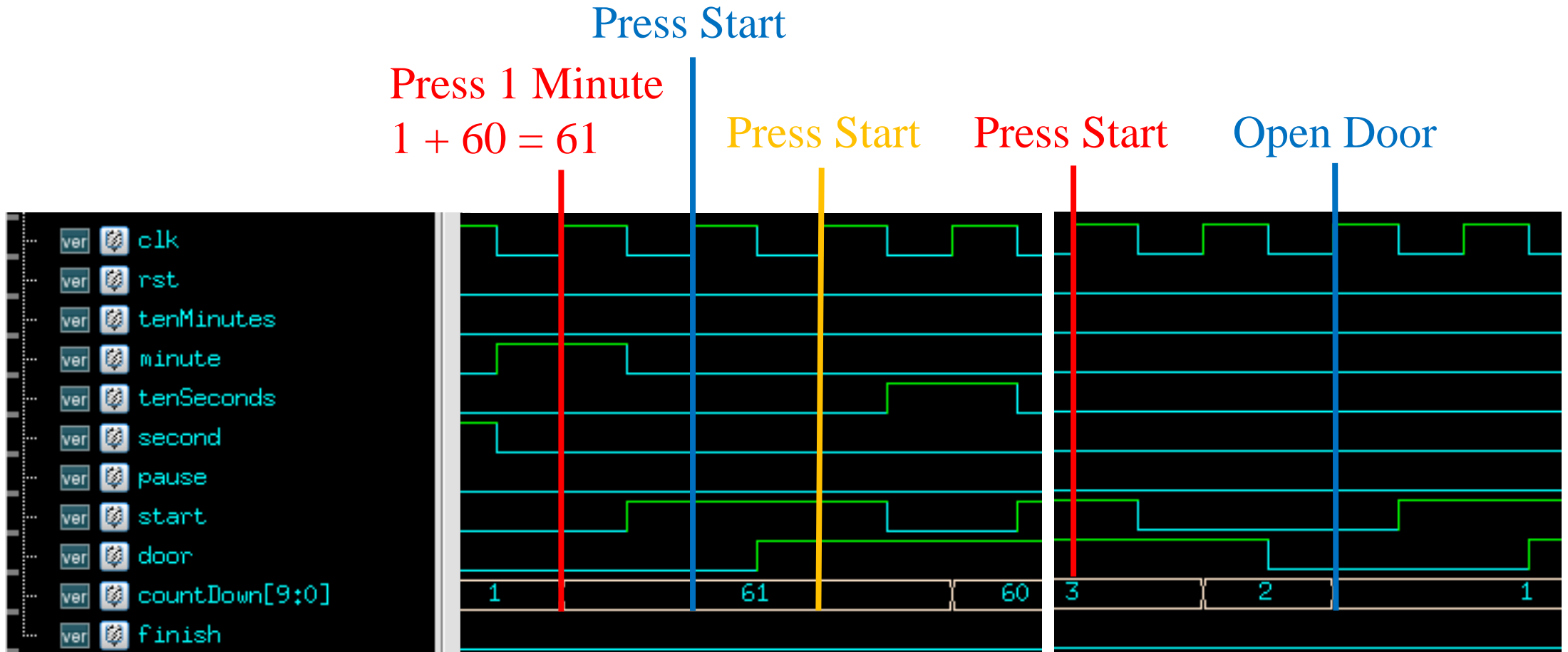

# TA Checking & Laboratory Report

# TA Checking & Laboratory Report

- TA Checking
  1. Implementation(1)'s Code & Pass Result
  2. Implementation(2)'s Code & Pass Result
- Laboratory Report
  1. Implementation(1)'s Finite State Machine and waveform
  2. Implementation(2)'s Finite State Machine and waveform
  3. How do you think about this time's laboratory class?

# Reference

# Reference

- Finite-State Machine (FSM): <https://reurl.cc/ye4gyM>
- Verilog HDL Design: <https://pse.is/3rypr5>

**Thank for Listening**