

Example Report

(格式不用一模一樣，只是列出 report 要求的五個點大概所需之內容)


a. Introduce how you define the circuit

- 此 sequence detector 為 overlap one pattern 的 sequence detector。
- 可以偵測連續不同 cycle 的輸入，當連續三個 cycle 拿到的值為 101 時，下一個 cycle 就會輸出 1

.....

.....

- 電路 input/output port :

 

```
module SQD (  
    clk,  
    rst,  
    in_data,  
    out_data,  
);  
  
input clk,rst,in_data;  
output out_data;
```

in_data : ...


clk :

rst :


out_data :

b. State machine and hardware block diagram

- State machine

 

- Block diagram

 

- Asynchrone reset 的電路，程式碼怎麼實現.....
-

c. Verify

寫了 c++ 程式碼產生 input 輸入給 testbench 跟對應的 golden 驗證結果是不是正確，解釋程式碼...

....

d. Result

```
=====
START!!! Simulation Start .....
=====
input= 1, out data equal to 0
input= 0, out data equal to 0
input= 1, out data equal to 0
input= 1, out data equal to 1
input= 1, out data equal to 0
input= 0, out data equal to 0
input= 1, out data equal to 0
input= 1, out data equal to 1
input= 0, out data equal to 0
input= 1, out data equal to 0
=====
Simulation END, SUCCESS!!!
=====
```

這是在 terminal 輸成功的結果，output 正確

```
=====
START!!! Simulation Start .....
=====
input= 1, out data equal to 0
input= 0, out data is 1 but golden is 0
input= 1, out data equal to 0
input= 1, out data equal to 1
input= 1, out data is 1 but golden is 0
input= 0, out data is 1 but golden is 0
input= 1, out data equal to 0
input= 1, out data equal to 1
input= 0, out data is 1 but golden is 0
input= 1, out data equal to 0
=====
Simulation END, there are some errors.....
=====
```

驗證失敗的結果 會顯示應該正確的值...

....

....

e. What you learn

....

....